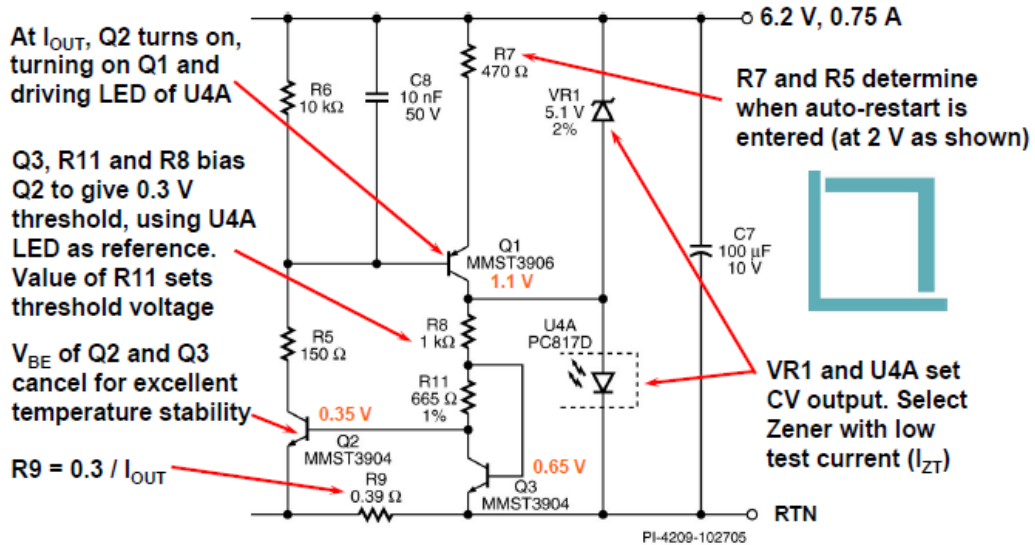


LowDrop-CC™ (0.3 V) CV/CC Feedback Circuit



- **Example of the value of *PI* external intellectual property**
 - This circuit can be employed with no royalty to *PI* when *PI* parts are used in the circuit