

# DI-61 Design Idea

## TinySwitch-II

### 3 W Charger: <200 mW No-load Consumption

Application	Device	Power Output	Input Voltage	Output Voltage	Topology
Charger	TNY264PN	3 W	85 – 265 VAC	5 V, 600 mA	Flyback

#### Design Highlights

- Less than 200 mW no-load power consumption (for 115 or 230 VAC input)
- Meets CISPR-22 Class B without Y capacitor
- Low cost, low component count solution

#### Operation

The TinySwitch-II flyback converter in Figure 1 generates a constant voltage, constant current (CV/CC) 5 V, 600 mA output. Typical applications include wall-mounted chargers for cell phones, PDAs and other battery powered portable equipment.

The key performance characteristic of the circuit shown is the extremely low no-load consumption of <200 mW. A linear transformer charger of similar rating will typically consume 1 W to 4 W at no-load. At \$0.12/kWh, the TinySwitch-II can therefore reduce energy costs by \$1 to \$4 per year.

The no-load performance is achieved by use of TinySwitch-II, and by careful transformer design.

The circuit meets CISPR-22 Class B conducted EMI limits without a Y capacitor, and therefore has very low AC leakage current. This EMI performance is achieved via the TinySwitch-II internal jitter, use of a shield winding, an output RC snubber, and the primary RCD clamp.

#### Key Design Points

- Minimize secondary circuit bias currents. Use low current feedback Zeners for best tolerance. The very low Zener bias current in this design will provide approximately  $\pm 10\%$  output voltage tolerance. A precision reference (e.g. TL431) can be used if higher precision is required.
- Design transformer with low reflected voltage to minimize clamp losses. A larger device (TNY266) may allow further reduction in  $V_{OR}$ .
- Wind transformer for lowest leakage inductance. Choose wire gauges to completely fill winding layers.
- Winding the transformer with tape between primary layers further reduces intra-winding capacitance and no-load consumption.
- Resistor R7 limits the peak current into the optocoupler LED to prevent damage during unusual transients.

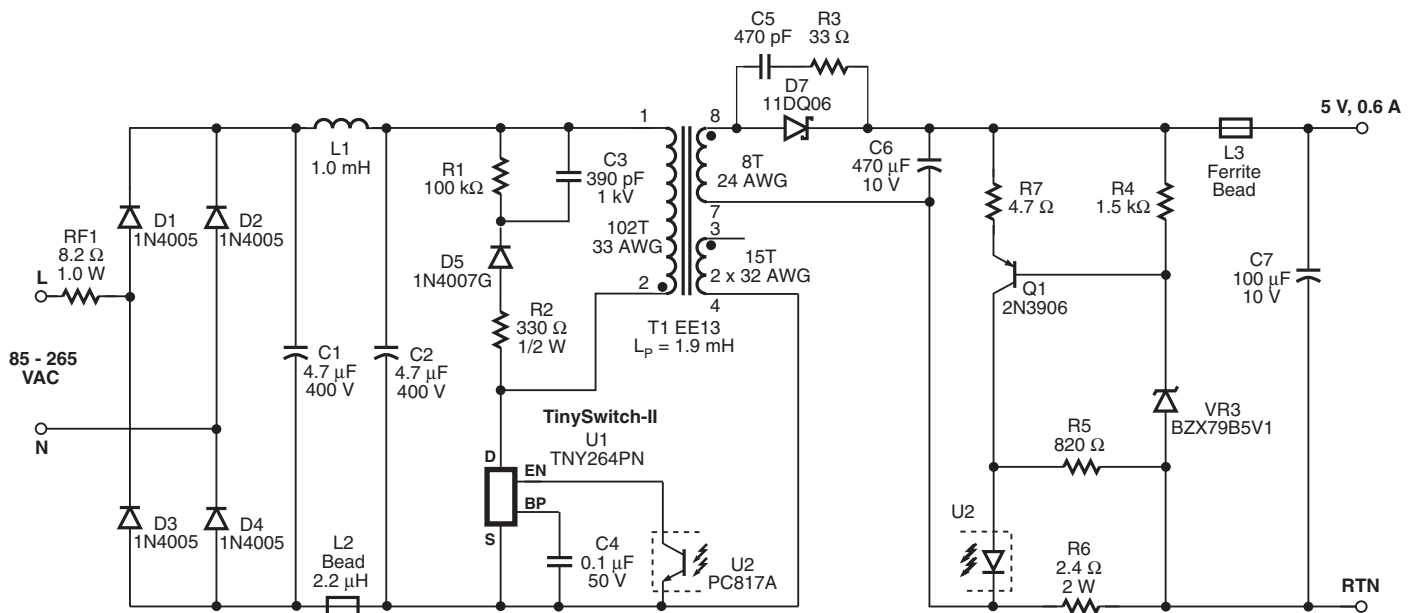


Figure 1. TinySwitch-II 3 W Cell Phone Charger.

PI-3681-102108

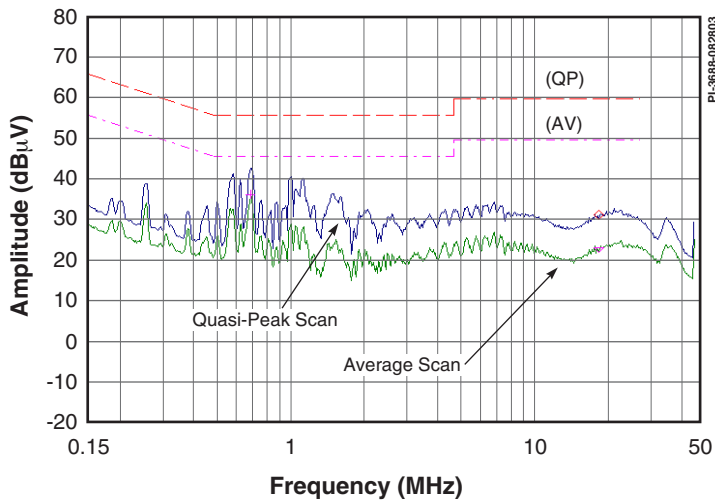


Figure 2. Conducted EMI, Full Load, 230 VAC, Grounded to "Artificial Hand" of LISN.

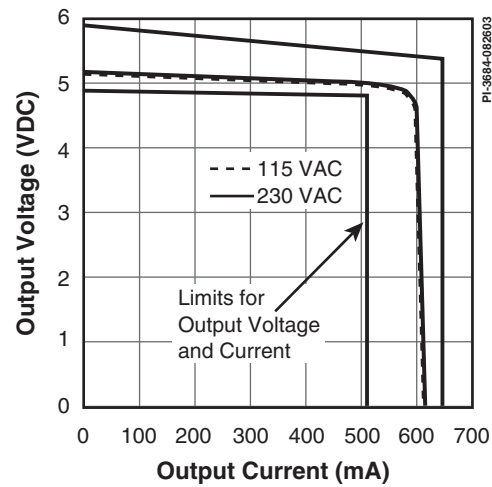


Figure 4. 5.0 VDC, 600 mA CV/CC Curve.

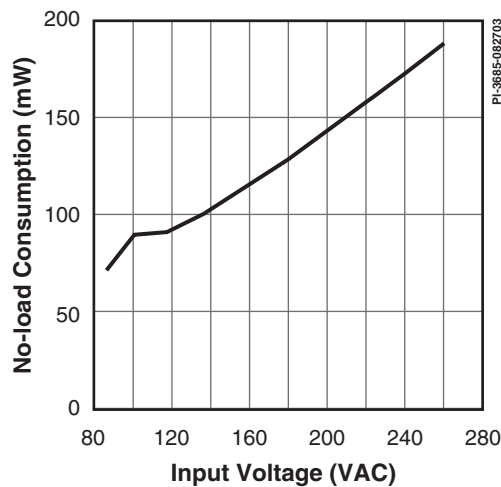


Figure 3. No-load Input Power vs. Line Voltage.

### Transformer Parameters

<b>Core Material</b>	EE13 TDK PC40 or equivalent, gapped for ALG of 128 nH/t <sup>2</sup>
<b>Bobbin</b>	EE13, 8 pin
<b>Winding Order (pin numbers)</b>	Primary (1-2), tape, Bias (3-4), tape, Secondary (7-8), 5 V, tape
<b>Primary Inductance</b>	1.9 mH, $\pm 10\%$
<b>Primary Resonant Frequency</b>	500 kHz (minimum)
<b>Leakage Inductance</b>	50 $\mu$ H (maximum)

Table 1. Transformer Parameters.

Power Integrations  
 5245 Hellyer Avenue  
 San Jose, CA 95138, USA.  
 Main: +1 408-414-9200  
 Customer Service  
 Phone: +1-408-414-9665  
 Fax: +1-408-414-9765  
 Email: [usasales@powerint.com](mailto:usasales@powerint.com)

On the Web  
[www.powerint.com](http://www.powerint.com)

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS. The products and applications illustrated herein (transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at [www.powerint.com](http://www.powerint.com). Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.powerint.com/ip.htm>.

The PI logo, TOPSwitch, TinySwitch, LinkSwitch, DPA-Switch, PeakSwitch, EcoSmart, Clampless, E-Shield, Filterfuse, StackFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2004, Power Integrations, Inc.