



Design Example Report

Title	<i>2.2W Charger using LNK501P</i>
Specification	Input: 198 – 253 VAC Output: 3.6V / 0.6 A
Application	Cell Phone Charger
Author	Power Integrations Applications Department
Document Number	DER-15
Date	February 4, 2004
Revision	1.0

Summary and Features

This report details the design of an isolated Flyback converter for a cell phone charger.

- Uses LinkSwitch LNK501
- European input voltage
- Typical Efficiency > 65 %
- Meets EN550022 Class B EMI tests with No Y1 capacitor
- Very low earth leakage current
- Uses only 20 components

The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com

Table Of Contents

1	Introduction.....	4
2	Power Supply Specification	4
3	Schematic.....	5
4	PCB Layout	5
5	Bill Of Materials	6
6	Transformer.....	7
6.1	Transformer Winding.....	7
6.2	Electrical Specifications.....	7
6.3	Transformer Construction.....	8
6.4	Winding Instructions.....	8
6.5	Materials.....	9
6.6	Design Notes:.....	9
7	Performance Data	10
7.1	Efficiency.....	10
7.2	Regulation	11
7.3	No Load Input Power.....	12
7.4	Output Ripple Measurements.....	13
7.4.1	Ripple Measurement Technique	13
7.4.2	Output Voltage Ripple	14
8	EMI Tests	15
9	Revision History	17



List Of Figures

Figure 1 – Flyback Converter – 2.2W 3.6V 0.6A.....	5
Figure 2 – PCB Layout	5
Figure 3 – Transformer Winding.....	7
Figure 4 – Transformer construction	8
Figure 5 – Efficiency Vs Output Current.....	10
Figure 6 – Efficiency Vs Input Voltage.....	10
Figure 7 – Load Regulation	11
Figure 8 – Line Regulation	11
Figure 9 – No Load Input Power.....	12
Figure 10 – Oscilloscope Probe Prepared for Ripple Measurement.....	13
Figure 11 – Oscilloscope Probe with Probe Master 5125BA BNC Adapter	13
Figure 12 – Output Voltage Ripple at $V_{in} = 220 \text{ Vac}$, $V_o = 3.6 \text{ V}$, $I_o = 600 \text{ mA}$	14
Figure 13 – EN55022 Class B, Line, artificial hand connected to output return	15
Figure 14 – EN55022 Class B, Neutral, artificial hand connected to output return.....	15
Figure 15 – EN55022 Class B, Line, with out artificial hand connected to output return.....	16
Figure 16 – EN55022 Class B, Neutral, with out artificial hand connected to output return	16

List Of Tables

Table 1 – Power Supply Specification	4
Table 2 – Bill of Materials	6
Table 3 – Transformer BOM	9

Important Notes:

Although this board is designed to satisfy safety isolation requirements, the engineering prototype has not been agency approved. Therefore, all testing should be performed using an isolation transformer to provide the AC input to the prototype board.

Design Reports contain a power supply design specification, schematic, bill of materials, and transformer documentation. Performance data and typical operation characteristics are included. Typically only a single prototype has been built.



1 Introduction

This document is an engineering report giving performance characteristics of an isolated Flyback converter with European input voltage and 3.6V 0.6A output. This design uses LinkSwitch – an integrated IC comprising a high voltage MOSFET, PWM controller. The controller provides an I^2t type characteristic to provide a constant current output current without secondary side current sensing.

This document contains the power supply specification, schematic, and bill of materials, transformer documentation, printed circuit layout, and performance data.

2 Power Supply Specification

Description	Symbol	Min	Typ	Max	Units	Comment
Input Voltage	V_{IN}	198	220	253	Vac	
Output Output Voltage 1	V_{OUT1}	2.88 1.7	3.6	4.14	V	at 220Vac
Open circuit voltage	V_{OCV}	5.62		5.1 6.48	V	at 198 Vac at 253 Vac at 220Vac
Output Ripple Voltage 1	$V_{RIPPLE1}$			1.2	V	20 MHz Bandwidth
Output Current 1	I_{OUT1}	498	600	684	mA	
Total Output Power Continuous Output Power	P_{OUT}		2.16		W	
Conducted EMI Margin						EN550022 B, FCC B
Efficiency	η		65		%	At full load
Ambient Temperature	T_{AMB}	0		40	°C	Free convection, Sea level

Table 1 – Power Supply Specification



3 Schematic

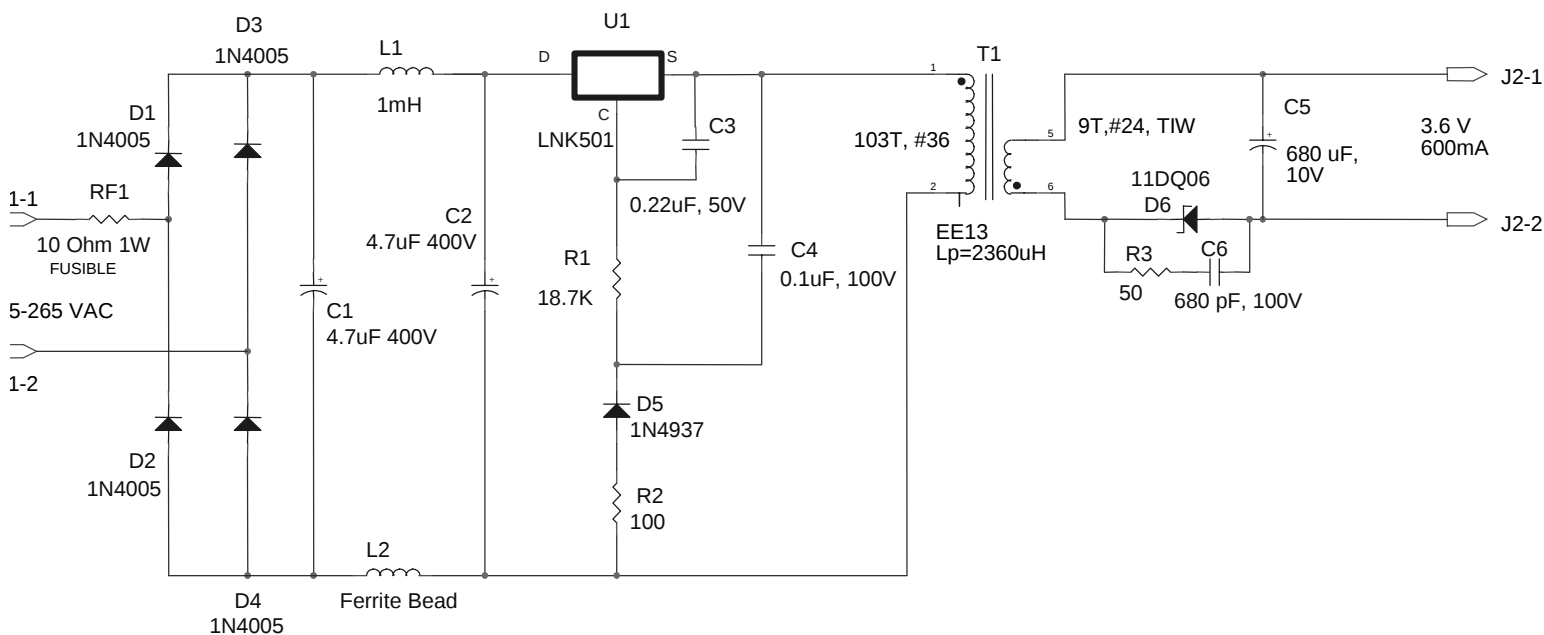


Figure 1 – Flyback Converter – 2.2W 3.6V 0.6A.

4 PCB Layout

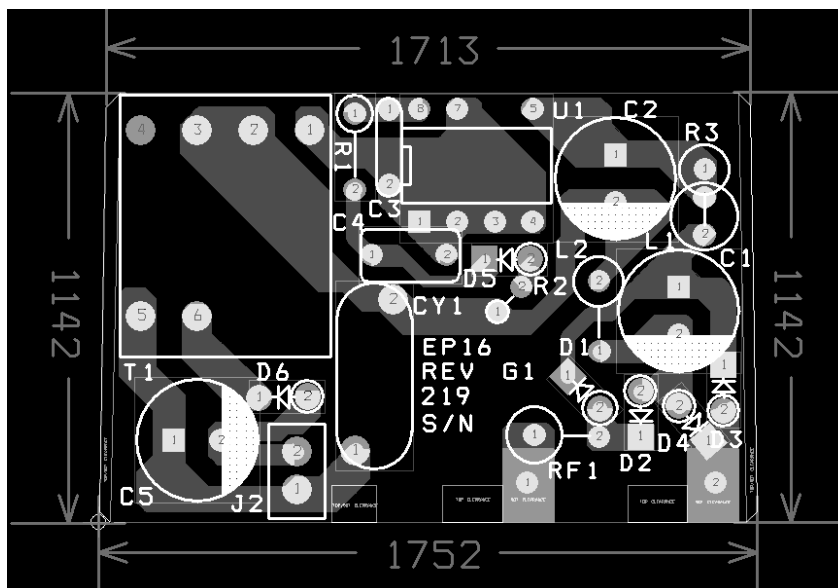


Figure 2 – PCB Layout



5 Bill Of Materials

Item	Quantity	Reference	Part Description
1	2	C1, C2	4.7uF 400V, Electrolytic D=8.5mm, L=12mm
2	1	C3	0.22uF, 50V, Ceramic
3	1	C4	0.1uF, 100V, Metal Film
4	1	C5	680uF, 10V, AL
5	1	C6	680 pF, 100V, ceramic
6	4	D1, D2, D3, D4	1N4005, 1A, 600V
7	1	D5	1N4937, 1A, 600V, Fast Rectifier.
8	1	D6	11DQ06, 1A, 60V, Schottky
9	1	L1	1mH, Inductor Tokin SBCEP-47HY102B
10	1	L2	Ferrite Bead
11	1	RF1	10 Ohm 1W, Fusible
12	1	R1	18.7K 1%, 1/8W
13	1	R2	100, 5%, 1/8W
14	1	R3	50 Ohm, 5%, 1/8W
15	1	T1	Custom EE13
16	1	U1	LNK501

Table 2 – Bill of Materials



6 Transformer

6.1 Transformer Winding

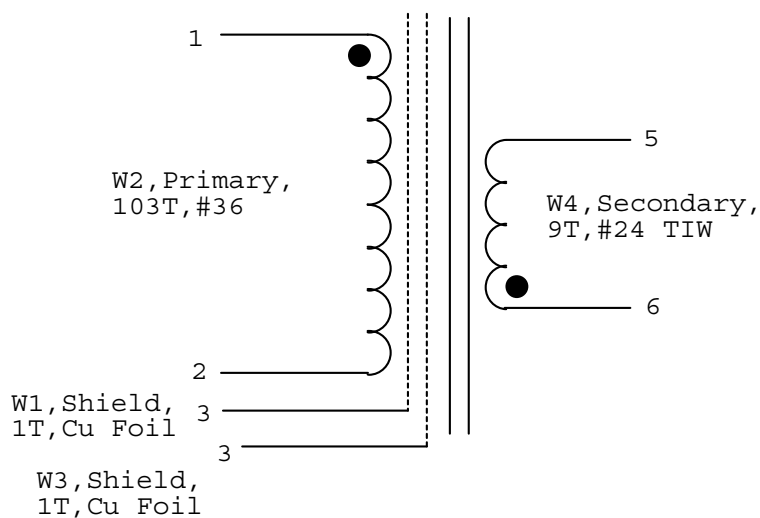


Figure 3 – Transformer Winding

6.2 Electrical Specifications

Electrical Strength	60Hz 1minute, from Pins 1-3 to Pins 5-6	3 kV for 1 minute
Primary Inductance (Pin 1 to Pin 2)	All windings open	2200 μ H – 2530 μ H
Resonant Frequency	All windings open	300 kHz min.
Primary Leakage Inductance	L ₁₃ with pins 5-6 shorted	100 μ H max.

6.3 Transformer Construction

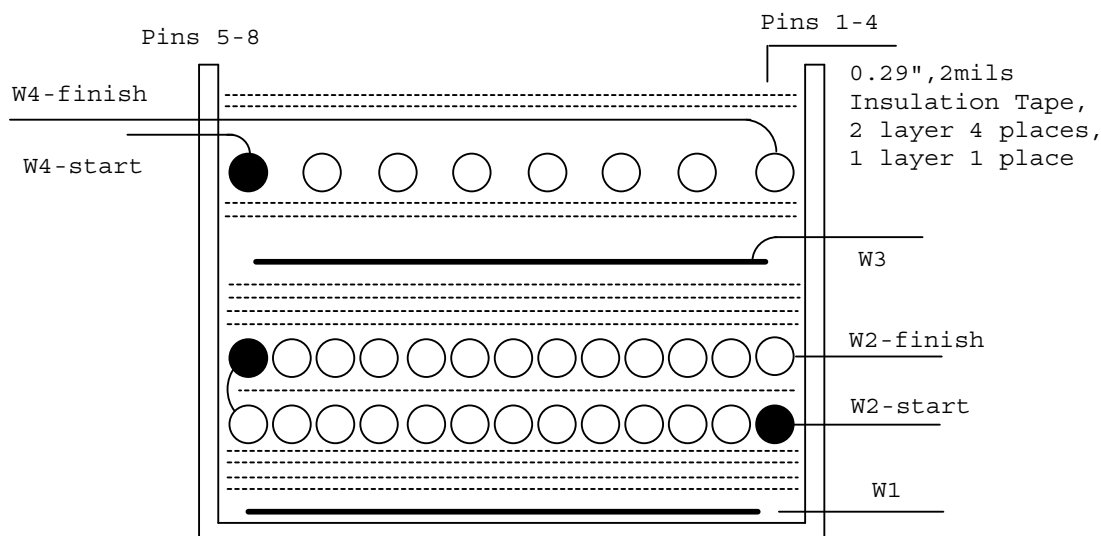


Figure 4 – Transformer construction

6.4 Winding Instructions

Place the bobbin on the winding machine with pins 1-4 on the right side and pins 5-8 on the left side.

W1 (Shield)	Wind 1 turn with 0.25" x 2 mils copper foil, <i>with start and finish ends insulated from each other with tape</i> . Solder a piece of #34 wire to the copper foil and terminate it at pin 3 (primary return). Make sure start and finish ends do not short.
Basic Insulation	4 layers of tape for insulation.
W2 (Primary Winding)	Wind 103 turns in 2-3 layers with # 36 AWG magnet wire – first layer 50T from right to left starting from pin 1 – one layer of insulation tape – second layer 50T from left to right – 3T in the third layer (do not spread), and finish at pin 2.
Basic Insulation	4 layers of tape for insulation.
W3 (Shield)	Wind 1 turn with 0.25" x 2 mils copper foil, <i>with start and finish ends insulated from each other with tape</i> . Solder a piece of #34 wire to the copper foil and terminate it at pin 3 (primary return). Make sure start and finish ends do not short.
Basic Insulation	2 layers of tape for insulation.
W4 (Secondary Winding)	Wind 9 turns with #24 triple insulated wire from left to right starting from 6 and finishing at 5.
Outer Insulation	2 layers of tape for insulation.
Core Assembly	Assemble and secure core halves.
Final Assembly	Impregnate transformer uniformly with varnish.

6.5 Materials

Item	Description
[1]	Core: EE13, PC40EE13, TDK Gapped for $A_L = 225 \text{ nH/T}^2$
[2]	Bobbin: Horizontal 8 pins
[3]	Magnet Wire: #36 AWG
[4]	Triple Insulated wire: # 24 AWG
[5]	Copper foil: 0.25" x 2 mils
[6]	Tape: 3M 1298 Polyester Film (white) 0.29" x 2 mils
[7]	Varnish

Table 3 – Transformer BOM

6.6 Design Notes:

Power Integrations Device	LNK501
Frequency of Operation	42 KHz
Mode	Discontinuous
Peak Current	0.25 A
Reflected Voltage (Secondary to Primary)	49 V
Maximum AC Input Voltage	253 V
Minimum AC Input Voltage	198 V



7 Performance Data

All measurements are performed at room temperature unless otherwise specified. The output voltages are measured at the end of the output cable.

7.1 Efficiency

The measurements are made for various load and line conditions. The efficiencies are calculated and shown in Figure 5 and Figure 6.

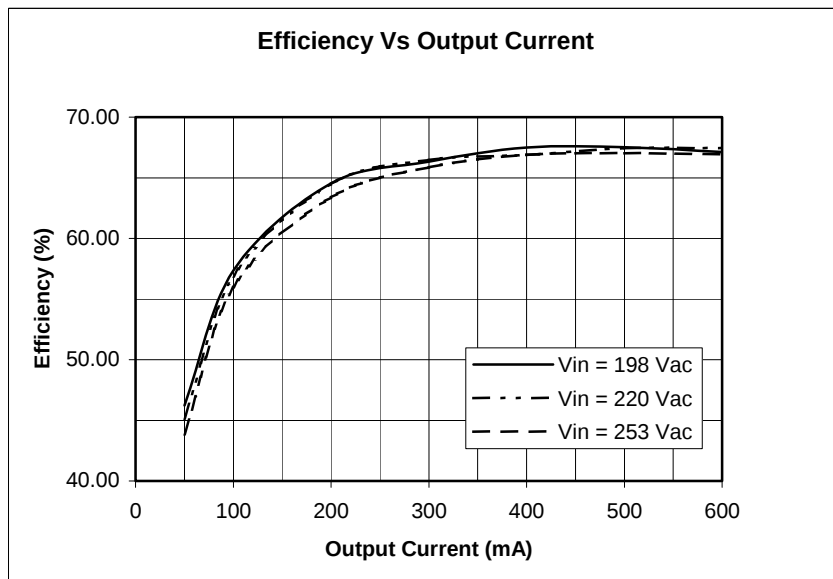


Figure 5 – Efficiency Vs Output Current

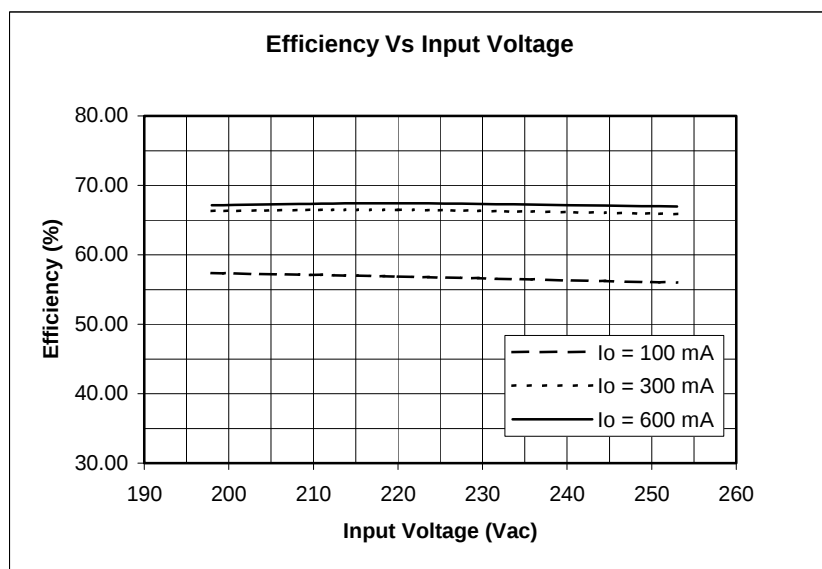


Figure 6 – Efficiency Vs Input Voltage



7.2 Regulation

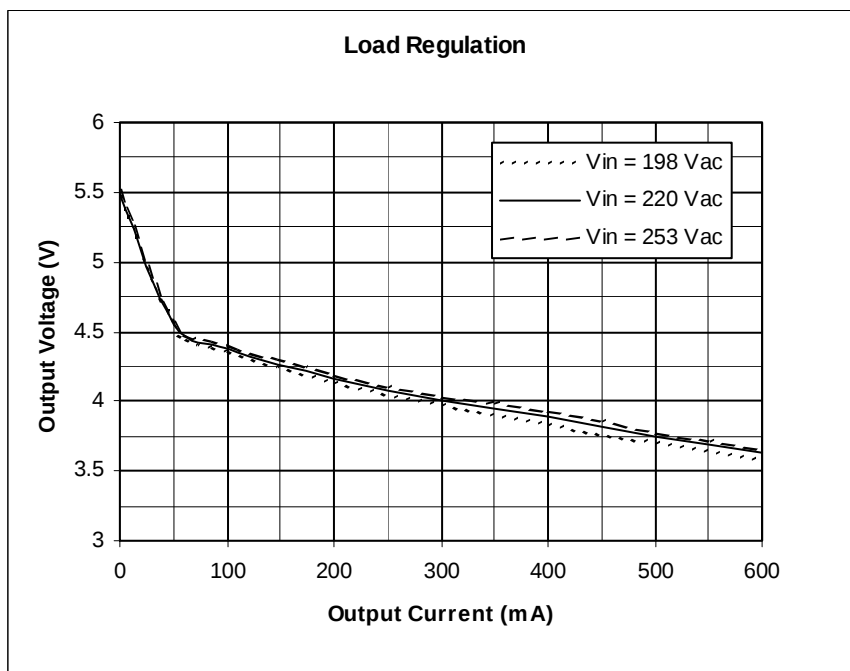


Figure 7 – Load Regulation

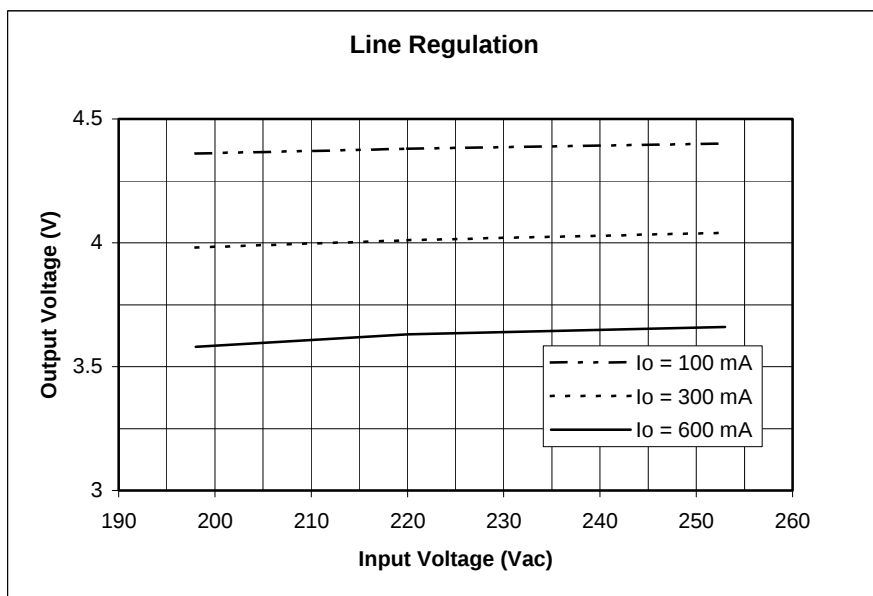


Figure 8 – Line Regulation



7.3 No Load Input Power

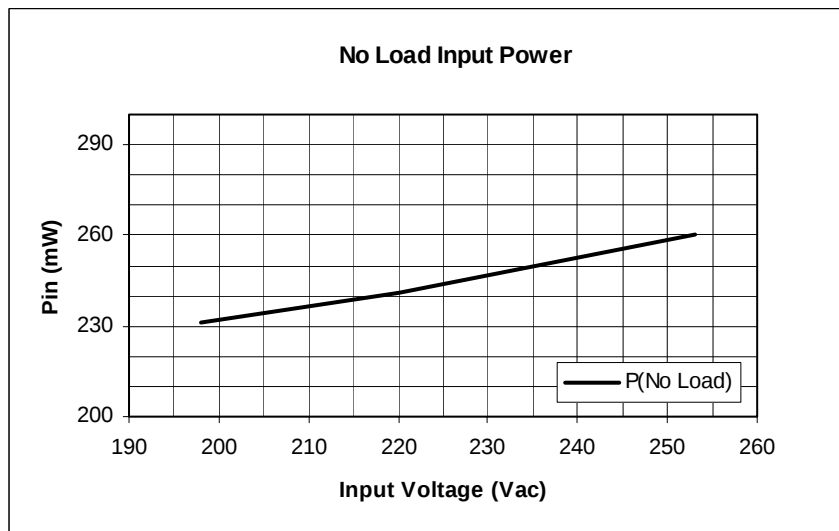


Figure 9 – No Load Input Power

7.4 Output Ripple Measurements

7.4.1 Ripple Measurement Technique

For DC output ripple measurements, a modified oscilloscope test probe must be utilized in order to reduce spurious signals due to pickup. Details of the probe modification are provided in Figure 10 and Figure 11.

The 5125BA probe adapter is affixed with two capacitors tied in parallel across the probe tip. The capacitors include one (1) 0.1 μF /50 V ceramic type and one (1) 1.0 μF /50 V aluminum electrolytic. *The aluminum electrolytic type capacitor is polarized, so proper polarity across DC outputs must be maintained (see below).*

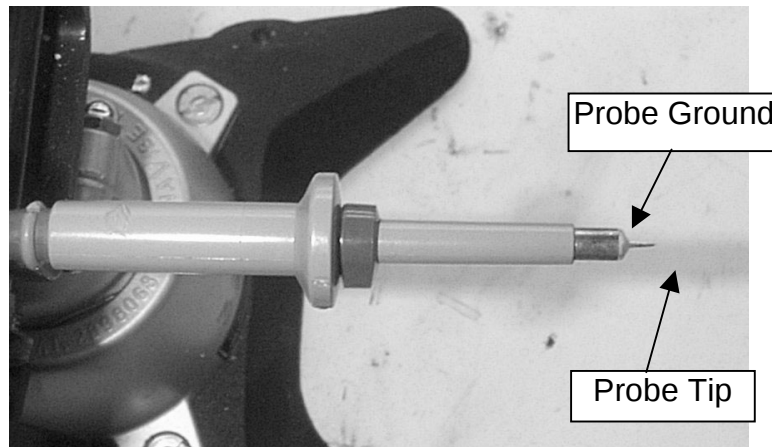


Figure 10 – Oscilloscope Probe Prepared for Ripple Measurement.
(End Cap and Ground Lead Removed)

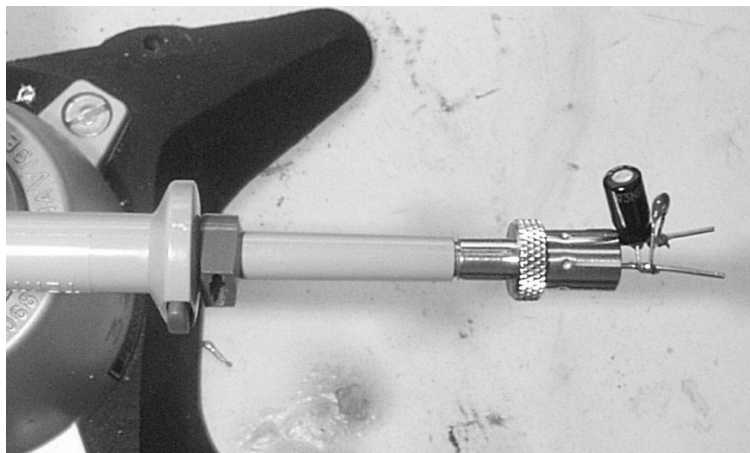


Figure 11 – Oscilloscope Probe with Probe Master 5125BA BNC Adapter

(Modified with wires for probe ground for ripple measurement, and two parallel decoupling capacitors added).

7.4.2 Output Voltage Ripple

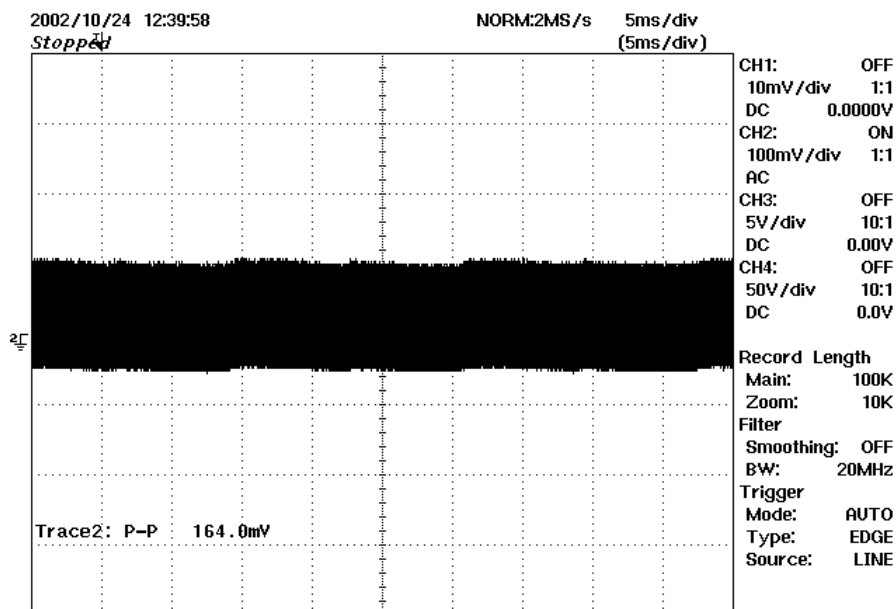


Figure 12 – Output Voltage Ripple at $V_{in} = 220 \text{ Vac}$, $V_o = 3.6 \text{ V}$, $I_o = 600 \text{ mA}$



8 EMI Tests

The EMI tests are done at 220 Vac input and 6 Ω (600 mA) load.

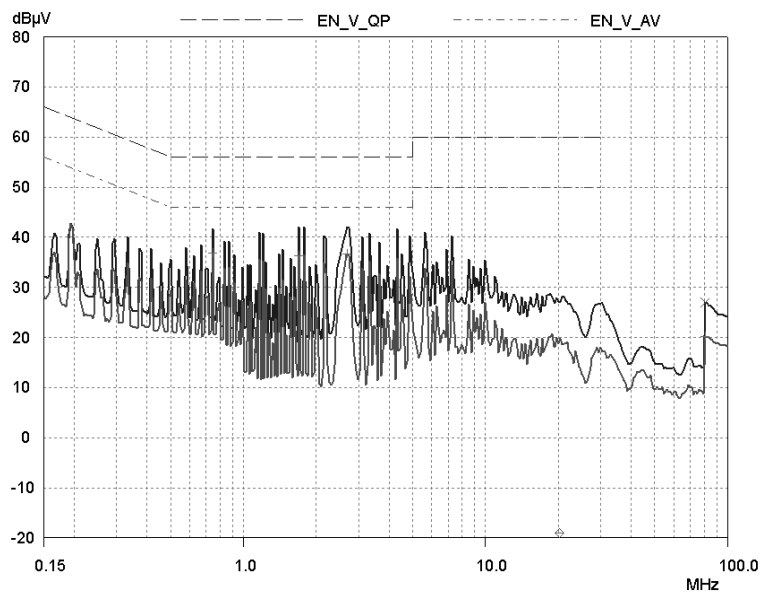


Figure 13 – EN55022 Class B, Line, artificial hand connected to output return

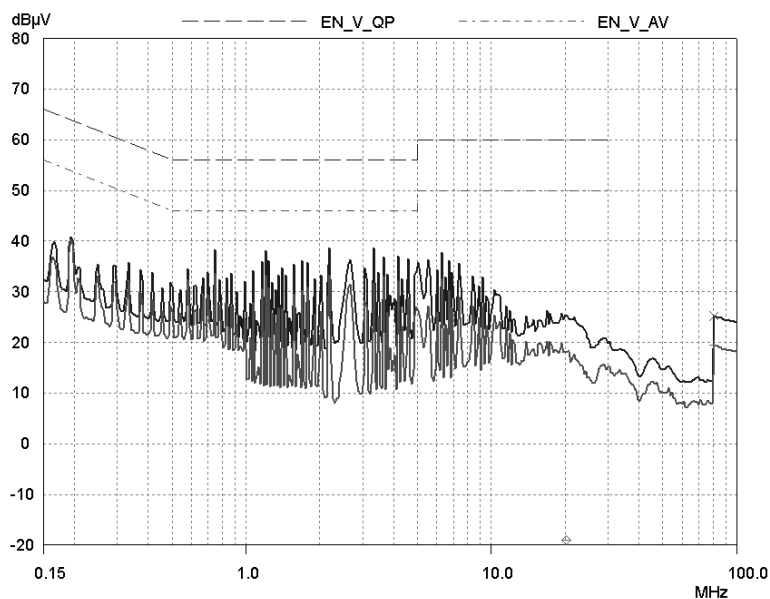


Figure 14 – EN55022 Class B, Neutral, artificial hand connected to output return

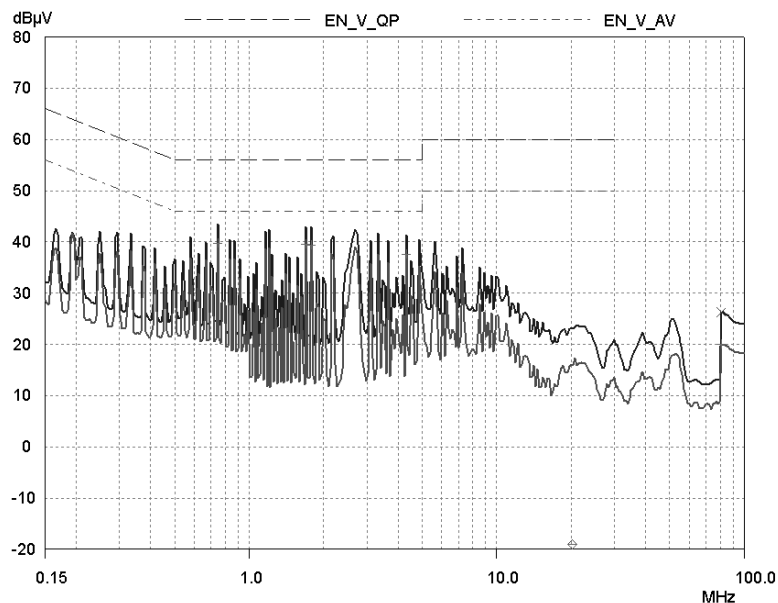


Figure 15 – EN55022 Class B, Line, with out artificial hand connected to output return

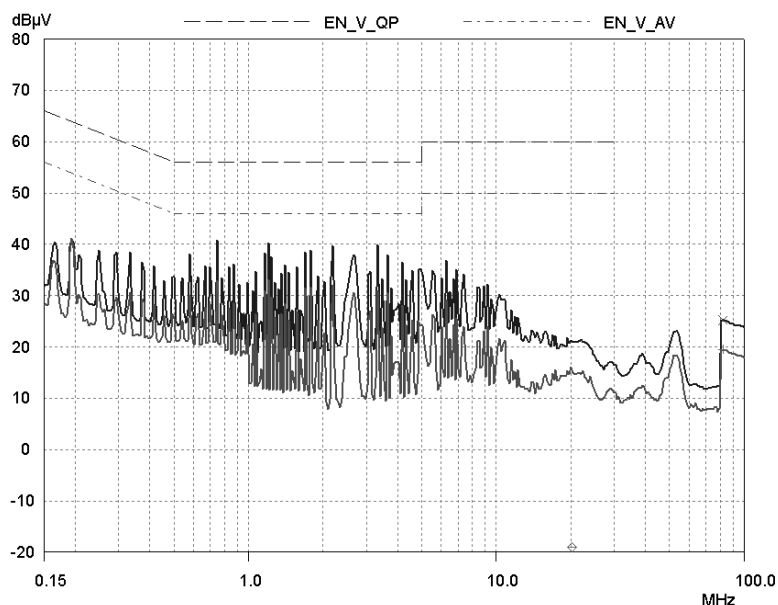


Figure 16 – EN55022 Class B, Neutral, with out artificial hand connected to output return

9 Revision History

Date	Author	Revision	Description & changes	Reviewed
February 4, 2004	MJ	1.0	Initial release	AM/VC



Notes



For the latest updates, visit our Web site: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others.

The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI Logo, **TOPSwitch**, **TinySwitch**, **LinkSwitch**, and **EcoSmart** are registered trademarks of Power Integrations, Inc. **PI Expert** and **DPA-Switch** are trademarks of Power Integrations, Inc.
© Copyright 2003, Power Integrations, Inc.

**WORLD HEADQUARTERS
AMERICAS**

Power Integrations
5245 Hellyer Avenue
San Jose, CA 95138 USA.
Main: +1-408-414-9200
Customer Service:
Phone: +1-408-414-9665
Fax: +1-408-414-9765
E-Mail:
usasales@powerint.com

CHINA

Power Integrations
International Holdings, Inc.
Rm# 1705, Bao Hua Bldg.
1016 Hua Qiang Bei Lu
Shenzhen Guangdong,
518031, China
Phone: +86-755-8367-5143
Fax: +86-755-8377-9610
E-Mail:
chinasales@powerint.com

APPLICATIONS HOTLINE

World Wide +1-408-414-9660

EUROPE & AFRICA

Power Integrations (Europe) Ltd.
Centennial Court
Easthampstead Road
Bracknell
Berkshire RG12 1YQ,
United Kingdom
Phone: +44-1344-462-300
Fax: +44-1344-311-732
E-Mail:
eurosales@powerint.com

KOREA

Power Integrations
International Holdings, Inc.
8th Floor, DongSung Building
17-8, Yoido-dong,
Youngdeungpo-gu,
Seoul, 150-874, Korea
Phone: +82-2-782-2840
Fax: +82-2-782-4427
E-Mail:
koreasales@powerint.com

APPLICATIONS FAX

World Wide +1-408-414-9760

SINGAPORE

Power Integrations, Singapore
51 Goldhill Plaza #16-05
Republic of Singapore 308900
Phone: +65-6358-2160
Fax: +65-6358-2015
E-Mail:
singaporesales@powerint.com

JAPAN

Power Integrations, K.K.
Keihin-Tatemono 1st Bldg.
12-20 Shin-Yokohama
2-Chome,
Kohoku-ku, Yokohama-shi,
Kanagawa 222-0033, Japan
Phone: +81-45-471-1021
Fax: +81-45-471-3717
E-Mail:
japansales@powerint.com

TAIWAN

Power Integrations
International Holdings, Inc.
17F-3, No. 510,
Chung Hsiao E. Rd., Sec. 5,
Taipei, Taiwan 110, R.O.C.
Phone: +886-2-2727-1221
Fax: +886-2-2727-1223
E-Mail:
taiwansales@powerint.com

INDIA (Technical Support)

Innovatech
#1, 8th Main Road
Vasanthnagar
Bangalore, India 560052
Phone: +91-80-226-6023
Fax: +91-80-228-9727
E-Mail:
indiasales@powerint.com

