

DI-187 Design Idea

TOPSwitch[®]-HX

35 W LCD Monitor

| Application | Device | Power Output | Input Voltage | Output Voltage | Topology |
|-------------|----------|--------------|---------------|----------------|----------|
| LCD Monitor | TOP257EN | 35 W | 90 – 264 VAC | 13 V | Flyback |

Design Highlights

- Low component count, high efficiency
 - Delivers 35 W in 50 °C ambient temperature environments
- EcoSmart[®] multi-mode technology meets energy efficiency standards
 - 0.55 W output power for <1 W input
 - No-load power consumption: <200 mW at 230 VAC
 - >82% Full-load efficiency
- Uses new low profile eSIP-7C high-power package that reduces device height and PCB area
- 132 kHz switching frequency minimizes size and cost of power magnetics
- Integrated safety and reliability features
 - Accurate, auto-recovering hysteretic thermal shutdown maintains safe PCB temperatures in any condition
 - Auto-restart protects against output short circuits and open feedback loops
 - Output overvoltage protection (OVP), configurable for latching or self-recovery
 - Input undervoltage (UV) protection prevents power-up or power-down output glitches
 - Input overvoltage (OV) protection extends line surge limit
- Compliance to EN55022 and CISPR-22 Class B conducted EMI: >6 dB margin

Operation

The design schematic in Figure 1 shows an LCD monitor power supply utilizing the TOPSwitch-HX TOP257EN (U1) in a flyback configuration. This supply operates over a wide input range (90 to 264 VAC), delivering a 13 V, 35 W supply to the load.

Y-capacitors C1, C2, and C7 together with inductor L1 provide common mode filtering. Differential mode filtering is provided by X-capacitor C3 and by the bulk capacitor C4. The filtered AC goes to a bridge rectifier. Thermistor RT1 limits the inrush current when AC is applied.

IC U1 turns on when the current into the V pin exceeds 25 μ A. Resistor R3 sets this input voltage threshold to 100 V DC.

IC U1 regulates the output by adjusting the duty cycle of the PWM controller which drives the integrated switching MOSFET. The controller within U1 uses a multi-mode control scheme which seamlessly transitions between different switching modes to maximize efficiency at any load.

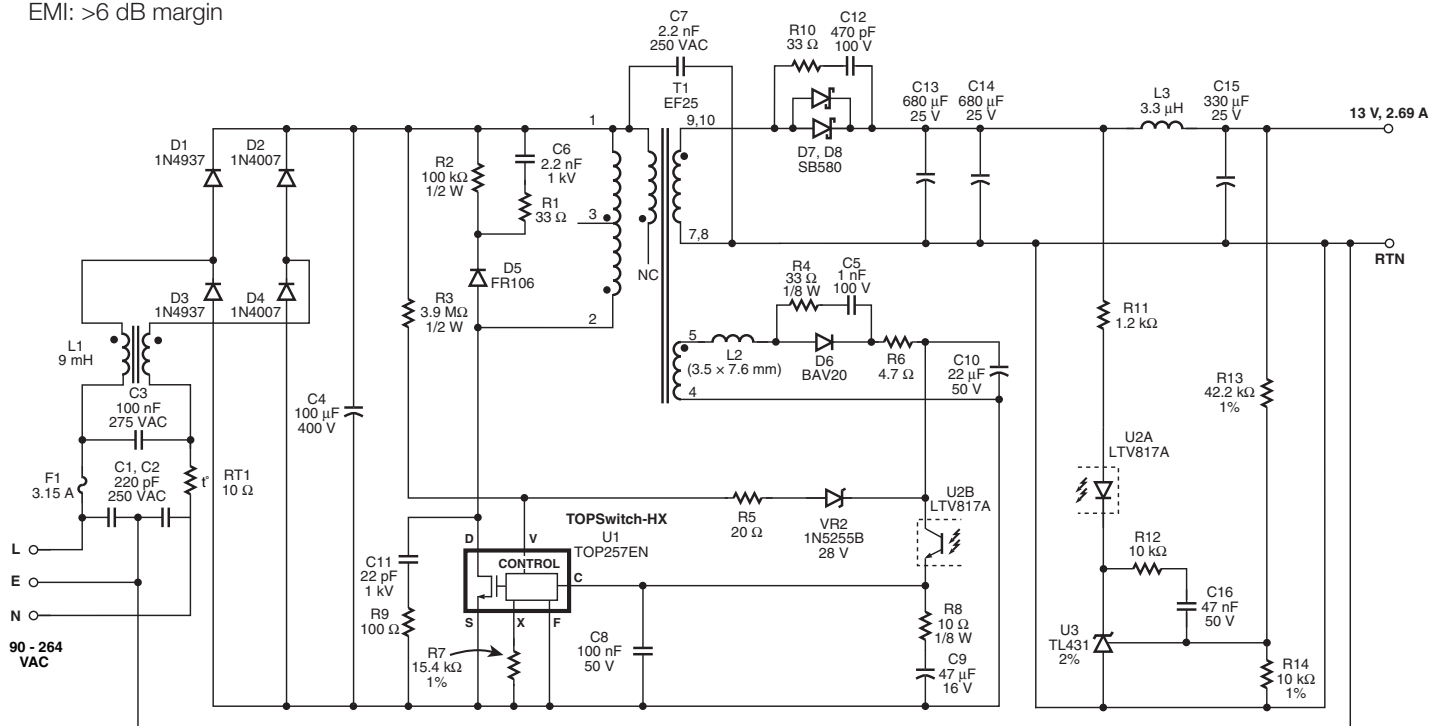


Figure 1. Schematic of a 35 W LCD Monitor Using TOP257EN.

PI-5156-060508

A clamp network formed by D5, C6, R1, and R2 limits U1's drain voltage at turn-off. Fast-recovery diode D5 recovers some of the clamp energy; R1 limits reverse diode currents and dampens high-frequency ringing.

The output of the bias winding is rectified by D6 and filtered by C10. Zener diode VR2 and resistor R5 form a latching output overvoltage protection (OVP) circuit. Increased voltage at the output causes increased voltage across C10. In an overvoltage condition Zener VR2 breaks down and current flows into the V pin of IC U1, initiating a latching shutdown. The shutdown can be either latching or auto-recovering depending on the value of R5.

Diodes D7 and D8 rectify the secondary side output. Low-ESR capacitors (C13, C14) filter the output from D7 and D8. A second-order filter made up of L3 and C15 provides additional filtering on the output that switching noise across C13 and C14.

Resistors R13 and R14 act as a potential divider to sense the output voltage. U3 drives optocoupler U2 through resistor R11 to provide feedback information to U1's C pin.

Key Design Points

- Fast-recovery diodes D1 and D3 reduce radiated EMI (by eliminating voltage spikes inherent to regular diode high-frequency turn-off snap, and by not conducting AC line-induced noise). Their placement ensures one of the two conducts in each half cycle.
- Y-capacitor C7 placed across the transformer (T1) isolation barrier reduces conducted EMI. The switching frequency is modulated (jittered) to reduce EMI.

 


Figure 2. No-load Input Power vs Line Voltage.

- OVP may be configured for latching (as in this design) or for self recovery (non-latching). For non-latching recovery increase R5 to 5.1 k Ω .
- Resistor R4 and C5 form a snubber network across diode D6. With ferrite bead L2 they reduce high-frequency conducted and radiated EMI.

 


Figure 3. Conducted EMI with EN55022 B Limits. Input: 230 VAC, Maximum Steady-state Load.

Transformer Parameters

| | |
|-----------------------------------|--|
| Core Material | EF25, gapped for ALG of 220 nH/t ² |
| Bobbin | EF25 10 pins, Horizontal |
| Winding Details | First half primary: 29T, #26 AWG Bias/feedback: 8T \times 4, #30 AWG Secondary: 7T \times 2, #23, TIW Shield: 9T \times 4, #39 AWG Second half primary: 27T, #26 AWG |
| Winding Order | First half primary (2-3), Bias/feedback (5-4), Secondary (9,10-7,8), Shield (NC-1), Second half primary (3-1) |
| Primary Inductance | 690 μ H, \pm 5% |
| Primary Resonant Frequency | 1.8 MHz (minimum) |
| Leakage Inductance | 13 μ H (maximum) |

Table 1. Transformer Parameters. (AWG = American Wire Gauge, TIW = Triple Insulated Wire, NC = No Connection)

Power Integrations
5245 Hellyer Avenue
San Jose, CA 95138, USA.
Main: +1 408-414-9200
Customer Service
Phone: +1-408-414-9665
Fax: +1-408-414-9765
Email: usasales@powerint.com

On the Web
www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS. The products and applications illustrated herein (transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com. Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.powerint.com/ip.htm>.

The PI logo, TOPSwitch, TinySwitch, LinkSwitch, DPA-Switch, PeakSwitch, EcoSmart, Clampless, E-Shield, Filterfuse, StackFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2008, Power Integrations, Inc.