

FilterFuse™ Low Cost Input Filter/Fuse Configuration

- D1/D2, L1, C1 and the input AC line capacitance form the input pi filter
 - L1 can also act as a fuse element
- Saves >\$0.06 over traditional pi filter input stage which requires two electrolytic bulk capacitors and separate fuse/fusible resistor

