

# Application Note AN-69

## LinkSwitch-4 Family

### Design Guide and Considerations

#### Introduction

The LinkSwitch™-4 family of ICs dramatically simplifies low power CV/CC charger/adaptor design by eliminating an optocoupler and secondary control circuitry. The LinkSwitch-4 family adaptive BJT drive technology uses combined base and emitter switching to boost switching performance and deliver higher efficiency, wider Reverse Bias Safe Operating Area (RBSOA) margin and the flexibility to accommodate a wide range of low cost BJT. The device incorporates a multimode PWM / PFM controller with quasi-resonant switching to maximize the efficiency, meets <30 mW no-load and at same time maintains fast transient response greater than 4.3 V with a load change from 0% to 100%.

#### Advanced Performance Features

- Dynamic base drive technology provides flexibility in choice of BJT transistor by dynamically optimizing BJT switching characteristics
- Extends RBSOA of BJT
- Dramatically reduces sensitivity to BJT gain
- Compensates for transformer inductance tolerances
- Compensates for input line voltage variations
- Compensates for cable voltage drop
- Compensates for external component temperature variations
- Very accurate IC parameter tolerances using proprietary trimming technology
- Frequency up to 65 kHz to reduce transformer size
- The minimum peak current is fixed to improve transient load response

#### Advanced Protection/Safety Features

- Single fault output overvoltage and short-circuit
- Over-temperature protection

#### EcoSmart™ – Energy Efficient

- Meets DoE 6 and CoC V5 2016 via an optimized quasi-resonant switching PWM / PFM control
- No-load consumption of <30 mW at 230 VAC input

#### Green Package

- Halogen free and RoHS compliant package

#### Applications

- Chargers for cell/cordless phones, PDAs, MP3/portable audio devices, adapters, etc.

#### LinkSwitch-4 Family

There are four main family groups covering a power range of nominally 2 W to 18 W and they come in either a SOT23-6 or SO-8 package. Groups are further subdivided by cable drop compensation levels of 0%, 3% and 6%.

LNK43xxx and LNK4x15D devices have an enhanced base drive optimization for reduced BJT losses. For example, the LNK4322S can output 5 W using a TO92 13003 BJT instead of a TO251 13005 and remain thermally safe. The LNK43x3 devices also include a debounce delay after a low output voltage is detected to prevent false UVP foldback being triggered in noisy environments.

#### Output Power Table

Product <sup>3,4</sup>	85 - 265 VAC	
	Features <sup>5</sup>	Adapter <sup>1</sup> Open Frame <sup>2</sup>
<b>LNK43x2S</b>	13003 Drive	5 W
<b>LNK40x2S</b>	STD	6.5 W
<b>LNK40x3S</b>	STD	8 W
<b>LNK4323S</b>	STD	8 W
<b>LNK40x3D</b>	STD	10 W
<b>LNK4323D</b>	STD	10 W
<b>LNK40x4D</b>	STD	15 W
<b>LNK4114D</b>	Easy Start	15 W
<b>LNK4214D</b>	Easy Start + Constant Power	15 W
<b>LNK4115D</b>	Easy Start	18 W
<b>LNK4215D</b>	Easy Start + Constant Power	18 W

Table 1. LinkSwitch-4 Selection Table Based on Output Power.

 


Figure 1. LinkSwitch-4 Packages.

Note that the LNK4xx3D and LNK4xx4D SO-8 packages have the SUPPLEMENTARY BASE DRIVE (SBD) pin and BASE DRIVE (BD) pins swapped. This is to avoid problems with charger/adaptor reliability. The 10 W rated LNK40X3D would otherwise work in a 15 W LNK40X4D design and may pass production final test, but it would be over-stressed and probably result in field failures.

**Scope**

This application note is intended for engineers designing an isolated AC-DC flyback power supply using the LinkSwitch-4 family of devices. It provides guidelines to enable an engineer to quickly select key components and to complete a suitable transformer design. To simplify the task this application note refers directly to the PIXIs design spreadsheet, part of the PI Expert design software suite.

**Basic Circuit Topology**

The circuit in Figure 2 shows the basic topology of a flyback power supply designed using LinkSwitch-4. Because of the high-level integration of LinkSwitch-4, far fewer design issues are left to be addressed externally, resulting in one common circuit configuration for all applications. For example, different output power levels may require different values for some circuit components, but the circuit topology stays unchanged. The exception to this is the optional SBD resistor used with the SO-8 package parts. This increases the available base drive current for higher power designs without increasing the package power dissipation.

**Schematic Features**

- $R_{IN}$  provides inrush current limiting at turn-on and under transient surge conditions.
- $C_{IN1}$ ,  $C_{IN2}$  and  $L_{FILT}$  provide filtering to reduce switching noise impressed upon the AC supply, the capacitors also provide energy storage to power the converter during the valleys of the rectified AC.
- $R_{HT}$  provides start-up current, which is amplified by the BJT to charge CVCC via the EMITTER DRIVER (ED) and VOLTAGE SUPPLY (VCC) pins.

- $R_{CS}$  converts the positive ramping primary current into a negative ramping voltage, which is monitored by the PRIMARY CURRENT SENSE (CS) pin. It allows cycle-by-cycle peak primary current and hence output power control, primary current limiting and, with the transformer turns ratio, sets the maximum output current limit.
- $R_{CS2}$  reduces ESD susceptibility on all devices. Though highly recommended, it is not strictly necessary on LNK40x2S parts. On the remaining parts, it sets one of four minimum primary current levels to control no-load behavior.
- $R_{SBD}$  is only used on SO-8 packaged parts. It allows for extra base drive in higher power designs without increasing package dissipation significantly.
- T1 is the flyback transformer. It stores energy in the primary winding and transfers it to the secondary and bias windings. There are usually additional screen windings, not shown, to reduce EMI.
- The bias diode and  $C_{VCC}$  provide operational power to the controller IC.
- The bias winding is also used to measure the output voltage level on the secondary winding.
- For FEEDBACK (FB) pin positive voltage excursions,  $R_{FB1}$ ,  $R_{FB2}$  and the turns ratio between the secondary and bias windings set the output voltage.
- For negative voltage excursions, the FEEDBACK pin is a virtual earth amplifier and is held at zero volts by sourcing current into  $R_{FB1}$ . This is translated internally into a voltage that represents the HT voltage across  $C_{IN2}$ . This is used to provide input undervoltage detection, brown-out detection and BJT desaturation detection.
- $R_{OUT}$  is a dummy load for controlling no-load behavior.

In addition to this application note, you may also find the LinkSwitch-4 Design Examples Reports (DER). Further details on downloading PI Expert, Design Example Reports, and updates to this document can be found at [www.power.com](http://www.power.com).

 


Figure 2. Typical LinkSwitch-4 Circuit Topology.

## Quick Start

To start immediately, use the following information to quickly design the transformer and select the components for a first prototype. Only the information described below needs to be entered into the PIXIs spreadsheet gray cells in column [B]. Some gray cells have entries in bold font, these contain drop down selections. If an invalid selection is made, then Info or Warning text will appear in column [C] and [D], a description of the error is displayed in column [H]. Other parameters and component values will be automatically calculated. References to spreadsheet cell locations are provided in square brackets [cell reference].

The default design presented in a blank spreadsheet is for a 5 V, 2 A adapter with 6% cable compensation and standard universal AC input voltage range. All gray cells are blank except for those with bold text drop down selections, which are set to the appropriate selections for the default adapter. The default values are displayed in column [E] and [F]. When an entry is made in a column [B] gray cell, its value is transferred into the corresponding cell in columns [E] and [F] and from there, used in the calculations.

*It is only necessary to enter values into column [B] if they are different to the default values in column [E].*

- If a non-standard AC input voltage range is required, enter the values for  $V_{AC\_MIN}$ ,  $V_{AC\_MAX}$  and  $f_i$  into cells [B3, B4, B5] as required.
- Enter the nominal output voltage (at the end of the cable if applicable),  $V_o$  [B6].
- Enter the output diode forward volt drop if different to the standard Schottky value,  $V_D$  [B8].
- Enter the minimum required output current value,  $I_o$  [B9]. Notice that cell [E10] is updated with a suggested minimum CC value for ICC. See Figure 4.
- Enter the required CC limit, ICC [B10], if it is higher than the suggested minimum I [E10]. See Figure 4.
- Enter an efficiency estimate,  $\eta$  [B12]. Use the target figure from the applicable efficiency standard.
- Use the drop down selection menu in [B19] to select the desired cable compensation. Output voltage at the PCB,  $V_{O\_PCB}$ , is now given in [E7].
- The minimum recommended bulk capacitance value ( $C_{IN1} + C_{IN2}$ ) is given in [E13]. If a larger value, or standard values are to be used, enter their total value into [B13].
- Using the value for 'rated output power' in cell [E11], use table 1 on page 1, to choose the correct LinkSwitch-4 device. Use the drop down selection menu in [B18] to select that device.
- BJT types TS13003 and TS13005 are auto selected based on output power. To use a different BJT, enter PART\_NUMBER, HFE\_STARTUP (low current gain), HFE (high current gain) and VSWMAX ( $V_{CBO}$ ) into [B24, B25, B26, B27].
- Use the drop down selection menu in [B35] to select 'AUTO'. A suitable core, bobbin and parameters will automatically be entered into cells [E35 – E43].
- To optimize for efficiency enter an alternative value for the reflected output voltage, VOR in [B49], the default is 100 V. While trying different values, observe the changes in KCRMV [E65] and aim to get between 0.95 and 0.98. At the same time ensure VCRMV-VMIN [E56-E57] is less than 15 V, but the higher VCRMV the better. The spreadsheet will produce a reasonable solution if VOR is left at the default 100 V.
- Fixing the number of secondary turns in [B50] while sweeping the VOR value [B49] offers further optimization possibilities.
- The default primary inductance tolerance is 10%, an alternative value can be entered in [B88]. Tighter tolerance allows better average efficiency across production.
- The default number of primary winding layers is 3 [E98], if the primary current density [E103] is less than 3.8 Amps / mm<sup>2</sup> it can be reduced to 2 by an entry into [B98]. If greater than 10 Amps / mm<sup>2</sup>, increase to 4 etc. The fewer layers the better for leakage inductance and hence efficiency.
- The default calculated number of turns for the bias winding, NB [E105] is based on providing a no-load bias voltage,  $V_{B\_NOLOAD}$  [E107] that achieves the lowest no-load power. However, start-up may be compromised so enter a value between 8 and 9 into  $V_{B\_NOLOAD}$  [B107]. NB will be recalculated; check the value of  $V_{B\_NOLOAD\_MEASURED}$  [E109] is between 8 and 9 V. If not, adjust the value in [B107] and recheck.
- One secondary layer is optimal for efficiency, but if the output voltage is high resulting in the secondary wire being impractically thin, DIAS [E120], then it can be increased by entering a value in LS [B116]. The spreadsheet calculates for a triple insulated wire size that will fill the bobbin width in an integer number of layers given in [E116].
- For low voltage designs, particularly at higher powers and larger cores, the wire thickness becomes impractically thick to wind. By winding the secondary with a number of parallel conductors, the wire thickness is reduced to a practical value, also leakage inductance is decreased which improves efficiency. To use more than one conductor, enter a value into Filars [B117] and recheck the new calculated wire size, DIAS [E120].
- Enter a BJT voltage derating factor into SWITCH\_DERATING [B126] if other than 0.10 (10%) is required.
- Use the drop down selection menu in VCS\_MIN [B135] to set the minimum value of peak primary current at no-load. It is represented by the peak mV across  $R_{CS}$ . For the LNK40X2S devices, only 88 mV should be selected and a 1 k $\Omega$  value be used for  $R_{CS2}$  for filtering. For other devices select the lowest value (56 mV) for the first iteration.
- If the application requires no-load to partial or full load transient capability, where the output voltage must not fall below a minimum value as in USB charger applications, check the value of CBIAS [E138] if it is more than 2  $\mu$ F, enter the value '2' into [B138]. Check DELTA\_BIAS [E139] is less than 1.6 V.
- Output capacitor calculation for starting up into a resistive load: Use the drop down selection menu in LOAD\_TYPE [B141] to select 'Resistive Load'. The spreadsheet calculates the maximum value of output capacitance the circuit will start up into i.e. before CBIAS runs out of charge.
- For a CC load at start-up, use [B141] to select 'CCLoad'. The default start-up CC load current is 75% of  $I_o$ , the rated output current (not the CC limited value) if another value is specified, enter it into ICC\_STARTUP [B142].
- If the suggested output capacitance value needs to be rounded up to a preferred value, enter this into COUT\_FINAL [B145].

If no-load to partial or full load transient step is required as in USB chargers:

- Enter the load step value into I\_LOADSTEP [B148] if it is different to the rated output current.
- Enter the minimum load voltage allowed during no-load to partial or full load transient testing into V\_UNDERSHOOT [B149].
- Check that FSW\_NOLOAD value in [E154] is greater than FSW\_UNDERSHOOT in [E150]. If not, select a lower value for VCS\_MIN [B135], if already at the lowest setting or a LNK40x2S device is being used, enter a lower value for R\_PRELOAD [B152] until the condition is met.
- Check that the no-load power specification is met, P\_NOLOAD\_TOTAL [E174], if not select a higher value of VCS\_MIN [B135] (not LNK40X2S) and recheck that the FSW\_NOLOAD > FSW\_UNDERSHOOT and no-load power requirements are met. If using a LNK40X2S, R\_PRELOAD [B152] can be increased, but no more than 2x.

If no transient step requirement:

- Select a value of VCS\_MIN [B135] and R\_PRELOAD [B153] that gives a FSW\_NOLOAD of between 1 kHz and 2 kHz and still meets the no-load specification.
- Enter the maximum allowed start-up time into STARTUP\_TIME [B156] if it is not to be 1 second. Or enter a preferred value into R\_STARTUP [B157], a new value of the resultant startup time is given in STARTUP\_TIME\_FINAL [E158].

#### Supplementary Base Drive


Resistor  $R_{SBD}$  is used on SO-8 packaged devices to provide extra base drive in higher power applications (7.5 W to 18 W). It should have a value of between 390  $\Omega$  and 220  $\Omega$  for standard designs, or 120  $\Omega$  for applications using the EasyStart feature. Refer to the 'Design Testing' section to check that correct value has been selected.

Component values for the design are found in:

$C_{IN1} + C_{IN2}$ , CIN [E13]  
 Selected device – [E20]  
 Q1 BJT – [E24]  
 T1 Core - [E35]  
 T1 Bobbin – [C37]  
 T1 Primary turns – [E51]  
 T1 Primary layers – [E98]  
 T1 Primary wire diameter – [E101, E102]  
 T1 secondary turns – [E50]  
 T1 Secondary layers – [E116]  
 T1 Secondary flars – [E117]  
 T1 Secondary wire diameter – [E120, E121]  
 T1 Bias turns – [E106]  
 T1 Core gap – [E93]  
 $C_{VCC}$ , Bias capacitor value – [E138]  
 Total output capacitance  $C_{OUT}$  [E145]  
 Output capacitance ripple – [E81]  
 $R_{OUT}$  Dummy load – [E152]  
 $R_{HT}$  Start-up resistor – [E157]  
 $R_{FB1}$  Upper feedback resistor – [E161]  
 $R_{FB2}$  Lower feedback resistor – [E162]  
 $R_{CS}$  Current sense resistor – [E74]  
 $R_{CS2}$   $V_{CSMIN}$  setting resistor – [E136]  
 Bias diode  $V_{RRM}$  – [E129] usually 1N4148  
 $D_{OUT}$   $V_{RRM}$  – [E128]  
 $D_{OUT}$  Peak current – [E79]  
 $D_{OUT}$  RMS current – [E780]

Explore the spreadsheet for more informative data.

Step-by-Step Design Procedure

 

PI-7977-012417

Figure 3. Design Flow Chart.

**General Guidance for Using the PIXIs Design Spreadsheet**

Only the information described below needs to be entered into the PIXIs spreadsheet gray cells in column [B]. Some gray cells already have entries in bold font, these contain drop down selections. If an invalid selection is made, then Info or Warning text will appear in column [C] and [D], a description of the error is displayed in column [H]. Other parameters and component values will be automatically calculated. References to spreadsheet cell locations are provided in square brackets [cell reference].

The default design presented in a blank spreadsheet is for a 5 V, 2 A adapter with 6% cable compensation and standard universal AC input voltage range. All gray cells are blank except for those with bold text drop down selections, which are set to the appropriate selections for the default adapter. The default values are displayed in column [E] and [F]. When an entry is made in a column [B] gray cell, its value is transferred into the corresponding cell in columns [E] and [F] and from there, used in the calculations.

Do not read off calculated component values etc, until all the data has been entered.

It is only necessary to enter values into column [B] if they are different to the default values in column [E].

**Step 1 – Enter Application Variables  $V_{AC_{MIN}}$ ,  $V_{AC_{MAX}}$ ,  $f_L$ ,  $V_o$ ,  $V_D$ ,  $I_o$ ,  $I_{CC}$ ,  $\eta$**

**AC Input Voltage Range,  $V_{AC_{MIN}}$ ,  $V_{AC_{MAX}}$**

Determine the input voltage from Table 2 for common choices, or enter the application specification values into [B3, B4].

Nominal Input Voltage (VAC)	$V_{AC_{MIN}}$	$V_{AC_{MAX}}$
100/115	85	132
230	195	265
Universal	85	265

Table 2. Standard Worldwide Input Line Voltage Ranges.

Note: For designs that have a DC rather than an AC input, enter the values for minimum and maximum DC input voltages,  $V_{MIN}$  [B57] and  $V_{MAX}$  [B58], directly into the grey override cell on the design spreadsheet (see Figure 5).

**Line Frequency,  $f_L$**

Typical line frequencies are 50 Hz for universal or single 100 VAC, 60 Hz for single 115 VAC, and 50 Hz for single 230 VAC inputs. These values represent typical, rather than minimum, frequencies. For most applications this gives adequate overall design margin. To design for the absolute worst case, or based on the product specifications, reduce these numbers by 6% (to 47 Hz or 56 Hz). For half-wave rectification use  $F/2$ . For DC input enter the voltage directly into cells,  $V_{MIN}$  [B57] and  $V_{MAX}$  [B58].

**Nominal Output Voltage,  $V_o$  (V)**

For both CV/CC and CV only designs,  $V$  is the nominal output voltage measured at the end of an attached cable carrying nominal output current. The tolerance for the output voltage is  $\pm 5\%$  (including initial tolerance and over the data sheet junction temperature range).

**Output Diode Forward Voltage Drop,  $V_D$  (V)**

Enter the average forward-voltage drop of the output diode. Use 0.4 V for a Schottky diode or 0.7 V for a PN-junction diode (if specific diode data is not available).  $V_D$  has a default value of 0.4 V.

**Minimum Required Output Current,  $I_o$  (A)**

This is the nameplate current and is the current that must be supplied at the nameplate voltage, before the VI curve follows the decreasing voltage CC characteristic. It is the output current level at which efficiency measurements are taken. See Figure 4.

 


Figure 4. VI Curve With Parameter Positions Identified.

**CC Mode Current Output Level,  $I_{CC}$  (A)**

In CC mode, the output current is regulated to the  $I_{CC}$  value. There is a 7% overall tolerance on the regulated value, so the spreadsheet automatically defaults to setting this level to  $I_o + 8\%$ . It is possible to set  $I_{CC}$  to a higher level by entering a value into [B10], a higher value will help start-up into CC and/or high capacitance loads. It is recommended that  $I_{CC} < I_o + 20\%$  else efficiency will be significantly reduced.

**Power Supply Efficiency,  $\eta$**

Enter the estimated efficiency of the complete power supply, as would be measured at the output cable end (if applicable). In practice, use the applicable energy saving standard value. If the completed power supply fails to meet this value of efficiency, some components may be over stressed, but as the design has failed the efficiency specification it will need modifying anyway, before being accepted for production.

**Total Input Capacitance,  $C_{IN}$**

This is calculated from the maximum power drawn from the bulk capacitors at  $V_{AC_{MIN}}$ , the minimum allowable bulk capacitor voltage ( $V_{MIN}$ ) at which the converter will operate efficiently, nominally 80 V, and the line frequency ( $F_L$ ). The value calculated in [E13] - with [B13] blank, is the minimum required capacitance. A higher value may be entered into [B13] to round up to the nearest standard value, or increase the operating efficiency of the converter stage over the AC input voltage range. The total value of  $C_{IN}$  is then split into two approximately equal values,  $C_{IN1}$  and  $C_{IN2}$ , to provide the input pi filter. It is advisable to make at least  $C_{IN2}$  a low ESR type.

The following equation may be used to calculate the minimum capacitance required:

$$C_{IN1} + C_{IN2} \geq \frac{P_o}{(\eta F_{L(MIN)}) \times (2 \times V_{ACMIN}^2 - V_{MIN}^2)} \times \arccos\left(\frac{-V_{MIN}}{\sqrt{2} \times V_{ACMIN}}\right)$$

Use higher values to allow for capacitor tolerance.

ENTER APPLICATION VARIABLES			Design title
VACMIN		90 Volts	Minimum AC Input Voltage
VACMAX		265 Volts	Maximum AC Input Voltage
fL		50 Hertz	AC Mains Frequency
VO		5.00 Volts	Output Voltage at the end of the cable
VO_PCB		5.30 Volts	Output Voltage at PCB. Changes with cable compensation selection
VD		0.40 Volts	Output Winding Diode Forward Voltage Drop
IO		2.00 Amps	Full load rated current. Used for all waveshape related calculations.
ICC		2.16 Amps	CC setpoint. Must be >= IO+7%. Affects Rcs.
PO		10.60 Watts	Rated output power including cable drop compensation. Calculated from IO
n		0.80 %/100	Efficiency Estimate
CIN		20.0 uFarads	Total input bulk Capacitance

Figure 5. Application Variables Section of the Design Spreadsheet.

## Step 2 – Enter LinkSwitch-4 Selection

### Select the Cable Drop Compensation Option

Select the cable compensation option from the drop down selection menu in [B19] to most closely match the percentage output voltage drop in the output cable. For example, a 5 V, 2 A LNK40x4D design with a cable impedance of 150 mΩ has a cable voltage drop of -0.3 V. With a desired nominal output voltage of 5 V (at the end of the cable), this represents a voltage drop of 6%. In this case, select the +6% compensation, to give the smallest error. 0%, 3% or 6% can be selected.

### Selecting the Correct LinkSwitch-4 Part

Using the value for rated output power' in cell [E11], use Table 1 on page 1, to choose the correct LinkSwitch-4 device. Use the drop down selection menu in [B18] to select that device. The full part number is given in [E20].

The full load switching frequency of standard LinkSwitch-4 devices is 65 kHz.

### Enter BJT selection

BJT types TS13003 (up to 5 W) and TS13005 (up to 18 W) are auto selected based on output power. There are 800 V and 900 V rated TS13003 parts for special circumstances, such as snubberless design or higher AC input voltage e.g. 420 VAC. To use a different BJT, enter PART\_NUMBER, HFE\_STARTUP (low current gain), HFE (high current gain) and VSWMAX ( $V_{CB0}$ ) into [B24, B25, B26, B27].

## Output Power Table

Product <sup>3,4</sup>	85 - 265 VAC	
	Features <sup>5</sup>	Adapter <sup>1</sup> Open Frame <sup>2</sup>
<b>LNK43x2S</b>	13003 Drive	5 W
<b>LNK40x2S</b>	STD	6.5 W
<b>LNK40x3S</b>	STD	8 W
<b>LNK4323S</b>	STD	8 W
<b>LNK40x3D</b>	STD	10 W
<b>LNK4323D</b>	STD	10 W
<b>LNK40x4D</b>	STD	15 W
<b>LNK4114D</b>	Easy Start	15 W
<b>LNK4214D</b>	Easy Start + Constant Power	15 W
<b>LNK4115D</b>	Easy Start	18 W
<b>LNK4215D</b>	Easy Start + Constant Power	18 W

Table 3. Selection Table of LinkSwitch-4 Parts by Power and Maximum BJT Emitter Current (Primary Current).

BJT	Output Power
TS13005	Up to 15 W
TS13003	Up to 5 W

Table 4. Recommended BJTs.

ENTER LINKSWTCH-4 VARIABLES			
LinkSwitch-4	LNK40X4D		Select LNK-4
Cable drop compensation option	6%	6%	Select level of cable drop compensation
DEVICE		LNK4024D	Complete reference of select part number with the selected cable drop compensation option
FSW		65000 Hertz	LinkSwitch-4 typical switching frequency
ILIM_MAX		1.10 A	Maximum emitter pin sink current
<b>Transistor</b>			
PART_NUMBER		TS13005	Example transistor for the current application
HFE_STARTUP		12	Minimum DC current gain at no load and startup. Affects start-up delay
HFE		25	Minimum DC current gain for load transient
VSWMAX		700 Volts	Switch Breakdown voltage
V_CGND_ON		3.0 Volts	BJT + LNK-4 on-state Collector to ground Voltage (3V if no better information available)

Figure 6. LinkSwitch-4 and BJT Selection.

**Step 3 – Core and Bobbin Selection Based on Output Power and Enter  $A_{E_f}$ ,  $L_{E_f}$ ,  $A_{L_f}$ ,  $B_w$ ,  $M$**

These symbols represent core effective cross-sectional area  $A_E$  (cm<sup>2</sup>), core effective path length  $L_E$  (cm), core ungapped effective inductance  $A_L$  (nH/Turn<sup>2</sup>), bobbin width  $B_w$  (mm) and safety margin width  $M$  (mm).

Due to the small transformer size that results at these power levels, triple insulated wire is generally used for the secondary, so Safety Margin Width is not used and left set to the default '0' setting. If the Safety Margin method is preferred and standard wire used, enter the safety margin width. The spreadsheet will double it and subtract it from the bobbin width ( $B_w$ ) and give the effective bobbin width, or winding width ( $B_{we}$ ). Universal input designs typically require a total margin of 6.2 mm, and a value of 3.1 mm entered into [B42]. The spreadsheet uses the value of  $B_{we}$  to calculate the required wire diameter to fill the available bobbin width to minimize leakage inductance.

For designs using triple-insulated wire it may still be necessary to enter a small margin to meet required safety creepage distances. Typically many bobbins exist for each core size, each with different mechanical spacing. Refer to the bobbin data sheet or seek guidance from your safety expert or transformer vendor, to determine the requirement for your design. The margin reduces the available area for windings, so margin construction may not be suitable for transformers with smaller cores. If, after entering the margin, more than three primary layers (L) are required, either select a larger core or switch to a zero-margin design using triple-insulated wire.

If the drop down selection menu in [B35] is used and 'AUTO' selected, the spreadsheet selects the smallest core size, by  $A_{E_f}$  that meets the peak flux density limit. The user can select an alternative core from drop down list of commonly available cores (shown in Table 6). Table 5 provides guidance on the power capability of specific core sizes.

If the user has a preferred core not in the list, then the appropriate parameters can be entered into [B36 – B42].

Core Size	Output Power Capability
EF12.6	3.3 W
EE13	3.3 W
EE16	6.1 W
EF20	10 W

Table 5. Output Power Capability of Commonly used Sizes in LinkSwitch-4 Designs.

Transformer Core Size	
EE10	EF32
EF12.6	EFD15
EE13	EFD25
E24/25	EFD30
EE16	EI16
EE19	EI19
EE22	EI22
EEL16	EI25
EE16W	EI28
EEL19	EI30
EEL22	EI35
EE25	EI40
EEL25	EPC17
EEL28	EPC19
EER28	EPC25
EER28L	EPC30
EER35	ETD29
EER40	ETD34
EES16	ETD39
EF16	EE42/21/15
EF20	EE55/28/21
EF25	EF32
EF30	

Table 6. List of Cores Provided in LinkSwitch-4 PIXIs Spreadsheet.

ENTER TRANSFORMER CORE/CONSTRUCTION VARIABLES			
Core Type	EPC17	EPC17	Core Type
Custom Core (Optional)			If Custom core is used - Enter Part number here
Bobbin		P/N:	BEPC-17-1110CPH
AE		0.23 cm <sup>2</sup>	Core Effective Cross Sectional Area
LE		4.02 cm	Core Effective Path Length
AL		1150 nH/T <sup>2</sup>	Ungapped Core Effective Inductance
BW		9.55 mm	Bobbin Physical Winding Width
M		0 mm	Safety Margin Width (Half the Primary to Secondary Creepage Distance)
BWE		9.6 mm	Effective Bobbin Width

Figure 7. Transformer Core Selection.

#### Step 4 – Select Reflected Voltage and Secondary Turns

These are the main optimization inputs that effect efficiency and the minimum DC bulk capacitor voltage the converter will operate at, under full load. The spreadsheet will produce a reasonably optimized design, but further improvement may be possible. To optimize for efficiency enter an alternative value for the reflected output voltage, VOR in [B49], the default is 100 V. Whilst trying different values, observe the changes in KCRMV [E65] and aim to get between 0.95 and 0.98, though 0.945 to 1.05 is acceptable. At the same time ensure VCRMV-VMIN [E56-E57] is less than 15 V. The higher VCRMV the better for efficiency at the cost of some twice line frequency ripple in the output at ICC and VO (maximum power point). Fixing

the number of secondary turns in [B50] while sweeping the VOR value [B49] offers further optimization possibilities.

The default primary inductance tolerance is 10%, an alternative value can be entered in [B88]. Tighter tolerance allows better average efficiency across production.

F\_RES is the idle ring frequency of the transformer whilst in the application, so includes the effects of BJT collector capacitance and snubber capacitance. Use the default 400 kHz if no other figure is available. Once the application has been tested, the true figure can be entered and further optimization performed as required. Usually a lower F\_RES in the application will have an adverse effect, but it would have to be significantly lower to have a measurable effect, say -25%.

MAIN OPTIMIZATION INPUTS			
<b>Turns and ratio</b>			
VOR		100.00 Volts	Reflected Output Voltage. Use Goal Seek to get VCRMV to desired value.
NS		6	Number of Secondary Turns. Adjusting up or down along with VOR may improve efficiency.
NP		105	Primary Winding Number of Turns

Figure 8. VOR and Secondary Turns Selection - Main Optimization Values.

DC INPUT VOLTAGE PARAMETERS			
VCRMV		94 Volts	Vbulk at CRMV, at max LP tolerance. Higher value typically more efficient.
VMIN		82.6 Volts	Bulk cap "trough" voltage at VACMIN. Leave blank to calculate from capacitance and load.
VMAX		375 Volts	Maximum DC Input Voltage
VBROWN		51 Volts	Bulk voltage it loses regulation

Figure 9. DC Input Parameter Entry and VCRMV Optimization Watch Value.

PRIMARY WAVEFORM PARAMETERS			
F_RES		400 kHz	Anticipated resonant frequency on the primary side ( $180 < F_{trf} < 1200$ )
KCRMV		0.95	Ratio of primary switch off time to secondary conduction plus first valley time
IRMS		0.25 Amps	Primary RMS Current (calculated at load=IO, VMIN)
IP		0.60 Amps	Peak Primary Current (calculated at load=IO, VMIN)
IOCP		0.79 Amps	Pulse by pulse current limit. Appears during large load transients and brownout operation.
IAVG		0.16 Amps	Average Primary Current (calculated at load=IO, VMIN)
IP_CRMV		0.56 Amps	Ipeak when Vin=Vcrm
F_CRMV		65000 Hz	Fsw when Vin=Vcrm
FVMIN		62410 Hz	Fsw at VMIN. If < 65kHz, is in frequency reduction mode
VCS_VMIN		0.273 Volts	Vcs_pk at VMIN and load = IO
RCS		0.453 Ohm	Calculated RCS value. Changes with Icc and VOR

Figure 10. Figure 10: Primary Waveform Parameters and KCRMV Optimization Watch Value.

SECONDARY WAVEFORM PARAMETERS			
ISP		10.53 Amps	Peak Secondary Current @ VMIN
ISRMS		3.67 Amps	Secondary RMS Current @ VMIN
IRIPPLE		3.08 Amps	Output Capacitor RMS Ripple Current @ VMIN

Figure 11. Secondary Waveform Design Parameters.

**Step 5 – Transformer Core Parameters**

The default peak core flux is set to 3900 Gauss. If the users selected core material requires a different value, enter it into [B86].

The default tolerance on the primary inductance is ±10%. A tighter tolerance allows better average efficiency across production, an alternative value may be entered into [B88].

**Step 6 – Transformer Primary Winding Design Parameters**

The default number of primary winding layers is 3, however if [H103] indicates that the current density is low, then 2, or even 1, can be

entered into [B98] and the wire diameter will be reduced accordingly. The lower the number of primary layers, the lower leakage inductance is likely to be. However it may be possible that sandwiching the secondary between 2 primary layers would result in the lowest leakage inductance at the cost of a more complicated transformer construction.

If [H103] indicates that the current density is high, then a higher value must be entered into [B98]. More than 3 primary layers will result in high primary to secondary leakage inductance, resulting in high-voltage stress on the BJT or increased clamp/snubber losses, so it may be necessary to sandwich the secondary between layers of the primary.

TRANSFORMER CORE PARAMETERS			
BP		3900 Gauss	Peak Flux Density @ max IOCP & max LP. 3900 Gauss. Lower BP may reduce efficiency
LP		1099 uHenries	Nominal Primary Inductance
LP Tolerance		10	Tolerance of Primary Inductance. Tighter tolerance allows better average efficiency across production.
ALG		100 nH/T <sup>2</sup>	Gapped Core Effective Inductance
BM		2763 Gauss	Maximum Flux Density at PO, VMIN, LP (BM<3000)
BAC		1381 Gauss	AC Flux Density for Core Loss Curves (0.5 X Peak to Peak)
ur		1614	Relative Permeability of Ungapped Core
LG		0.26 mm	Gap Length (Lg > 0.1 mm)

Figure 12. Transformer Core Operational Parameters.

TRANSFORMER PRIMARY DESIGN PARAMETERS			
L		3.0	Number of Primary Layers
OD		0.25 mm	Maximum Primary Wire Diameter including insulation to fill layers
INS		0.05 mm	Estimated Total Insulation Thickness (= 2 * film thickness)
DIA		0.20 mm	Bare conductor diameter
AWG		33 AWG	Primary Wire Gauge (Rounded to next smaller standard AWG value)
Primary Current Density (J)		5.23 Amps/mm <sup>2</sup>	Primary Winding Current density (3.8 < J < 10)
<b>Bias/Feedback Winding</b>			
NB		9 Turns	Suggested number of turns for the bias / feedback winding
VDB		0.70 Volts	Bias Winding Diode Forward Voltage Drop
VB_NOLOAD		7.40 Volts	Desired Minimum Bias voltage at no load
PB_NOLOAD		4.14 mW	Bias winding power consumption estimate at no load
VB_NOLOAD_MEASURED		7.40 Volts	Measured Bias voltage at no load

Figure 13. Transformer Primary Design Parameters.

## Step 7 – Bias / Feedback Winding Design Parameters

The bias / feedback winding performs two functions, as its name suggests. Firstly, it provides power to the controller after the start-up period and secondly, it provides the feedback signal to monitor output voltage and bulk capacitor voltage.

During the start-up period, the controller is powered by the charge held on the  $V_{CC}$  capacitor  $C_{VCC}$ . Before the voltage on  $C_{VCC}$  falls to  $V_{VCC(SLEEP)} - 4.5 V$ , the output voltage from the bias winding must exceed  $V_{VCC(SLEEP)} + V_{DB}$ . The voltage from the Bias winding during start-up is related to the voltage on the secondary winding, which in turn, is related to the voltage on the output capacitor, which is charging from 0 V to  $V_{OUT}$ . Hence more turns on the bias winding results in easier starting with high output capacitance or constant current loads, but results in a higher no-load power. Conversely, a lower number of turns results in a reduced output capacitance or constant current load start-up capability, but lower no-load power. A good starting point is to aim for a no-load  $V_{CC}$  voltage of between 8 V and 9 V, 7 V is the minimum. The no-load level of  $V_{CC}$  is determined by the turns ratio of the secondary and bias turns, whereas the  $V_{CC}$  level with load applied is increased by energy scavenged from leakage inductance and is not practical to calculate. Check the  $V_{CC}$  level on the completed design, checking that at the maximum AC input voltage and at maximum load or start-up,  $V_{CC}$  does not exceed 16.5 V.

$$N_{BIAS} = \frac{V_{CC(No-Load)} + V_{DBIAS}}{V_{OUT} + V_{DOUT}} \times N_S$$

The bias supply diode should be a silicon junction device, a Schottky has too much reverse leakage and may prevent start-up. The spreadsheet has 0.7 V entered as the default forward volt drop of the bias supply diode, suitable for a silicon junction diode. An alternative value may be entered into [B106] if required.

The spreadsheet defaults to calculating the required number of bias wind turns to give at least 7 V with an integer number of turns. The number of turns calculated is given in [E105] and the resulting  $V_{CC}$  level, at no-load, is given in [E109]. As previously discussed, between 8 V and 9 V is recommended, so enter '8' into [B107]. The spreadsheet will recalculate the number of turns to achieve a level of at least 8 V. The revised number of Bias wind turns are given in [E105] and the actual  $V_{CC}$  level, at no-load, is given in [E109].

For applications that have challenging start-up conditions, CC load and/or high output capacitance, a higher value of target  $V_{CC}$  may be entered into [B107], 9 V for example. Note however, that the Bias winding power, given in [E108], increases with Bias voltage. Check the no-load power estimation in [E174] is within specification. Check the  $V_{CC}$  level on the completed design, confirm that at the maximum AC input voltage and at maximum load or start-up,  $V_{CC}$  does not exceed 16.5 V.

### Bias Supply Diode Selection

In most circumstances a 1N4148 is adequate. In situations where more leakage energy scavenging is required, to assist start-up for example, a higher current ultrafast silicon diode may be used. The maximum reverse voltage across the Bias diode is calculated in [E129], add margin to this value before selecting a suitable part. Suggested parts are given in Table 7.

$$V_{DBIAS(MAX)} = \sqrt{2} \times V_{ACMAX} \frac{N_A}{N_P} + V_{CC(MAX)}$$

Where  $V_{CC(MAX)} = 16.5 V$  worst case.

Type	$T_{RR}$ (ns)	$V_{RRM}$ (V)	$V_{FD}$ (V) @	$I_F$ (A)
1N4148	4	75	1.0	0.15
1N4933	50	50	1.0	1.0
SF11G	35	50	1.0	2.0
UF4001	50	50	1.0	2.0
BYV27-50	25	50	1.0	2.0
UG1A	25	50	1.0	3.0
ES1A	35	50	1.0	3.0
STTH1R02	15	200	1.0	3.0

Table 7. Suggested Bias Supply Diodes.

**Step 8 – Secondary Winding Design Parameters**

Generally only one winding layer is used for the secondary, but for high output voltage designs or very narrow winding window bobbins, more may be needed. However, be aware that more layers mean more leakage inductance and probably a reduction in efficiency.

The spreadsheet defaults to 1 layer and calculates the required wire diameter that will fill the bobbin width in the calculated number of secondary turns.

recalculate the number of layers or filars. It does recalculate the bare conductor diameter in [E120] and is useful for investigating the effect on secondary winding current density.

The default secondary wire insulation thickness is 0.1 mm, as would be found on available triple insulated wire. This is doubled to give the space required for the insulation on the bobbin in [E119]. A custom value (2 x insulation thickness) can be entered into [B119]. [E120] gives the bare conductor diameter, this can be used to select

TRANSFORMER SECONDARY DESIGN PARAMETERS				
LS			1.0	Number of Secondary Layers
FilarS			2	# of paralleled secondary wires
ODS			0.76 mm	Maximum Secondary Wire Diameter including insulation to fill layers
INSS			0.20 mm	Estimated Total Insulation Thickness (= 2 * film thickness)
DIAS			0.56 mm	Bare conductor diameter
AWGS			24 AWG	Secondary Wire Gauge (Rounded to next smaller standard AWG value)
Secondary Current Density (J)			7.56 Amps/mm <sup>2</sup>	Winding Current density (3.8 < J < 10)

Figure 14. Transformer Secondary Design Parameters.

If more layers are required to increase wire diameter, enter the value into [B116].

For low voltage designs with a wide bobbin width, the required wire thickness to fill the bobbin width may result in a wire thickness that is too large to easily wind on the bobbin. To alleviate this problem, the secondary can be wound in a number of filars (strands) in parallel and side by side with each other. The spreadsheet calculates a recommended number of filars displayed in [E117] required to keep wire diameter practical. Approximately 1 mm outside diameter is the spreadsheet target limit, but by entering the number of required filars in [B117] the wire diameter can be reduced or increased as required.

From the effective bobbin width, number of turns, layers and filars, the maximum outside diameter of the secondary wire is calculated. A custom value can be entered into [B118], but this does not

the nearest available diameter e.g. the 0.56 mm value in the example can be rounded down to 0.55 mm standard diameter. [E121] gives the closest rounded down AWG standard wire gauge. If using AWG sized wire, check that the rounded down AWG size is not too big a reduction on the optimum size and not fill the bobbin width. If the reduction is significant, add a turn to the value in [B50] and check if the AWG size suggested is closer to the optimum diameter. Then re-check the primary wind results. A small adjustment to the reflected voltage VOR in [B49] can be used to optimize the primary winding to fill the bobbin winding width.

Secondary winding current density is given in [E122], a value below 10 should be the target to limit transformer temperature rise at full load. If the value is below 3.8, a smaller transformer may be possible, but this is also determined by the primary winding parameters.

## Step 9 – Voltage Stress Parameters

VOLTAGE STRESS PARAMETERS			
SWITCH_DERATING		0.10 %/100	Desired derating factor for switch
VCOLLECTOR		605 Volts	Maximum Collector Voltage Estimate (Includes Effect of Leakage Inductance)
PIVS		27 Volts	Output Rectifier Maximum Peak Inverse Voltage
PIVB		49 Volts	Bias Rectifier Maximum Peak Inverse Voltage

Figure 15. Voltage Stress Parameters.

The default BJT switch derating factor is given in [E126] as 10%, enter a custom value in [B126] if required. [E127] gives an estimate of the maximum collector voltage of the switching BJT based on the maximum bulk capacitor voltage, VOR and an estimate of the leakage inductance spike. If this exceeds the maximum allowed BJT collector voltage, a warning is given in [C127]. If a warning is given, check the BJT derating factor is correct, if it is, select a BJT with a higher  $V_{CBO}$ .

The maximum reverse voltage across the secondary diode is calculated in [E128], add margin to this value before selecting a suitable part. For low output voltage designs i.e. 5 V, the forward voltage drop of the output diode greatly affects efficiency, so it is usual to choose a higher current part to help achieve the target efficiency i.e. >10 times rated output current.

Series Number	Type	VR Range (V)	$I_F$ (A)	Package	Manufacturer
1N5817 to 1N5819	Schottky	20-40	1	Leaded	Vishay
SB120 to SB1100	Schottky	20-100	1	Leaded	Vishay
11DQ50 to 11DQ60	Schottky	50-60	1	Leaded	Vishay
1N5820 to 1N5822	Schottky	20-40	3	Leaded	Vishay
MBR320 to MBR360	Schottky	20-60	3	Leaded	Vishay
SB320 to SB360	Schottky	20-60	3	Leaded	Vishay
SB520 to SB560	Schottky	20-60	5	Leaded	Vishay
MBR1045	Schottky	35/45	10	Leaded	Vishay
UF4002 to UF4006	Ultrafast	100-600	1	Leaded	Vishay
UF5401 to UF5408	Ultrafast	100-800	3	Leaded	Vishay
MUR820 to MUR860	Ultrafast	200-600	8	Leaded	Vishay
BYW29-50 to BYW29-300	Ultrafast	50-200	8	Leaded/SMD	Vishay
ESA1A to ES1D	Ultrafast	50-200	1	SMD	Vishay
ES2A to ES2D	Ultrafast	50-200	2	SMD	Vishay
SL12 to SL23	Schottky (low $V_F$ )	20-30	1	SMD	Vishay
SL22 to SL23	Schottky (low $V_F$ )	20-30	2	SMD	Vishay
SL42 to SL44	Schottky (low $V_F$ )	20-30	4	SMD	Vishay
SBR1045SD1	Schottky (low $V_F$ )	45	10	Leaded	Diodes
SL42 to SL4	Schottky (low $V_F$ )	20-30	4	SMD	Vishay
SBR1045SP5	Schottky (low $V_F$ )	45	10	SMD	Diodes

Table 8. List of Recommended Secondary Diodes That May be used with LinkSwitch-4 Designs.

Step 10 – Additional Parameters

Bias Capacitor - CVCC

Bias Capacitor			
CBIAS		5.38 uF	Bias capacitor is greater than 2uF! Transient response could be unpredictable. For improved and repeatable transient response keep capacitor value < 2 uF
DELTAV_BIAS		100 mV	Voltage ripple on VCC capacitor at zero-load (should be between 0.05 V and 1.6 V)

Figure 16. Bias Capacitor Selection.

The bias capacitor serves three purposes:

1. Energy storage during the start-up procedure. The bias capacitor powers the controller until the bias winding generates enough voltage, which is limited by the voltage on the output capacitor, to power the controller.
2. Acts as an energy reserve between switching cycles to power the controller, particularly at no-load where the switching frequency is low.
3. Forms part of the timing mechanism for the switching frequency oscillator at no-load.

For easy starting into large output capacitance the bias capacitor value can be made large. However, it must be a ceramic type capacitor, an electrolytic capacitor will leak and possibly prevent start-up especially as it ages. Also the bias capacitor must not be so large that the ripple voltage on the VCC pin will be less than 50 mV at the zero load switching frequency. If the ripple is less than 50 mV at zero load, the controller will cease switching and power cycle. It must detect the step in VCC when the transformer discharges to move to the next state in the switching cycle when at zero load.

If the design has a zero load to partial or full load transient requirement, as found for USB charger designs, where the output voltage must not fall below a given limit, the bias capacitor value should not exceed 2 uF. Larger values of bias capacitor result in a very shallow discharge curve across the capacitor. A voltage shifted version of this curve is used to intersect with the internal switching frequency oscillator capacitor charge voltage to start the next switching cycle. If the angle of intersection is too shallow, thermal noise will make the trigger point less predictable and the zero load frequency will vary erratically. The average frequency will be such as to keep the output voltage under zero load to be within specification, but the resulting minimum frequency will allow a transient load to pull the output voltage below the minimum allowed, if the transient coincides with a low frequency cycle.

The bias capacitor ripple should not be allowed to exceed 1.6 V. If  $V_{CC}$  falls by more than 1.6 V in a switching cycle, an extra minimum primary current pulse is issued. This will recharge the bias capacitor

to prevent  $V_{CC}$  falling inadvertently to the sleep level, which would cause a power reset cycle. If this happens too often, the output voltage will rise and may exceed the specification.

The spreadsheet calculates the bias capacitor size to give 100 mV of ripple [E139]. Alternative values can be entered into [B138] and the new ripple level (Delta\_Vbias) will be given in [E139].

Zero-Load Collector Peak Current

VCS\_MIN is the minimum peak voltage that the controller can set across the  $R_{CS}$  resistor. This sets the minimum primary current and hence the minimum energy per switching cycle. On LNK4xx3x, LNK4x14D and LNK4x15D devices there are four discrete levels that can be set, 58 mV, 73 mV, 94 mV and 127 mV. These are set by the resistor  $R_{CS2}$  which can be 100  $\Omega$ , 270  $\Omega$ , 470  $\Omega$  or 1 k $\Omega$  respectively. No other values can be used, there are no intermediate values of VCS\_MIN. LNK40x2S devices only have one level for VCS\_MIN, 88 mV.

VCS\_MIN is used to control the zero load behavior of the circuit, particularly the zero load switching frequency. The higher the VCS\_MIN level, the lower the zero load switching frequency and the lower the zero load power. However, the lower the zero load switching frequency, the larger the output capacitors must be if there is a zero load transient requirement. Larger output capacitors require a larger bias capacitor which cannot be greater than 2 uF in this situation.

A zero load switching frequency of between 1 kHz and 2 kHz should be the target, calculated in [E154]. Use the drop down selection table in [B145] to select the required VCS\_MIN. The required value of  $R_{CS2}$  is given in [E136]. The higher the frequency, the easier it is to start-up and meet zero load transient requirements, but zero load power will be greater.

Dummy Load Resistor  $R_{OUT}$

The value of  $R_{PRELOAD}$  ( $R_{OUT}$ ) can be used to trim the zero load switching frequency [E154] by entering a value in [B152]. Aim to have the dummy load power dissipation [E153] no lower than the bias winding power at no-load [E108]. This aids consistent zero load behavior across production.

Zero-load Collector peak current			
VCS_MIN	73	73 mV	Drives peak current at zero load. Affects zero load frequency and consumption, and 0-100% load step
RCS2		270 Ohm	Resistance for setting VCS_MIN

Figure 17. Zero-Load Peak Collector Current Selection.

Dummy load and no load			
R_PRELOAD		5620 Ohm	Pre load resistor (1%). Affects FSW_NOLOAD, zero load consumption, and 0-100% load step dip
P_PRELOAD		4.4 mW	Preload resistor power consumption at no load
FSW_NOLOAD		1116 Hz	Estimated switching frequency at no load. Adjust with VCS_MIN and R_PRELOAD

Figure 18. Dummy Load Resistor Selection.

### Output Capacitor $C_{OUT}$

The spreadsheet will calculate the maximum size of output capacitor into which the circuit can start up. This is mainly governed by the size of the bias capacitor [E138], which has to supply power to the controller during start-up, and the ratio between secondary and bias winding turns. It can be selected to calculate this for either a constant current load at start-up or a resistive load via the drop down selection menu in [B141]. The level of the constant current load at start-up can be set in [B142], the default level is 75% of IO [E9]. The resistive load is made equal to that required to draw IO [E9] and includes any cable resistance implied by the selected cable compensation [E19].

The calculations do not take into account the effects of primary to secondary leakage inductance. The bias winding is quite effective in harvesting some of this energy and allows for a larger output capacitance than that given in [E144]. It would be reasonable to enter a value into [B145] that is 25% higher than that given in [E144] if the end design is thoroughly tested across a pre-production run.

Output capacitors must be rated to have sufficient current ripple capability i.e.  $\geq$ [E81]. Do not simply increase the capacitor value to meet the ripple requirement, else starting difficulties may occur, the capacitance must not exceed [E145]. Selecting a capacitor with a higher rated voltage will also achieve a higher ripple current rating. Select the capacitor voltage to be  $\geq 1.2 \times VO_{PCB}$ .

### Load Step and Undershoot

In this section the zero load transient response is evaluated. It is essential to have the zero load switching frequency in [E154] greater than the minimum undershoot switching frequency given in [E150]. Adjust VCS\_MIN [B135], COUT\_FINAL [B145 via E144] and  $R_{OUT}$  [B152] to achieve this. Parameters for load step current can be entered in [B148] and minimum undershoot voltage set in [B149].

The zero load switching frequency requirement comes from the operation of a primary side sensing flyback converter. The controller can only sample the output voltage at the end of the transformer discharge period. If a load transient occurs just after the discharge period, the output capacitor will be discharged until the next switching cycle measures the drop in output voltage. Therefore, if the output is not to fall too much, the output must be sampled often enough.

### Start-Up

Enter the allowed start-up time into [B156], 1 second is the default. The spreadsheet calculates the size of the start-up resistor from the current required to charge up the bias capacitor  $C_{VCC}$  from zero to the 'run voltage'  $V_{CC(RUN)}$  and divides it by the BJT low current gain and adds pin leakage currents.

Round down the value in [E157] to the nearest standard value and enter that into [B157]. An estimate of the start-up time is given in [E158].

Output Capacitor			
	Resistive Load	Resistive Load	Select load type for startup testing. This will help estimate the maximum output capacitance that will allow proper startup under any normal operating conditions
LOAD_TYPE			
ICC_STARTUP		1.50 A	Not used for resistive startup calculation
R_LOAD		2.65 Ohm	Equivalent resistive load placed at the end of PCB for simulating load and cable
COUT_ADVISED		2281 uF	Maximum Cout to guarantee proper startup and stability
COUT_FINAL		2281 uF	Total output capacitance on the secondary of the power supply

Figure 19. Output Capacitor Selection.

Load step and undershoot			
RCABLE_EST		0.150 Ohm	Estimated charger cable resistance
I_LOADSTEP		2.00 A	Required maximum current load step from zero load
V_UNDERSHOOT		3.70 V	Accepted undershoot during maximum load step
FSW_UNDERSHOOT		877 Hz	Minimum frequency at no load in order to satisfy undershoot requirements

Figure 20. Load Step and Undershoot Parameters.

Startup			
STARTUP_TIME		1.00 second	Desired startup delay time
R_STARTUP		14.70 MOhm	Startup resistor (default calculation assumes a standard resistor for desired startup)
STARTUP_TIME_FINAL		1.00 second	Final startup time assuming resistor value Rstartup

Figure 21. Start-up Resistor Value.

**Feedback Resistors**

$R_{FB1}$  sets the minimum HT voltage at start-up that will allow the controller to continue to run.  $73\% \text{ of } \sqrt{2} \times V_{AC\_MIN}$  is the default and will generally be satisfactory for most designs but an alternative value may be entered in [B160] for special circumstances. It also sets the brown-out level which is 43% of this value.

$R_{FB2}$  in conjunction with  $R_{FB1}$  sets the output voltage and is calculated in [E162]. Two resistors in series can be used to make up  $R_{FB1}$ , one high value and one low value. The low value may be trimmed in

value to obtain an accurate output voltage. In fact the spreadsheet will tend to result in a slightly high output voltage as the high current value of output diode volt drop is used, but the chip measures the output voltage when the secondary discharge current is close to zero.

**Step 11 – No-Load Power Estimator**

Here, all the no-load losses are calculated and summed to give a no-load power estimate. Aiming for a 27 mW target should result in a 30 mW design with adequate margin.

Feedback Resistors			
V_UV+		92.9 V	DC voltage at which power supply will start up
RFB1		7500 Ohm	Initial estimate for top feedback resistor (std value, use 1% tolerance)
RFB2		2370 Ohm	Initial estimate for bottom feedback resistor (std value, use 1% tolerance)

Figure 22. Feedback Resistor Values.

NO LOAD POWER ESTIMATOR			
EFF_NOLOAD		0.60 %/100	Assumed efficiency at no load (0.6 if no better data available)
VAC_INPUT		230 Volts	AC input voltage for no load power estimation
PB_NOLOAD		4.1 mW	Bias winding power consumption estimate at no load
P_PRELOAD		4.4 mW	Preload resistor power consumption at no load
P_STARTUPRES		7.2 mW	Energy dissipated by the startup resistor
PSW		6.6 mW	Power losses of the switch and clamp
P_NOLOAD_TOTAL		28 mW	Estimated no load power consumption. Affected by Vcs_min

Figure 23. No-Load Power Estimation.

## Step 12 – Results Check

Now that all the variables have been entered, the results can be assessed.

1. Check entered values and options are correct.
2. Check core gap is manufacturable [E93], generally >0.1 mm. If not, increase secondary turns [B50] which will increase the gap for the same inductance, or reduce Flux Density [B86] which lowers inductance, then re-optimize transformer.
3. Check primary current density [E103]. If low, try decreasing layers [B98]. This will reduce leakage inductance and improve efficiency.
4. If primary current density too high, increase layers.
5. Check bias voltage at no-load [E107] is between 8 V and 9 V. Lower voltage improves no-load power, higher voltage aids start-up into difficult loads.
6. Check secondary wire diameter is practical to wind on bobbin used i.e. not too large. If so, increase filars [B117], if this results in the secondary current density being too high [E122] increase layers [B116]. Alternatively, just reduce the single filar wire size to an acceptable diameter. This will not fully fill the bobbin winding window width and leakage inductance will increase, but it might be acceptable. Spreading the secondary winding evenly across the bobbin width will lessen the increase in leakage inductance.
7. Check peak collector voltage [E127] is lower than the derated maximum level.
8. Check PIV applied to the output diode [E128] is below the derated voltage rating of the selected output diode.
9. Check PIV applied to the bias diode [E129] is below the derated voltage rating of the selected bias diode.
10. Check high frequency ripple current rating of the chosen output capacitors against the secondary RMS current [E81].
11. Check bias voltage delta at no-load [E139] is between 50 mV and 1.6 V. It will tend to be a few hundred mV.
12. If there is a no-load transient test for the design, check that [E150] < [E154]. As [E154] is an estimate, this relationship must be tested and verified on the prototype circuit.

Component values for the design are found in:

$C_{IN1} + C_{IN2}$ CIN	[E13]
Selected device	[E20]
Q1 BJT	[E24]
T1 Core	[E35]
T1 Bobbin	[C37]
T1 Primary turns	[E51]
T1 Primary layers	[E98]
T1 Primary wire diameter	[E101, E102]
T1 Secondary turns	[E50]
T1 Secondary layers	[E116]
T1 Secondary filars	[E117]
T1 Secondary wire diameter	[E120, E121]
T1 Bias turns	[E106]
T1 Core gap	[E93]
$C_{VCC}$ Bias capacitor value	[E138]
Total output capacitance $C_{OUT}$	[E145]
Output capacitance ripple	[E81]
$R_{OUT}$ Dummy load	[E152]
$R_{HT}$ Start-up resistor	[E157]
$R_{FB1}$ Upper feedback resistor	[E161]
$R_{FB2}$ Lower feedback resistor	[E162]
$R_{CS}$ Current sense resistor	[E74]
$R_{CS2}$ $V_{CSMIN}$ setting resistor	[E136]
Bias diode $V_{RRM}$	[E129] usually 1N4148
$D_{OUT}$ $V_{RRM}$	[E128]
$D_{OUT}$ Peak current	[E79]
$D_{OUT}$ RMS current	[E780]

Explore the spreadsheet for more informative data.

Step 13 - Further Component Selection Input Stage

 


Figure 24. Input Stage.

The recommended input stage is shown in Figure 24. It consists of a fusable element ( $R_{F1}$ ), input rectification ( $D_{IN1-4}$ ), and line filter network ( $C_{IN1}$ ,  $C_{IN2}$ ,  $L_{IN1}$  and  $L_{IN2}$ ).

The fusable element can be either a fusible resistor or a fuse. If a fusible resistor is selected to limit switch on inrush current, use a flameproof type.

Depending on the differential line input surge requirements, a wire-wound type may be required. Avoid using metal or carbon film types as these can fail due to the inrush current when VAC applied repeatedly to the supply. A value of 10  $\Omega$ , 2 W is a typical value.

$C_{IN1}$  and  $C_{IN2}$  are approximately equal values, to provide the input pi filter. It is advisable to make at least  $C_{IN2}$  a low ESR type.

$L_{IN1}$  should be between 220  $\mu$ H to 2.2 mH, and have a current rating of approximately:

$$IL_{IN1} = (40 \times 10^3 \times C_{IN2}) + \frac{P_{OUT}}{V_{HT(MIN)}}$$

Although inductors have a current rating for a given temperature rise, that current is often the level at which the inductance has fallen to 90% of its low current value. So given that it is not desirable that the inductor saturates and reduces in inductance, hence reducing its filtering capability, it is a reasonable guide, though the inductor will be operating at a much lower average current than its rating.

The best EMI results are not always achieved by putting in the highest available inductor value. The inductor will have a self resonant frequency (SRF) which tends to decrease with inductor value. A high value inductor may well have a SRF that coincides with one of the switching generated frequencies and it will have minimal attenuating effect upon it. Decreasing the inductor value may move the SRF out of a sensitive frequency band and give better EMI results. Alternatively, a resistor can be placed in parallel with the inductor to damp the SRF, about 4.7 k $\Omega$  would suffice.

$L_{IN2}$  is optional and helps with higher frequency EMI emissions, >20 MHz. It is usually a low value SMT ferrite bead inductor of the order of 150  $\Omega$  to 1000  $\Omega$  impedance at 100 MHz.

**Primary Clamp Components**

- $D_{C1}$ : 1N4007 / FR107, 1 A, 1000 V
- $R_{C1}$ : 100  $\Omega$  – 300  $\Omega$
- $C_{C1}$ : 220 pF – 1000 pF 500 V
- $R_{C2}$ : 330 K $\Omega$  - 680 K $\Omega$

The clamp arrangement, shown in Figure 25, is suitable for LinkSwitch-4 designs. Minimize the value of  $C_{C1}$  and maximize  $R_{C2}$  while maintaining the peak Collector voltage to  $<(V_{CBO} \times \text{derating factor})$ . Larger

 


Figure 25. Primary Clamp Components and Effect of Diode Recovery Time of FEEDBACK Pin Voltage.

values of  $C_{C1}$  may cause higher output ripple voltages due to the longer settling time of the clamp voltage impacting the sampled voltage on the feedback winding, particularly at low loads. A value of 470 K $\Omega$  for  $R_{C2}$  with 470 pF for  $C_{C1}$  and 100  $\Omega$  for  $R_{C1}$  is a recommended starting point for the RCD design. Verify that the peak collector voltage is less than  $(V_{CBO} \times \text{derating factor})$  under all line and load conditions including start-up.

The clamp diode choice is governed by what weight is given to various performance factors and cost. Customers usually favor lowest cost at the power level and application type covered by LinkSwitch-4 devices. This indicates the use of a low-cost 1N4007 slow recovery type diode. Note from Figure 25, that a slow recovery diode has a lower frequency ring, and faster settling time, this can be useful in reducing EMI.

The choice of snubber components affects no-load power, no-load frequency, no-load output voltage stability, peak collector voltage, efficiency and EMI.

Reducing  $C_{C1}$  will reduce energy lost in the clamp, reduce the no-load switching frequency and hence reduce the no-load power. The compromise is that the peak collector voltage is increased and EMI emissions may increase, but as long they are within the set limits it is an option to control no-load power.

### Supplementary Base Drive

Resistor  $R_{SBD}$  is used on SO-8 packaged devices to provide extra base drive in higher power applications (7.5 W – 18 W) without increasing package dissipation.

It should have a value of between 220  $\Omega$  and 390  $\Omega$  for standard designs, or 100  $\Omega$  to 150  $\Omega$  for applications using the EasyStart feature. Refer to 'Step 15 – First Time Start-up and Troubleshooting' to check that correct value has been selected.

### Output Diode Snubber

It is advisable to allow for an output diode snubber in the application design. It may not be required, but will aid EMC development if there are places allocated on the PCB for these components. The snubber consists of a resistor in series with a capacitor and are then placed in parallel with the output diode. The snubber dissipates energy during operation and reduces efficiency, so it is advisable to only provide as much snubbing as is required to pass EMC requirements. A 10  $\Omega$  resistor in series with a 1 nF ceramic capacitor is a good starting point. As a guide, the capacitor voltage rating should be equal or greater than the output diode voltage rating.

### Current Sense Resistor $R_{CS}$

The value of  $R_{CS}$  [E74] may need some adjustment to obtain the desired maximum output current i.e. the position of the constant current region of the VI curve. This is due to the effects of the bias winding, primary clamp and core losses drawing energy that would otherwise go to the secondary. There is a nominal correction factor in the calculations, but the amount of correction required varies with power level and transformer design. Once the value has been adjusted to give the desired current level, it will not change much across production of the particular design. Some effort will have to be made in centralizing the design so it remains within specification across production, due to component tolerances, if required.

### $V_{CS(MIN)}$ Setting Resistor $R_{CS2}$

LNK4xx2S parts do not need this resistor to set  $V_{CS(MIN)}$ , but a 1 k $\Omega$  resistor should be included to enhance ESD immunity.

### Voltage Feedback Resistor $R_{FB1}$

If  $R_{FB1}$  is to be SMT then it should be at least 0805 size, preferably two in series. During ESD events, a large voltage can be present across this resistor and it can be damaged.

## Step 14 - Transformer Topology

The starting point for transformer design is not always the same because it depends on constraints such as operating frequency and transformer size. The transformer interacts with nearly all other design considerations so it is impossible to design the transformer in isolation. These interactions need constant consideration and review, and the transformer design needs to be iterated to accommodate an acceptable compromise throughout the design of the power supply.

For best efficiency, use a core with as high a cross section area as affordable. Also ensure that the winding window width is enough to accommodate the secondary winding. The aim is a single layer of secondary that fully fills the winding width; a 12 V design will therefore need a wider width than a 5 V design at the same power level.

### Common LinkSwitch-4 Transformer Topologies

A simple 3 winding transformer structure has been developed that is suitable for all LinkSwitch-4 designs up to 18 W. It may be necessary to use a more complicated sandwiched secondary type structure with 5 windings, including a foil screen, at 7.5 W or greater to minimize primary to secondary leakage inductance to optimize converter performance. However, in a specific application a 5 winding structure is not guaranteed to be superior to a 3 winding design. For cost and manufacturing simplicity, it is recommended that a 3 winding transformer is tried first.

EMI conducted emissions are optimized by altering the number of turns on the compensation winding. The number of turns on the bias winding remains unchanged as it is designed to power the LinkSwitch-4 controller. It is the imbalance of the bias and compensation winding turns, which are wound in the opposite sense, which provides the compensation effect. The best balance is usually found within  $\pm 2$  turns. Fractional turns can be used on the compensation wind for optimal balance.

BJTs have slower switching edges than power MOSFETs, hence a screen winding between the primary and the core is not usually required. It tends to add significant capacitance to the collector node which degrades efficiency and no-load power.

Wire size should be chosen such that each layer completely fills the bobbin winding width. This can be compromised a little when a turn or two is added or subtracted from the compensation winding, to obtain the best EMI emissions performance.

Z-winding the primary, where each layer end is brought back to the start side before winding the next layer, reduces the effect of inter layer capacitance and significantly reduces the no-load power.

Do not use unnecessary layers of tape as this will increase leakage inductance and reduce efficiency.

### Simple 3 Winding Transformer

The 3 winding transformer is wound as the primary first, with the collector node pin as the start so that it is screened by succeeding primary layers from the secondary.

The second winding is a combined bias winding and compensation winding wound as a trifilar (3 strand) winding. It is arranged that the bias and compensation wind senses are in the opposite direction. On average this tends to make the trifilar winding have no net electrostatic voltage change, so it acts like a foil screen, though an imperfect one. Two strands are used for the bias wind and a single strand for the compensation wind. It is possible to swap this to help obtain a better compensation balance, or reduce  $V_{CC}$  at maximum load if it is too high.

The third winding is the secondary, wound in triple insulated wire.

A contact to the core material is made with tinned copper wire and taken to +HT.

 


Figure 26. 3 Winding Transformer Construction.

**5 Winding Transformer**

The 5 winding transformer is wound as the primary first, with the collector node pin as the start so that it is screened by succeeding primary layers from the secondary.

The second wind is a complete turn of copper foil that has the same width as the bobbin winding window width. Care must be taken to ensure the ends of the foil are insulated with tape so as not to form a shorted turn. This is connected to the Bias wind GROUND pin.

The third winding is the secondary, wound in triple insulated wire.

The fourth winding is a combined bias winding and compensation winding wound as a trifilar (3 strand) winding. It is arranged that the

bias and compensation wind senses are in the opposite direction. On average this tends to make the trifilar winding have no net electrostatic voltage change, so it acts like a foil screen, though an imperfect one. Two strands are used for the bias wind and a single strand for the compensation wind. It is acceptable to swap this to help obtain a better compensation balance, or reduce  $V_{CC}$  at maximum load if it is too high.

The fifth winding is the remaining turns of the primary.

A contact to the core material is made with tinned copper wire and taken to +HT.

 


Figure 27. 5 Winding Transformer Construction.

### Step 14 – PCB Layout Guidelines

Good layout practice helps with:

- Achieving low EMI
- Good ESD immunity
- Thermal optimization
- Design for manufacture

Some simple, good practices and guidelines for routing are:

- Make track widths appropriate for current to be carried
- Space tracks according to voltage difference between them
- Keep tracks as short as possible.
- Prioritize critical paths: highest first (high current, high frequency, high-voltage)
- Keep thin tracks away from board edge
- Route tracks to center of a connecting pad

#### Functional Considerations

Loops (signal paths and ground returns) that carry fast edges are a potential source of radiated EMI. The faster and larger the current fluctuations, the higher the radiated EMI power will be. Also the larger the area enclosed by the loop, the higher the level of EMI. The latter is where good PCB design can help, and poor design can cause a real problem. The key is to keep current loops small and run out/return tracks close together. Doing so keeps the loop area and radiated emissions down.

#### Critical Connections

- The track between the feedback resistor  $R_{FB2}$  and LinkSwitch-4 GROUND pins must be as short as possible to avoid poor performance.  $C_{VCC}$  recharge currents and primary current out of the

GROUND pin must not generate volt drops in the GND tracking that interfere with voltage on the FEEDBACK pin due to the GND connection of  $R_{FB2}$ .

- The impedance driving the FEEDBACK pin is quite high. As a result, the FEEDBACK pin waveform can easily be distorted by parasitic capacitive coupling from the primary BJT switch. When laying out the PCB, it is important to minimize stray capacitance between the switch and feedback node. This can be achieved by placing the  $R_{FB1}$  and  $R_{FB2}$  resistors adjacent to the FEEDBACK pin, making the FB node small in area.
- The tracks between the BJT base and emitter to the BD and ED pins of the IC must be as short as possible to avoid poor EMI performance.
- The tracks between the transformer and BJT collector must be as short as possible and the total area as small as possible. If there is a primary clamp circuit, the diode anode should connect to the collector, not the resistor  $R_{C1}$ , to minimize the high dv/dt node area.
- The current sense resistor  $R_{CS}$  programs the power supply giving it the required rated current. The connections should be as small as possible and the track as wide as possible. The  $R_{CS}$  resistance is small and any track resistance will affect the operation of the power supply. There should be dedicated tracks between  $R_{CS}$  and both  $C_{IN2}$  and  $R_{CS2}$ . Highlighted nodes in Figure 29.
- Mount  $R_{CS2}$  very close to the CS pin of the IC.
- Having a star point at the ground of the IC to all grounded components will help EMC and circuit performance, see Figure 28. Note that the bias wind,  $D_{BIAS}$  and  $C_{VCC2}$  form their own close small loop, then its GND is connected to the star point.


 
 


Figure 28. Star Point Ground Connections.

 

PI-8164d-110116

Figure 29. Chip GND,  $R_{CS}$ ,  $R_{CS2}$ ,  $C_{IN2}$  Connections.

PI-8164a-110116

Figure 30. Primary Current Loop.

- The primary current loop (highlighted in Figure 30) must be kept as small as possible because it has a moderate amplitude and fast edges so needs low impedance (short, wide) paths. Keeping the enclosed area as small as possible will help to reduce impedance and EMI.
- The  $V_{CC}$  power rail needs to be tightly decoupled to reduce any EMI resulting from the switching action of the BJT and the recharging of the  $V_{CC}$  capacitors; highlighted in Figure 31. Two  $V_{CC}$  capacitors are usually required, each half the value given in [E138]. Keep  $D_{BIAS}$  and  $C_{VCC2}$  very close to the bias wind pins on the transformer to form a very tight loop for the bias capacitor recharge current, this significantly helps radiated RF EMC.  $C_{VCC1}$  must be very close to the  $V_{CC}$  and GROUND pins of the IC.
- One capacitor can be used, but this requires that the IC is also next to the transformer bias wind pins and this can be difficult to arrange.
- The output current path is where current from the output diode is smoothed by an output electrolytic capacitor to make a DC output and to reduce EMI. Due to high amplitude and fast switching voltages and currents, it is important that the loop from transformer, diode and capacitor is made as small as possible. Keeping the secondary snubber loop small will also help. The track area of the secondary and output diode anode node must be kept small to minimize capacitive coupling from the high  $dv/dt$ . If a through hole output diode is used and mounted vertical to the PCB, place the body anode end next to the PCB and the cathode end terminal

 
 
Figure 31.  $V_{cc}$  and Bias Current Loops.

Figure 32. Input Components and Tracks Susceptible to Noise from BJT Collector Node.

lead loop down to the output capacitor  $+V_E$  track. Unfortunately this is not optimal for good thermal cooling of the diode. The cathode side track can be made large, as it only has a small ac ripple voltage on it. It can act as a heat sink but the diode heat has now to flow along the cathode lead before reaching the track. Testing may be required to determine the best compromise. An SMT diode would not have this problem.

- EMC will be reduced by ensuring a small loop area, for the primary clamp circuit. Keep the components close to the transformer primary pins.
- Noisy paths (shown in red in Figure 32) should be kept away from the input loop (shown in green) to reduce capacitive coupling and improve EMC. In particular, keep the BJT away from the input diodes,  $L_{IN1}$  and  $R_{IN}$ . BJT collector node is the noisiest.

- A Y capacitor is effective at reducing EMI conducted emissions, particularly in the upper bands of 10 MHz plus. Power levels of 10 W and above may benefit from the use of a Y capacitor. However, only low values should be used in wall adapters, about 470 pF maximum, due to leakage currents presenting an unpleasant mild shock risk. The Y capacitor should be connected from the  $+HT$  pin of the transformer primary to the  $-V_E$  of the secondary output as shown in Figure 33. The Y capacitor provides a path for the high frequency current through the transformer, capacitively coupled from the primary to the secondary windings, to loop back to the primary side, instead of flowing down the output lead in a loop via the EMI test equipment (LISN) and back up in a loop via the AC input leads to the primary side. Currents flowing through the Y capacitor will not be measured by the LISN so the resulting measurements will be lower.

 


Figure 33. Y Capacitor Connection.

 


Figure 34. Alternative Y Capacitor Connection.

- Figure 34 shows an alternative Y capacitor connection and output diode arrangement that may be more effective in some designs.

**Thermal Considerations**

Thermal management of enclosed power supplies is challenging. PCBs are usually single-sided and do not have much copper to conduct heat away from hot spots. In a sealed plastic enclosure, there is little air circulation. Consider the following:

- Add printed copper (contrary to some EMC considerations).
- Keep hot components away from other components.
- Use 2 oz/in<sup>2</sup> copper.
- Use double sided boards.

The hottest components are likely to be the BJT and the output diode.

**BJT Thermal Management**

The LinkSwitch-4 drives the BJT in such a way as to greatly reduce conduction and switching losses. However, thermal management is still important. For good EMC, the BJT is required to be close to the transformer and input capacitors, but these components also run warm. Do not place the BJT body in contact with any other compo-

nents. Although the collector node should be kept physically small to reduce EMI, it is possible to use the connection to conduct heat away from the BJT, to the transformer. Base and emitter connections may be made wide to help conduct heat away from the BJT and into the PCB substrate.

Arrange for a substantial amount of copper to the GND pins. These pins conduct heat out of the chip, particularly on the SO8 packaged parts which dissipate higher power.

**Output Diode Thermal Management**

The output diode dissipates significant power. Consider the following when placing the diode:

- The connection between transformer secondary and diode (usually the anode) has a high frequency voltage on it so should be kept small in order to reduce stray capacitance and radiated EMI.
- The transformer may act as a heat sink for the diode so keep the connection short.
- Long leads on axial diodes increase the thermal resistance from the die to the PCB. Laying the diode flat reduces total lead length.
- The printed copper connected to the DC side of the diode (usually the cathode) may be large without radiated EMI so may be used as a heat sink.

**ESD Considerations**

PCB layout for ESD should ensure low impedance from the source of the ESD transient on the output, to ground via the mains supply. Transformer insulation should present higher impedance to the surge than the spark gap. The spark gap must break down before the transformer insulation does.

A spark gap does not divert all the energy of an ESD event away from the control circuitry. The ESD strike is a low impedance, very high dv/dt event, and the capacitance between the secondary, bias, screen and primary windings will cause a high current to flow from the secondary side to the primary side tracking, particularly from the transformer GND and +HT pins. Also, when the spark gap breaks down, the transformer capacitances are discharged, causing a high current flow in the opposite direction. The circuitry will probably be more susceptible to one direction than the other, so if the initial strike has no effect, the spark gap breakdown may cause a failure.

The PCB has to provide the lowest possible impedance to ground through the spark gap.

- Distance between the spark gap points should be the minimum and no more.
- Some customers can work with a 4.6 mm gap with a routed slot. Check with the customer before designing the PCB. The standards state 6.4 mm.
- The spark gap should have short, wide tracks from as close to the output as possible, to as close to the mains terminations as possible.
- It should go to the AC side of the rectifier bridge rather than the DC side, and directly to the AC terminal, not through any input surge limiting resistor.
- The primary-to-secondary creepage path, that is, the path over the PCB surface, must be shortest through the spark gap.
- The greater the difference between the spark gap length and the other primary to secondary creepage distances the better.
- Spark gap terminals should be pointed to minimize the spark overvoltage.
- Be aware of discharge paths through air – from output caps to core, for example. A common path is from the secondary terminals to the core, which is usually connected to the +HT which may not be a problem, but it may be connected to the chip GND for EMI purposes; this would probably lead to a failure.
- Cut the leads of through-hole components flush with the solder fillet so there are no sharp points to encourage sparking along an undesirable path.
- Input filter inductors  $L_{IN1}$  and  $L_{IN2}$  should have single point short spark gaps in parallel with them, to prevent inductor damage during an ESD event, especially if a Y capacitor is used. This spark gap can be the minimum gap allowed by the PCB layout rules, say 0.25 mm. Each side of the gap should be a single point so a minimum of additional capacitance is added across the inductor which could reduce its filtering effectiveness.
- As a large current may pass along the chip GND tracking, it is important that the GND tracking layout guidance is followed.
- Always include  $R_{CS2}$  in LNK4xx2S designs at 1 k $\Omega$ . It affords some protection to the primary CURRENT SENSE pin from ESD events.
- Include a low value resistor in series with  $D_{BIAS}$  of 1.2  $\Omega$ . This greatly enhances ESD immunity. It does have a side effect of causing a slight uplift in no-load output voltage of about 50 mV/ $\Omega$ , the higher the resistance the greater the uplift.
- Some customers require ESD immunity up to 20 kV+, this can be challenging. An additional capacitor, 100 pF / 220 pF between the BASE DRIVE and EMITTER DRIVE pins, can provide extra immunity. The chip may be glitched into the restart cycle, but should not fail catastrophically at the higher test voltages.

## Step 15 – First Time Start-up and Troubleshooting

### Safety

Offline power supplies, particularly in a development situation, can exhibit hazards including but not limited to electric shock, high temperatures, fire and smoke. They should be operated and used only by competent, trained personnel. In particular:

- The unit to be tested should be checked for design and build errors before applying mains power;
- The unit under test should be powered via a suitable isolating transformer and a variac;
- Hazardous voltages are present in both normal and abnormal operating conditions;
- Insulation between high-voltage and low voltage parts may not provide safety isolation;
- All connections should be regarded as LIVE and HAZARDOUS;

- Before modifying the circuit or applying a soldering iron to add/remove components, it is essential to discharge the bulk capacitors completely. Also the  $C_{VCC}$  capacitors must be completely discharged. Damage can occur to the chip if there is charge on the  $C_{VCC}$  capacitors and a soldering iron is applied to the chip pins or associated components. This is in addition to the usual shock hazard presented by residual charge on capacitors.

Attach test points and connect oscilloscope probes to:

1. Collector node, use HV x100 probe 50 V / div. DC, GND clip to chip GND node;
2. VCC node, 5 V / div. DC, GND clip to chip GND node;
3. –HT/RCS node, 20 mV / div. DC inverted for clarity, GND clip to chip GND node. This should be a small loop area RF type connection across  $R_{CS}$  to acquire accurate waveforms.

Monitor AC input with DMM or metered AC source and monitor output with DMM or electronic load.

Set to zero AC voltage input and no-load. Set scope to auto run and 10 ms/div time base.

Assuming a standard design;

Turn on AC source and increase to about 40 VAC.

Collector node should increase to  $\sqrt{2} \times$  AC input.

$V_{CC}$  should ramp up to  $V_{CC(RUN)}$ , then quickly discharge back to  $V_{CC(SLEEP)}$ , then ramp up again and repeat. The output remains at zero volts.

If the  $V_{CC}$  remains low,  $\sim 0.7$  V, then check the chip is mounted correctly. Measure the EMITTER DRIVE pin voltage, if it is  $\sim 0.7$  V above the  $V_{CC}$  level, then the chip has been damaged and must be replaced.

Switch scope to Normal sweep and trigger from the  $V_{CC}$  node channel, -ve edge and set level to trigger just below  $V_{CC(RUN)}$ . Zoom in to where  $V_{CC}$  just starts to fall and locate the collector and  $V_{RCS}$  pulses.

Captured waveforms should look similar to Figure 35.

 


Figure 35. Start-Up Waveforms Where  $V_{IN}$  is Below UVLO Level.  
CH1 = Collector Node, CH2 =  $V_{RCS}$ , CH3 =  $V_{CC}$

Sequence of events;

1.  $V_{CC}$  rises to  $V_{CC(RUN)}$   $\sim 13.5$  V;
2. LinkSwitch-4 wakes up, initializes and draws a higher current  $I_{VCC(RUN)}$  and  $C_{VCC}$  starts to discharge.
3. Once initialized, a single pulse is issued (Probe Pulse). This measures the voltage level of +HT via primary/bias winding turns ratio plus the value of resistor  $R_{FBI}$ ;
4. As AC/HT level is below UVLO, the probe pulse terminates after about 600 ns;

 


Figure 36. Start-Up Waveforms Where  $V_{IN}$  is Above UVLO Level.  
CH1 = Collector node, CH2 =  $V_{RCS}$ , CH3 =  $V_{CC}$

5. No more pulses are issued and  $V_{CC}$  discharges to  $V_{CC(SLEEPY)} \sim 4.5$  V;
6. LinkSwitch-4 goes to sleep and  $V_{CC}$  rises again and the cycle repeats.

Increase the AC supply to  $\sim 90$  VAC, the circuit should run continuously and the output voltage should rise to the designed level.

To compare the probe pulse when  $V_{IN}/HT$  are above UVLO level, turn off the AC source, discharge the bulk and  $V_{CC}$  capacitors and set the scope to single shot. Turn on the AC source and the scope will trigger near the probe pulse. The resulting waveforms should look similar to Figure 36.

Notice that the BJT ON-time has increased to  $\sim 1.8$   $\mu$ s and  $V_{RCS}$  reaches the  $V_{CS(MIN)}$  level set by  $R_{CSZ}$  or the single level set by the LNK40X2S parts. It is the  $V_{CS(MIN)}$  threshold that terminates the probe pulse when the UVLO level is exceeded. This time, after the probe pulse, the circuit continues switching at the maximum rate until the output voltage reaches its design level. The LinkSwitch-4 draws power from  $C_{VCC}$  capacitance until the bias winding generates enough voltage to charge the capacitance and power the chip as can be seen in Figure 37 and Figure 38.

 


Figure 37. No-Load Start-Up Detail.

The  $V_{CC}$  voltage is designed to be 8 V – 9 V at no-load, but when supplying current to the output when under load or during start-up, when the output capacitance is being charged, the higher primary current stores more energy in the leakage inductance. This is harvested by the bias winding, which is more closely coupled to the primary, and causes  $V_{CC}$  to rise above the no-load level.

Care must be taken to ensure  $V_{CC}$  does not rise above 16 V, else the chip may be damaged.

The bias winding voltage is related to the output voltage by the secondary/bias turns ratio. Initially the output voltage is zero due to the zero charge on the output capacitance and it takes time for the output voltage to rise to a level where enough voltage is generated by the bias winding to power the chip. When starting into no-load, all the generated output current,  $I_{CC}$ , charges the output capacitance, so the output voltage rises quickly, so the bias winding soon reaches a level where it can power the chip. During this time the voltage on  $C_{VCC}$  will only fall by about 5 V.

Start-up when fully loaded, particularly into a CC load, charging the output capacitance takes much longer as the available current to charge the output capacitance is now only  $I_{CC} - I_{LOAD}$ . This allows  $V_{CC}$  to fall much lower before the bias winding can supply power, see Figure 38. If  $V_{CC}$  is allowed to fall to  $V_{CC(SLEEPY)}$  the chip will cease switching and the start-up process will begin again and the circuit may never fully start-up. To avoid this check that  $V_{CC}$  does not fall below 6 V during start-up, or at least 5.5 V as an absolute minimum but with reduced production tolerance.

Starting into a highly capacitive load also runs the same risk.

 


Figure 38. Start-up into Full Load.

If start-up problems are encountered:

1. Reduce the output capacitance. Retaining the can size increases the rated voltage and maintains the ESR and current rating of an electrolytic capacitor. If there is a no-load transient specification, reduce  $V_{CS(MIN)}$  to compensate i.e. increase no-load frequency.
2. Increase the value of maximum current  $I_{CC}$  for the design to charge the output faster.
3. Increase the value of  $C_{VCC}$  but do not exceed 2.2  $\mu$ F.
4. Use a LNK40x4D, with the EasyStart feature.

#### No-Load Power

A target of 30 mW no-load power is usually easily achievable using the component values suggested by the design tool and a 'Z' wound primary.

Optimization may be required where there is insufficient margin or meeting USB dynamic transient response has increased the no-load power level.

To improve no-load power, the following steps can be taken;

1. Start-up resistor can be increased. 30 M $\Omega$  is a value that is usually used to provide a fast sub 1 second start-up, but 40 M $\Omega$  should just be OK across production spreads for a universal input application. Above 40 M $\Omega$  BASE DRIVE pin leakage at higher temperatures can cause problems.
2. The primary clamp/snubber components can be made less lossy. Reducing the value of the capacitor can be helpful if using a slow clamp diode (1N4007). This will reduce the no-load frequency.
3. Increase the value of the dummy load resistor. Ideally, the power dissipated by the dummy load should be equal to the power dissipated by the IC. This helps to control the no-load output voltage to the desired level across production variations. Leakage inductance might allow a 25 or 50% increase in dummy load resistance without incurring no-load output voltage drift, usually upward.

(2) & (3) will result in the no-load frequency reducing, which is good for no-load power as switching losses which are dominant at 230 VAC, but this may compromise USB transient response performance. On LNK40x3/4 devices, no-load frequency and USB transient response performance can be restored by selecting a lower level of  $V_{CS(MIN)}$ . No-load frequency will increase again, but the energy per cycle has been reduced.

Thorough pre-production testing would be required to check the suitability of these changes as they depart from the safe recommended design values.

### SBD Resistor Check

Referring to Figure 46, for a standard design, if the value of the SBD resistor is correct, then the time period t3 – t4 should be visible when monitoring the BASE DRIVE pin voltage. It will appear as a slight step down towards the end of the base drive period and should be present from 90 VAC to 240 VAC on a universal input design. Beyond 240 VAC, the period may reduce to zero, this is OK and not critical. Referring to Figure 50, for designs using EasyStart, t3 – t4 must be visible up to 264 VAC in order for EasyStart to function at all input voltages and aid starting.

### Initial Basic Design Check List

- Check design specification points met i.e. VI curve, no-load power, efficiency, start-up time.
- Check component temperatures at maximum load and at maximum and minimum input voltages.
- At maximum load  $I_{CC}$ , peak CS voltage should be about 70-85% of  $V_{CS(MAX)}$ .
- Check  $R_{CS}$  voltage waveform at maximum power, load transient and start-up at maximum and minimum input voltages for signs of transformer saturation.
- Check peak collector voltage at maximum load, transient load and start-up at maximum input voltage.
- Check output and bias diode maximum reverse voltage stress.
- Check short-circuit output current at maximum input voltage with  $R_{CS}$  shorted and un-shorted.
- Check no-load output voltage at maximum input voltage with  $R_{CS}$  shorted.
- At no-load, the peak of the AUX voltage must be greater than 6.5 V.
- Check AUX voltage at maximum output power and maximum input voltage.
- What is the ESD voltage at which the spark gap flashes over with the transformer removed from the circuit? Does the PCB flash over at points other than the spark gap?
- What is the ESD voltage at which the transformer flashes over between primary and secondary, when it is tested out of the circuit with primary pins shorted and secondary pins shorted? Is this greater than the PCB spark gap ESD breakdown voltage?

## LinkSwitch-4 Functional Description

### FEEDBACK Pin

The transformer voltage is monitored by dividing the bias (feedback) winding voltage and feeding the signal into the FB node. The signal contains all the information necessary for voltage regulation, current regulation, valley switching and protection of the BJT:

1. Input voltage ( $V_{HT}$ ).
2. Collector voltage.
3. Idle ring voltage peaks and valleys.
4. Output voltage before the output diode.
5. Charge time (primary conduction).
6. Discharge time (secondary conduction).

 


Figure 39. Bias Winding Feedback Waveform.

When bias winding voltage goes negative, an active internal circuit provides the current required to hold the FEEDBACK pin at zero volts. Current sourced from FEEDBACK pin matches current in upper feedback resistor  $R_{FB1}$ . Current in lower feedback resistor  $R_{FB2}$  is zero. Current sourced from FEEDBACK pin is internally translated to a positive voltage that represents a scaled bulk voltage.

 


Figure 40. Internal Virtual Ground Amp Holds FEEDBACK Pin at Zero Volts for  $-V_E$  Input.

The controller measures the FB source current to determine the voltage across the primary, and applies two thresholds,  $I_{FBHT(LO)}$  and  $I_{FBHT(START)}$ \*

$I_{FBHT(LO)}$  is the threshold at which the primary voltage might be too low to sustain normal operation, or it may indicate that the FEEDBACK pin is not connected to the feedback winding due to a fault. When detected, drive to the primary switch is disabled so  $V_{CC}$  decreases. When  $V_{CC}$  falls to  $V_{CC(LOW)}$ , the controller requests a new switching cycle but this is negated by the low mains condition. Therefore, the voltage continues to fall to  $V_{CC(SLEEP)}$  and the controller goes to sleep and a restart cycle is initiated.

$I_{FBHT(START)}$  is used by the first pulse, the probe pulse, to establish that the HT voltage level is high enough to sustain the start-up cycle safely and give a smooth monotonic output voltage rise.

 


Figure 41. Feedback Winding Voltage Waveform and Current into FEEDBACK Pin During  $-V_E$  Input.

The actual voltage levels these thresholds equate to on the primary are controlled by the primary / bias turns ratio and the value of  $R_{FB1}$ , i.e. For the HT brown-out voltage;

$$V_{HTLO} = R_{FB1} \times I_{FBHT(LO)} \times N_P / N_B$$

To calculate the AC input start voltage;

$$V_{INSTART} = \sqrt{2} \times R_{FB1} \times I_{FBHT(START)} \times N_P / N_B$$

 


Figure 42. Feedback Winding Reference Points as Voltages.

 


Figure 43. Slope Detection of Knee Point.

### FEEDBACK Pin, Measuring the Output Voltage

To obtain an accurate measure of the output voltage, the feedback waveform is sampled at the end of the secondary discharge period, Figure 42, when the secondary current has fallen to near zero. This avoids inaccuracies due to resistive volt drops associated with the resistances of the output diode, secondary wire, tracking and output capacitor ESR.

A slope detector is used to detect this point, the 'knee point'; the feedback waveform is sampled whenever the  $dv/dt$  of the input signal is equal to the slope detector value.

A sample is taken each time the slope detector triggers, even on the leakage inductance ringing, each sample overwriting the preceding sample. The last sample taken before the feedback waveform passes through 0 V (FEEDBACK pin voltage to current transition) is the value used in determining the output voltage at that time.

To ensure the correct zero crossing point is used, there is a blanking time,  $t_{FBBL}$  to mask off the leakage inductance ringing, where a ring may pass through zero and cause a false final sample detection. Under no-load conditions, it is essential that the secondary discharge time exceeds  $t_{FBBL}$  so that the true zero crossing point is not blanked, Figure 43. The design software checks for this.

Different values of  $t_{FBBL}$  are set depending on the level of  $V_{CS(MIN)}$  chosen and whether significantly in constant current mode or not.

 


Figure 44. FEEDBACK Pin Blanking Time  $t_{FBBL}$ .

The output voltage is determined by the formula;

$$V_{OUTCV} = V_{FB(REG)} \times \frac{R_{FB1} + R_{FB2}}{R_{FB2}} \times \frac{N_S}{N_B}$$

As  $R_{FB1}$  is used to set the brown-out and start-up voltages,  $R_{FB2}$  is used to set the output voltage.

The voltage control loop aims to maintain the sampled value at  $V_{FB(REG)}$ , about 1.98 V, see data sheet.

$$R_{FB2} = \frac{R_{FB1} \times V_{FB(REG)}}{V_{OUT(CV)} \times \frac{N_B}{N_S} - V_{FB(REG)}}$$

Small changes can be made to  $R_{FB1}$  to fine tune the output voltage.

If no signal is present on the FEEDBACK pin i.e. open circuit  $R_{FB1}$  or short-circuit  $R_{FB2}$  or open circuit tracking, switching will cease and the circuit will continuously run the start-up cycle (hiccup) due to the lack of signal.

### Quasi-Resonant Switching

The primary switch is only turned on when the voltage across it rings down to a minimum (voltage-valley, quasi-resonant switching). This reduces EMI and switch turn-on loss. Again, a slope detector is used to sense the idle ring valleys in the FEEDBACK pin signal. If the idle ring has decayed and is undetectable, the next switching cycle will start without waiting for a valley detection.

### Cable Compensation

Cable compensation is fixed per variant. The controller alters the voltage control signal produced during the comparison of  $V_{FB}$  and  $V_{FB(REG)}$ , thus making the necessary adjustment to compensate for the output voltage drop across the cable. The set value of cable compensation is accurate at the top right of the VI output curve i.e. the CC current setting, not necessarily the label current rating, which is usually lower.

### VOLTAGE SUPPLY Pin

The VCC pin supplies power to the internal circuitry. There is an ultra low power series regulator supplying logic and analogue circuitry. Constant current sources that drive the BJT are sourced directly from the VCC pin. Being an ultra low power regulator results in it being not very fast, so it is important that the VCC pin is very closely decoupled to the GROUND pin via  $C_{VCC}$ .

The VCC pin has several thresholds that prompt specific actions from the controller.

1.  $V_{VCC(SLEEP)}$ : If  $V_{CC}$  is below  $V_{VCC(SLEEP)}$  the controller will stop switching and enter sleep mode and the current drawn through the VOLTAGE SUPPLY pin falls to a few  $\mu A$  ( $I_{VCC(SLEEP)}$ ).
2.  $V_{VCC(RUN)}$ : If in sleep mode and  $V_{CC}$  rises to  $V_{VCC(RUN)}$ , the controller initializes and the VOLTAGE SUPPLY pin current increases to  $I_{VCC(RUN)}$  and a probe pulse is issued (see Start-up sequence section and Step 15, First time start-up).
3.  $V_{VCC(LOW)}$ : If the controller is in Run mode and the  $V_{CC}$  voltage falls to  $V_{VCC(LOW)}$ , an extra switching pulse is issued immediately as long as it does not overlap a pulse already issued. This function is useful when there is a high load to no-load transient. The output voltage will overshoot a little and will cause a frequency lower than the design no-load frequency to be set. The period of this frequency may be so long that the  $V_{CC}$  voltage falls lower than it would during a stable no-load situation. To prevent the  $V_{CC}$  voltage falling to  $V_{VCC(SLEEP)}$  and causing a shutdown and power cycle sequence, an extra no-load type pulse is issued which adds charge to  $C_{VCC}$  and prevents a shutdown. The side effect is that it will take a little longer to recover from the output voltage overshoot, but at least the switching operation is continuous and a power cycle glitch is avoided.
4.  $\Delta V_{VCC(PFM)}$ : During no-load operation, this is the difference between the peak and minimum  $V_{CC}$  voltage due to the charging and discharging of  $C_{VCC}$  during a switching cycle. During no-load operation, at least a 50 mV rise must be detected in the  $C_{VCC}$  voltage to proceed to the next stage of the switching cycle,

otherwise switching will cease,  $V_{CC}$  will fall and a power cycle sequence will occur. If  $V_{CC}$  falls by 1.6 V, an extra switching pulse is issued as if  $V_{CC}$  had fallen to  $V_{VCC(LOW)}$ , even if  $V_{CC}$  is higher than  $V_{VCC(LOW)}$ .

### CURRENT SENSE Pin

The CURRENT SENSE pin serves two functions;

1. During Initialize mode, during start-up, the value of  $R_{CS2}$  is measured by sourcing a constant current from the CURRENT SENSE pin and measuring the resulting voltage with a 2 bit ADC. This results in one of four possible values being detected, which sets the chosen level of  $V_{CS(MIN)}$  in an internal register. See data sheet for available values of resistor and corresponding levels of  $V_{CS(MIN)}$ .
2. The CURRENT SENSE pin measures the  $-V_E$  voltage across the CS resistor  $R_{CS}$ , which is due to the volt drop across  $R_{CS}$  caused by the primary current.

This voltage is scaled internally and compared to the control voltage and the over-current protection threshold ( $V_{CS(OC)}$ ) to determine when the switching BJT should be turned off. Note that if the over-current sense threshold is reached, there is a small delay ( $t_{CS(OFF)}$ ) before the BJT is turned off due to internal propagation delay. This results in the observed OCP level being higher than the expected value and it is dependant upon the HT voltage at that time. Conversely, when the voltage across  $R_{CS}$  is governed by the control voltage, the observed  $R_{CS}$  voltage is exactly as expected because the delays are compensated by the control feedback loop. In normal regulation the maximum value of voltage across  $R_{CS}$  is limited to  $V_{CS(MAX)}$ . This acts as a maximum power limit during transients or running at low HT voltage. Note that the transient power limit will usually be higher than the  $V_{OUT} \times I_{CC}$  steady state circuit power limit.

There is a CURRENT SENSE pin leading edge blanking time of  $t_{CS(B)}$ , so charging of stray capacitance does not cause a false triggering of BJT turn off.

If  $R_{CS}$  resistor is open circuit then the primary current will flow through the internal ESD protection diode between the GROUND pin and the CURRENT SENSE pin, the voltage on the CURRENT SENSE pin will very quickly reach the OCP or control voltage governed levels and the switching BJT will be turned off. This will result in very little energy in the primary, so at no-load, the output voltage may be correct, but when a load is applied, the output voltage will fall.

If the  $R_{CS}$  resistor is short-circuited or the connection to the CURRENT SENSE pin is open circuit at start-up, the controller will not start. It will issue the probe pulse and immediately go to SLEEP mode. It will then attempt to re-start. It will hiccup. If there is no-load on the output, the output capacitor will charge to a level dependent on the value of bleed (dummy load) resistor and the hiccup rate. Because the controller doesn't wake up properly, the output overvoltage protection will not be active.

The controller is able to detect if  $R_{CS}$  is shorted or connection open circuit during normal running. This is done by detecting switching BJT desaturation on the FEEDBACK pin signal. If the condition persists for a predetermined period, then the controller goes to SLEEP mode. If the output voltage reaches the output overvoltage threshold before the predetermined period expires, then the controller goes to SLEEP mode.

It is difficult to predict the output voltage with  $R_{CS}$  shorted so it must be measured at no-load and maximum input voltage.

### Constant Current Control by the CURRENT SENSE Pin Average Voltage

The controller evaluates the average voltage across  $R_{CS}$ . This is used to control the maximum output current of the circuit. A current control loop aims to limit the average voltage to  $V_{CS(CC)}$ . Before this limit, the voltage control loop is dominant, but at and beyond the limit, the current control loop is dominant.

$$Average\_primary\_current = \frac{V_{CS(CC)}}{R_{CS}}$$

So by transformer primary to secondary turns ratio;

$$I_{OUT(CC)} = \frac{N_P}{N_S} \frac{V_{CS(CC)}}{R_{CS}}$$

However, the  $V_{CC}$  supply and primary clamp take energy out of the transformer so an actual circuit will be a little lower than this calculated value. It can be trimmed by  $R_{CS}$  and once a design is fixed, this error remains fairly constant through production. So once trimmed for a design, the maximum output current will remain consistent across production.

### EMITTER DRIVE Pin

Internally, the EMITTER DRIVE pin is connected to a pull down MOSFET. This connects the switching BJT emitter to GND during the 'Charge' period of the switching cycle. This MOSFET must be capable of conducting the peak primary current without incurring significant power loss. There is also a pair of ESD protection diodes, one from GROUND Pin to the EMITTER DRIVE pin and a second from the EMITTER DRIVE pin to the VOLTAGE SUPPLY pin. This second diode is used during the start-up cycle to charge the capacitor  $C_{VCC}$  by passing the BJT's emitter bootstrap current from the EMITTER DRIVE to VOLTAGE SUPPLY pins.

The switching of this pin is synchronized with the BASE DRIVE pin to enable rapid and safe, controlled switching of the BJT, see Figures 45 and Figure 46.

### BASE DRIVE Pin

The BASE DRIVE pin supplies current through the switching BJT base to turn it on quickly, but provide only just enough charge to keep the BJT saturated whilst allowing it to be rapidly turned off. Like the EMITTER DRIVE pin there is a pull down MOSFET, but this is used to turn the BJT off. This too must be capable of conducting the peak primary current as the primary current is passed through the BJT base when the EMITTER DRIVE pin MOSFET is turned off. This speeds up the turn off of the BJT.

There are four stages in the base drive cycle, see Figure 45 and Figure 46;

1. A high initial level of base current for a short duration, the 'Force On Pulse', amplitude  $I_{F(ON)}$ , duration  $t_{F(ON)}$ .
2. A controlled level and duration of base drive based on the output power demand. The level is proportional to the control voltage and the duration is controlled by a feedback loop that aims to keep the time between pulling the base low and the collector rising by approximately 30 V to around 100 ns. Additional current may be supplied by the SBD resistor via the SUPPLEMENTARY BASE DRIVE pin, at this time for higher power designs using SO-8 packaged devices.
3. A period where the BASE DRIVE pin is high impedance and the BJT consumes the charge stored in the base region in order to conduct the primary current.
4. BASE DRIVE pin is pulled low to turn the BJT off. The EMITTER DRIVE pin simultaneously goes high impedance.

 


Figure 45. Simplified Base Drive Circuit.

 


Figure 46. BJT Switching Cycle Waveforms.

This scheme allows for a wide range of BJT HFE characteristics to be driven efficiently with minimum power loss. As the drive is essentially 'common base', the full RBSOA of the BJT can be used i.e.  $V_{CBO}$  rating is dominant, not  $V_{CEO}$ .

- (t1 – t2) Force ON pulse ("fon").
- (t2 – t3) Variable adaptive base drive.
- (t3 – t4) BJT storage time.
- (t4) BASE DRIVE pin pulled to GND, emitter released.
- (t4 – t5) VCE rise time, BJT turning OFF.

### SUPPLEMENTARY BASE DRIVE Pin

LinkSwitch-4 parts in a SO-8 package have a SUPPLEMENTARY BASE DRIVE pin. A resistor connects the SUPPLEMENTARY BASE DRIVE pin to the VCC supply. During the time period t2 to t3 in Figure 46, the SUPPLEMENTARY BASE DRIVE pin is connected to the BASE DRIVE pin, increasing the base drive current in higher power designs. The advantage of this approach is that the power dissipated by the SBD resistor is external to the SO-8 package hence the package thermal budget can be concentrated on the internal ED switch.

### Start-Up Sequence

To provide rapid start-up with low power consumption and no extra components, the gain of the BJT is used to minimize the power dissipation of the bootstrap resistor  $R_{HT}$ . See Figure 47.

 


Figure 47. Start-Up Circuit.

Start-up circuit operation.

1.  $I_{RHT} = V_{HT} / R_{HT}$
2.  $I_B = I_{RHT} - I_{BD(SLEEP)}$ . This current is amplified by the HFE of the BJT to become  $I_E$ .
3.  $I_E$  flows into the EMITTER DRIVE pin, through the internal ESD protection diode and out of the VOLTAGE SUPPLY pin, but minus  $I_{VCC(SLEEP)}$  to become  $I_{CVCC}$ .
4.  $I_{CVCC}$  charges  $C_{VCC}$  towards  $V_{CC(RUN)}$ .

The critical parameters that effects the duration of the initial start-up process i.e. how long it takes to reach  $V_{CC(RUN)}$ , are that of  $I_{RHT}$  and  $I_{BD(SLEEP)}$ . If  $R_{HT}$  is made too large to lower the no-load power,  $I_{RHT} - I_{BD(SLEEP)}$  can become very small and  $V_{CC}$  may never reach  $V_{CC(RUN)}$  or take 10 s.

When  $V_{CC}$  reaches  $V_{VCC(RUN)}$  a short base drive pulse is issued, during which time the voltage at FB is held at GND potential by current sourced from the FEEDBACK pin. The current depends on the

 


Figure 48. VOLTAGE SUPPLY Pin During Start-Up.

rectified mains voltage, the primary to auxiliary turns ratio, and resistor  $R_{FB1}$ . Measurement of this current enables the controller to compare the rectified mains input voltage with a threshold for allowing the next stage of start-up.

If the input voltage is too low ( $I_{FB} < I_{FBHT(START)}$ ), the controller will not issue further drive pulses, the VCC voltage will discharge to  $V_{VCC(SLEEP)}$  and the power-up sequence will repeat.

If the input voltage is high enough ( $I_{FB} > I_{FBHT(START)}$ ), the controller will enter Run mode and more drive pulses will be issued. To achieve smooth power-up (monotonic rise in  $V_{OUT}$ ),  $C_{VCC}$  must be large enough to power the IC (during Initialize mode and the first few cycles of Run mode), until sufficient power is provided by the transformer bias winding.

See **Step 15 – First time Start-up and Troubleshooting** for further details.

### Switching Frequency and Pulse Width Modulation

The controller regulates output power by modulating switching frequency and peak primary current (PWM). The  $V_{CS}$  threshold set for a given output is proportional to the control voltage. The switching frequency increases with control voltage from the minimum switching frequency, set by  $V_{CS(MIN)}$  and circuit no-load consumption, to the maximum switching frequency (65 kHz) when the control voltage is at 70% of maximum. This relationship is illustrated in Figure 49. The green line shows the relationship between the control voltage on the X-axis and the voltage across  $R_{CS}$  (or the CURRENT SENSE pin –  $V_{CS}$ ) at which the BJT will be turned off on the right hand side Y-axis. The blue line shows the relationship between the Control Voltage and the switching frequency on the left hand side Y-axis.  $V_{CTRL(FL)}$  is the control voltage at the top right corner of the VI curve, the maximum power point and translates to a CURRENT SENSE pin voltage of  $V_{CS(MAXACT)}$  and a switching frequency of  $F_{MAX}$ . It is usual to calculate the design so that  $V_{CS(MAXACT)}$  is at 85% of  $V_{CS(MAX)}$ . This puts the operating frequency in the middle of the plateau at  $F_{MAX}$  so that tolerances in inductance and other components will not cause maximum load switching at less than  $F_{MAX}$ . Also there will be sufficient margin between  $V_{CTRL(FL)} / V_{CS(MAXACT)}$  and  $V_{CTRL(MAX)} / V_{CS(MAX)}$  to allow good transient response. Ensuring operation at  $F_{MAX}$  at maximum load makes EMI emissions more consistent across production. However, this 'down the middle' design may not provide the maximum efficiency. Increasing the primary inductance will improve the efficiency due to the lower peak primary current and

resulting decrease in primary resistive losses. This will have the effect of moving the maximum load operating point to the left on Figure 49, to around 70-75% of  $V_{CS(MAX)}$ . In this case more testing will have to be done to verify that the operational specifications are met over the production spread of component tolerances.

PI Expert tends to aim for higher efficiency, so the  $V_{CTRL(FL)}$  operating point will tend to be to the left of 85% of  $V_{CTRL(MAX)}$ .

 


Figure 49. Relationship Between Control Voltage, Switching Frequency and  $V_{CS}$  Threshold.

### EasyStart Feature

Some adapter designs, particularly those for networking equipment, are required to operate with a large additional capacitance, around 3000  $\mu F$ , connected to the output. This is compounded by the fact that these adapters are usually 12 V output making start-up very challenging. For a standard design where the maximum current (CC current) is the label output current plus 7%, the time taken to charge the capacitance up to the label voltage at the label load current would take a long time. This would require a large  $C_{VCC}$  of some 10s of  $\mu F$  to power the IC until the bias wind has enough voltage to recharge  $C_{VCC}$ . Another option is to have the maximum current much higher than the rated load current, but this would be an expensive solution as the transformer, at least, would have to be oversized to operate at the higher current.

The LNK4x14D and LNK4x15D have the EasyStart feature enabled, so a normal value of  $C_{VCC}$  can be used, whilst allowing start-up into a high value of output capacitance. The size of the output capacitor that can be charged at start-up is only limited by the time allowed for this to be achieved.

The EasyStart feature modifies the timing of the BD and ED switching cycle so that when in period  $t_3$  to  $t_4$  (BJT storage time) in Figure 46 and 50, the EMITTER DRIVE pin pull down is turned off. An additional fast, low voltage diode is connected from the BJT emitter to  $C_{VCC}$ , see Figure 51, so that when the emitter rises to the  $C_{VCC}$  voltage level the emitter current flows into  $C_{VCC}$  charging it up. EasyStart only activates when  $V_{CC}$  is below 6 V, so once the bias winding starts powering  $V_{CC}$  and maintaining it above the usual design level of 8 V+, the EasyStart feature will not activate again and has no effect on performance i.e. efficiency and no-load power.

The extra diode only needs to be low voltage, 20 V+, and must support the peak primary current over the duty cycle at the lowest AC input voltage. ESD1 or UF4001 types would be suitable.

To enhance the operation of EasyStart the time period  $t_3 - t_4$  of Figure 49 should be maximized, so  $R_{SBD}$  should be reduced to 100  $\Omega$  to 150  $\Omega$ . This will speed up the charge entering the base region and reduce  $t_2 - t_3$  time period and extend  $t_3 - t_4$ .

A limitation of the technique is that it loses effectiveness at high-line voltages on universal input designs. The time period  $t_1 - t_3$  remains fairly constant during start-up, but the overall period  $t_1 - t_5$  reduces with increasing HT voltage, which reduces the  $C_{VCC}$  recharge time  $t_3 - t_4$ . It usually remains effective at 240 VAC, but gets marginal at 264 VAC. Monitoring the EMITTER DRIVE and VOLTAGE SUPPLY pins will give a measure of the effectiveness of EasyStart at higher input voltages.

Where difficulties are experienced, reduce  $R_{SBD}$  to 100  $\Omega$  or increase the primary inductance and the minimum input voltage.

 


Figure 50. Modified Base Drive and Emitter Drive Timing for EasyStart Feature.

 


Figure 51. Schematic with Extra Diode for EasyStart Feature.

### Thermal Shut Down

The LinkSwitch-4 has a thermal shut down feature. If the junction temperature of the IC exceeds  $T_{SD}$ , about 140 °C, the chip will shut down and cease switching. Once the temperature has fallen by  $T_{SD(H)}$ , the chip will restart, perform a normal start-up cycle and continue.

### Constant Power (CP) option

In addition to EasyStart, LNK4214D and LNK4215D devices have a constant power section to the VI curve, see Figure 52. This feature is intended to further improve start-up into large capacitive loads (5000  $\mu$ F at 12 V). At start-up, the constant current (CC) pull-up set point of the VI characteristic (bottom right of Figure 52) is set by the transformer turns ratio, the value of  $R_{CS}$  and the value of the device parameter  $V_{CC(SC)}$ . The value of  $V_{CC(SC)}$  is about 75% higher on LNK4214D and LNK4215D compared to LNK4014D and LNK4115D, so for a given transformer and  $R_{CS}$  value the CC level,  $I_{OUT(EXT)}$ , will be about 75% higher than the standard CV/CC VI curve parts, providing an extra 75% of start-up current into the output capacitance and aiding a successful rapid start-up. As the output voltage rises, the controller regulates in CC mode until it is above approximately 50% of the design CV level. It then operates in a power limited (CP) mode until the voltage reaches the design CV set point, at which point it changes to CV mode regulation.  $I_{OUT}$  at this point,  $I_{OUT(CP)}$ , will be greater than 57% of  $I_{OUT(EXT)}$ . The exact trajectory is somewhat dependent on the HT level (mains input level). This is due to the controller operating in open loop mode over the CP section of the VI curve i.e. feedback is not effective during this section, so inaccuracies due to efficiency variation over the CP section and mains input level are not corrected. Hence there is no single CP curve for a design, but minimum and maximum curves between which the actual curve will lie, see  $I_{OUT(CP)}$  for Low Mains and High Mains in Figure 52. The constant power value is set by the full load switching frequency parameter  $F_{SW}$ , the primary inductance, the peak primary current – set by the device parameter  $V_{CS(MAX)}$  divided by the value of  $R_{CS}$ , and the conversion efficiency. Due to the open-loop mode of operation on the CP section, tolerances in primary inductance, switching frequency,  $R_{CS}$ ,  $V_{CS(MAX)}$  and  $V_{CSCC}$  play a significant part in the accuracy of the CP section of the VI curve. This must be factored in when undertaking the design of a CP application.

 


Figure 52. Typical LNK4214D and LNK4215D CP Output Characteristic.

Primary inductance tolerance should be  $\pm 5\%$  or better,  $F_{SW}$  has a tolerance of  $\pm 7\%$ ,  $V_{CSCC}$   $\pm 2\%$ ,  $V_{CS(MAX)}$   $\pm 5.5\%$  and  $R_{CS}$  should be  $\pm 1\%$  or better.

The first step is to use the LinkSwitch-4 PIXIs tool to design the transformer and component values for a CV/CC equivalent to the CV/CP circuit. The important consideration is to have the CV/CP circuit be able to provide at least the specification label output current at the label output voltage to the load i.e.  $I_{OUTCP(MIN)}$  in Figure 52 must be equal or greater than the label current across component tolerances. Worst-case, this means that 15.5% must be allowed for. In practice, 10% should be acceptable mainly due to parameter tolerance safety margins in the chip and the statistics of getting the worst case values on the same board.

Enter a value of the label output current plus 10% into [B10], otherwise follow the CV/CC design procedure described above. This will produce a transformer and component set that will run efficiently up to the label current and if a standard CV/CC LinkSwitch-4 were to be used, the CV to CC transition point would be at the correct level.

The LNK4214D and LNK4215D have a modified value for  $V_{CSCC}$ . It is higher so that the circuit will reach the power limited CP condition before the CC condition and provide the VI curve given in Figure 52. What is required is a new value for  $R_{CS}$  to allow  $V_{CS(MAX)}$  to be reached when the output is delivering the current entered in [B10],  $I_{CC}$  at  $V_O$ . This can be calculated from the formula:

$$R_{CS} = \sqrt{\frac{L_P \times V_{CSMAX}^2 \times F_{SW} \times Eff_{OUT}}{2 \times I_{CC} \times V_O (1 + G_{CAB})}}$$

The maximum output current  $I_{OUTEXT}$  can be calculated from:

$$I_{OUTEXT} = N \times \frac{V_{CSCC}}{R_{CS}}$$

Where:

- $L_P$  = Nominal primary inductance in Henries.
- $V_{CS(MAX)}$  =  $V_{CS(MAX)}$  for LinkSwitch-4 device in volts, nominally 0.36 V.
- $F_{SW}$  = Maximum switching frequency of LinkSwitch-4 in Hz, nominally 65000 Hz.
- $Eff_{OUT}$  = Estimate of conversion efficiency from primary to secondary output. Default to 0.9 if no other figure is available via measurement.
- $I_{CC}$  = Label rated output current plus margin, normally +10%.
- $V_O$  = Label output voltage.
- $G_{CAB}$  = Design cable compensation at  $I_{CC}$ , i.e. 0.03 for 3%.
- $N$  = Transformer primary to secondary turns ratio.
- $V_{CSCC}$  = Constant current control reference level for the appropriate LinkSwitch-4 device in volts.

Due to the estimation of  $Eff_{OUT}$ , the resulting value of  $R_{CS}$  calculated may have to be trimmed to obtain the correct positioning of the CV to CP corner point.

It is prudent to check the resulting VI curves with transformers gapped for the maximum and minimum primary inductance to ensure the desired  $I_O$  is met.

Check the rating of the output diode, the output current can now be 75% higher than a CV/CC design, though it may only be during start-up, depending on usage.

The CP parts also have the EasyStart function, so the EasyStart diode must be used or the LinkSwitch-4 will be damaged.

	Device	Min	Typ	Max	Units
Primary Current Sense Threshold for CC Operation $V_{CSCC}$	Except LNK4115D, LNK4214D, LNK4215D	-62	-60.8	-59.6	mV
	LNK4115D only		-68		
	LNK4214D only		-105		
	LNK4215D only		-119		

---

Notes

Revision	Notes	Date
A	Initial Release.	01/17
B	Updated Figure 34.	10/17

**For the latest updates, visit our website: [www.power.com](http://www.power.com)**

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS.

**Patent Information**

The products and applications illustrated herein (including transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents, or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations patents may be found at [www.power.com](http://www.power.com). Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.power.com/ip.htm>.

**Life Support Policy**

POWER INTEGRATIONS PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF POWER INTEGRATIONS. As used herein:

1. A Life support device or system is one which, (i) is intended for surgical implant into the body, or (ii) supports or sustains life, and (iii) whose failure to perform, when properly used in accordance with instructions for use, can be reasonably expected to result in significant injury or death to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

The PI logo, TOPSwitch, TinySwitch, SENZero, SCALE-iDriver, Qspeed, PeakSwitch, LYTSwitch, LinkZero, LinkSwitch, InnoSwitch, HiperTFS, HiperPFS, HiperLCS, DPA-Switch, CAPZero, Clampless, EcoSmart, E-Shield, Filterfuse, FluxLink, StakFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2017, Power Integrations, Inc.

**Power Integrations Worldwide Sales Support Locations**

**World Headquarters**

5245 Hellyer Avenue  
San Jose, CA 95138, USA  
Main: +1-408-414-9200  
Customer Service:  
Phone: +1-408-414-9665  
Fax: +1-408-414-9765  
e-mail: [usasales@power.com](mailto:usasales@power.com)

**China (Shanghai)**

Rm 2410, Charity Plaza, No. 88  
North Caoxi Road  
Shanghai, PRC 200030  
Phone: +86-21-6354-6323  
Fax: +86-21-6354-6325  
e-mail: [chinasales@power.com](mailto:chinasales@power.com)

**China (Shenzhen)**

17/F, Hivac Building, No. 2, Keji Nan  
8th Road, Nanshan District,  
Shenzhen, China, 518057  
Phone: +86-755-8672-8689  
Fax: +86-755-8672-8690  
e-mail: [chinasales@power.com](mailto:chinasales@power.com)

**Germany**

Lindwurmstrasse 114  
80337 Munich  
Germany  
Phone: +49-895-527-39110  
Fax: +49-895-527-39200  
e-mail: [eurosales@power.com](mailto:eurosales@power.com)

**Germany**

HellwegForum 1  
59469 Ense  
Germany  
Tel: +49-2938-64-39990  
e-mail: [igbt-driver.sales@power.com](mailto:igbt-driver.sales@power.com)

**India**

#1, 14th Main Road  
Vasanthanagar  
Bangalore-560052 India  
Phone: +91-80-4113-8020  
Fax: +91-80-4113-8023  
e-mail: [indiasales@power.com](mailto:indiasales@power.com)

**Italy**

Via Milanese 20, 3rd. Fl.  
20099 Sesto San Giovanni (MI) Italy  
Phone: +39-024-550-8701  
Fax: +39-028-928-6009  
e-mail: [eurosales@power.com](mailto:eurosales@power.com)

**Japan**

Yusen Shin-Yokohama 1-chome Bldg.  
1-7-9,, Shin-Yokohama, Kohoku-ku  
Yokohama-shi, Kanagawa  
222-0033 Japan  
Phone: +81-45-471-1021  
Fax: +81-45-471-3717  
e-mail: [japansales@power.com](mailto:japansales@power.com)

**Korea**

RM 602, 6FL  
Korea City Air Terminal B/D, 159-6  
Samsung-Dong, Kangnam-Gu,  
Seoul, 135-728, Korea  
Phone: +82-2-2016-6610  
Fax: +82-2-2016-6630  
e-mail: [koreasales@power.com](mailto:koreasales@power.com)

**Singapore**

51 Newton Road  
#19-01/05 Goldhill Plaza  
Singapore, 308900  
Phone: +65-6358-2160  
Fax: +65-6358-2015  
e-mail: [singaporesales@power.com](mailto:singaporesales@power.com)

**Taiwan**

5F, No. 318, Nei Hu Rd., Sec. 1  
Nei Hu Dist.  
Taipei 11493, Taiwan R.O.C.  
Phone: +886-2-2659-4570  
Fax: +886-2-2659-4550  
e-mail: [taiwansales@power.com](mailto:taiwansales@power.com)

**UK**

Building 5, Suite 21  
The Westbrook Centre  
Milton Road  
Cambridge  
CB4 1YG  
Phone: +44 (0) 7823-557484  
e-mail: [eurosales@power.com](mailto:eurosales@power.com)