

DI-29 Design Idea

DPA-Switch®

25 W Flyback DC-DC Converter

Application	Device	Power Output	Input Voltage	Output Voltage	Topology
DC-DC Converter	DPA425RN	25 W	36 – 75 VAC	7 V	Flyback

Design Highlights

- Extremely low component count
- High efficiency – 85% using Schottky rectifiers
- No current sense resistor or transformer required
- Accurate input under/over voltage meets ETSI standards
- Operates to zero load with no pre-load required
- Output overload, open loop and thermally protected
- 400 kHz operation minimizes size of magnetics

Operation

DPA-Switch greatly simplifies the design compared to a discrete implementation. Resistor R1 programs the input under/over voltages to 33 V and 86 V, respectively. Including tolerances these thresholds guarantee the converter is operational between 36 V and 75 V, without the cost of additional line sense components.

Resistor R3 programs the internal current limit of the DPA425R to 50% of nominal. The larger DPA-Switch selection reduces conduction losses, raising efficiency without circuit changes or increased overload power.

Zener VR1 clamps leakage inductance spikes, keeping the DRAIN voltage below BV_{DSS} . The bias supply for U1 is provided from an auxiliary flyback transformer winding.

On the secondary, a snubber across D2 (C9, R5 and R13) limits the secondary leakage inductance spikes generated by diode reverse recovery. Inductor L2, C13 and C14 form a post-filter to reduce high frequency output switching ripple. A soft-finish network, C18, D3 and R7, eliminates output turn-on overshoot. The remaining components provide output voltage regulation and loop compensation.

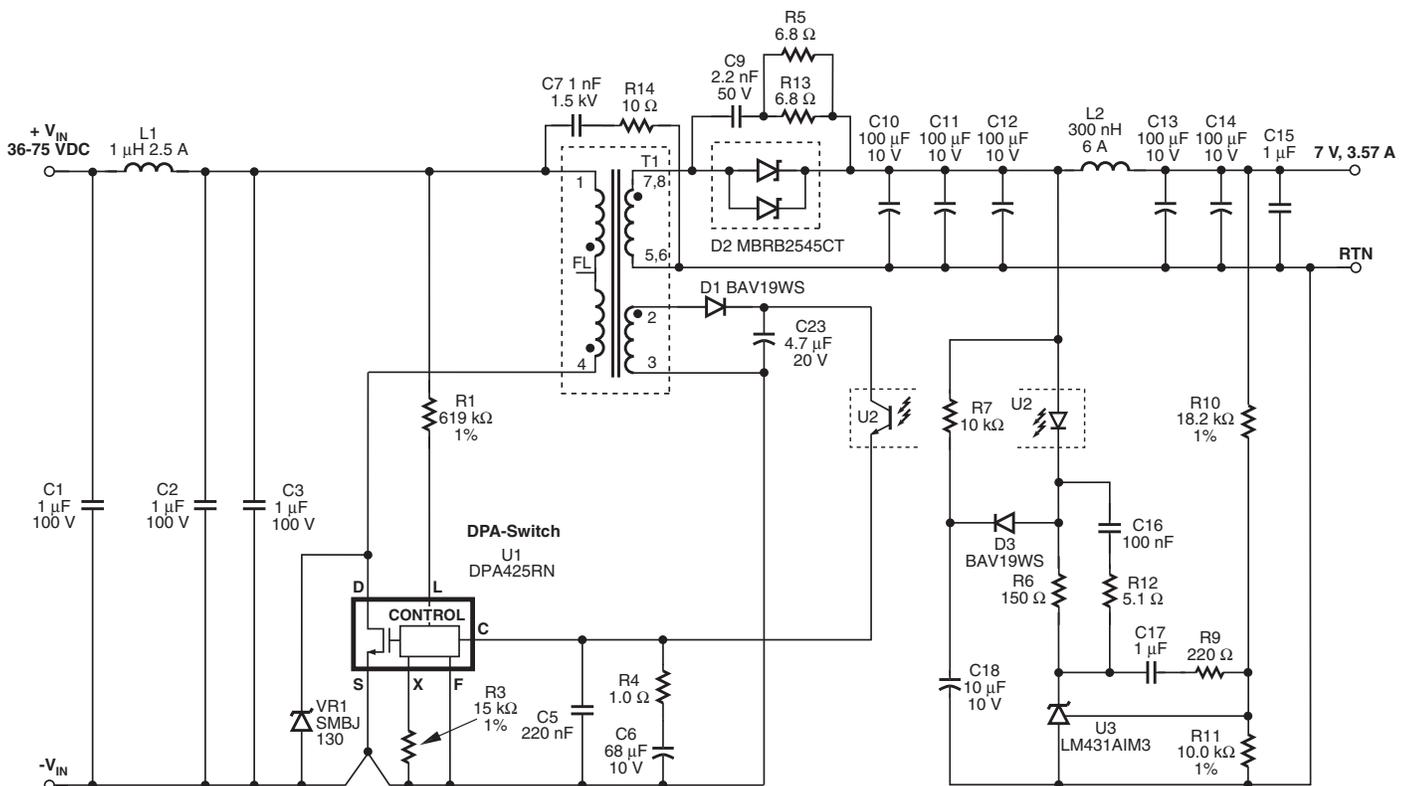


Figure 1. DPA-Switch Flyback DC-DC Converter Schematic.

PI-3012-011608

Key Design Points

- For nominal under-voltage set point V_{UV} :
 $R1 = (V_{UV} - 2.35 \text{ V}) / 50 \mu\text{A}$. $V_{OV} = (R1 \times 135 \mu\text{A}) + 2.5 \text{ V}$.
- Zener VR1 voltage is 130 V to safely limit the DRAIN voltage below V_{DSS} of 200 V.
- Opto U2 should have a CTR of between 100% and 200% for optimum loop stability.
- Set resonance of L2 and C13 + C14 to beyond loop crossover frequency (typically 5% to 10% of switching frequency).
- Good layout practices should be followed:
 - Locate C5, C6 and R4 close to U1, with grounds returned to the SOURCE pin.
 - Primary return should be connected to the DPA-Switch tab, not the SOURCE pin.
 - Minimize the primary and secondary loop areas to reduce parasitic leakage inductance.

Transformer Parameters

Core Material	PR1408 Siemens N87, gapped for 340 nH/t ²
Bobbin	P1408 8 pin (B&B B-096 or equivalent)
Winding Details	Primary: 6T + 6T, 2 × 27 AWG Secondary: 3T, 4 × 25 AWG Bias: 6T, 32 AWG
Winding Order (pin numbers)	Primary (4-FL), tape, Bias (2-3), tape, Secondary (5,6-7,8), tape, Primary (FL- 1), tape
Inductance	Primary: 49 μH, ±10% Leakage: 1 μH (maximum)
Primary Resonant Frequency	3.8 kHz (minimum)

Table 1. Transformer Parameters. (AWG = American Wire Gauge)

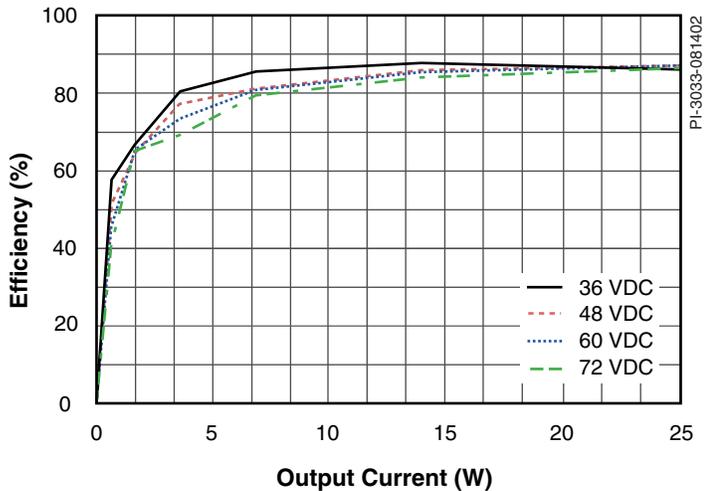


Figure 2. Efficiency vs. Output Power.

Power Integrations
 5245 Hellyer Avenue
 San Jose, CA 95138, USA.
 Main: +1 408-414-9200
 Customer Service
 Phone: +1-408-414-9665
 Fax: +1-408-414-9765
 Email: usasales@powerint.com

On the Web
www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS. The products and applications illustrated herein (transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com. Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.powerint.com/ip.htm>.

The PI logo, TOPSwitch, TinySwitch, LinkSwitch, DPA-Switch, PeakSwitch, EcoSmart, Clampless, E-Shield, Filterfuse, StackFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2002, Power Integrations, Inc.