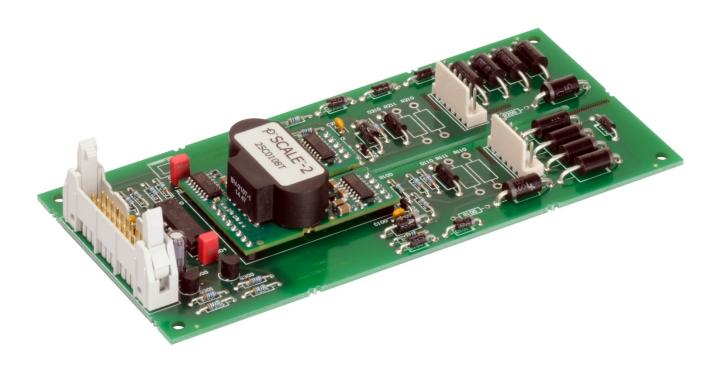


General Purpose THT Base Board for Gate Driver Core 2SC0108T

Application	General purpose drives, UPS, solar power and others	
Suitable for IGBT power modules in various house Up to 1200V DC-link voltage Specification Electrical interfaces Basic Active Clamping Short-circuit detection with Soft Shut Down (SSE		
Author	High-Power Application Engineering Department	
Document Number	RDHP-1531	
Revision ¹	A.3	



-

¹ The letter refers to the hardware revision. The number refers to the documentation revision.



Scope

This application proposal provides a circuit design for a general purpose base board for driving various IGBT power modules.

The main features of the design are:

- Suitable for IGBT power modules in various housings such as 17mm dual, 17mm six-pack, 62mm, PrimePACK™, etc. with a maximum blocking voltage of 1700V
- (Optional) Basic Active Clamping
- Short-circuit detection with Soft Shut Down (SSD)
- Electrical command inputs and status outputs
- 0V/15V command input logic
- 0V/15V status output logic
- Minimum pulse suppression
- Direct or Half-Bridge mode selection
- Adjustable blocking time
- 15V supply voltage
- Single PCB solution with soldered-in gate driver core

Intellectual Property Licensing

The design proposal, products and applications illustrated herein (including transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents, or potentially by pending U.S. and foreign patent applications assigned to Power Integrations.

A complete list of Power Integrations patents may be found at https://www.power.com/.

Power Integrations grants its customers a license under certain patent rights as set forth at https://www.power.com/company/intellectual-property-licensing/.

Application Conditions

The design is proposed for the following application conditions:

- General purpose applications and IGBT power modules
- Adaptations such as adjustment of gate resistors can easily be done



Design Description

In addition to the following design description, reference to the datasheet(s) and application manual of the 2SC0106T gate driver family is recommended.

Gate Resistors

Gate resistor values are not explicitly given as they depend on the IGBT power module used and on the application. THT (size PR02) gate resistors can be selected.

Turn-on gate resistors:

Channel	THT Package
1	R111
2	R211

Turn-off gate resistors:

Channel	THT Package
1	R110
2	R210

The gate resistors must be determined and assembled by the user. Minimum required gate resistor values are defined in the datasheet of the gate driver 2SC0106T.

V_{CEsat} Monitoring

2SC0106T gate drivers from Power Integrations provide sense inputs for monitoring IGBT short-circuit conditions. The details of the V_{CEsat} monitoring function are described in the corresponding application manual of the gate driver.

Soft Shut Down (SSD)

The gate driver cores 2SC0106T with SCALE-2+ chip set feature an SSD function, which reduces the turn-off $^{di}/_{dt}$ to limit V_{CE} overvoltage spikes as soon as a short-circuit condition is detected. An excessive turn-off overvoltage is therefore avoided and the IGBT is turned off within its safe operating area.

The SSD function is only active under short-circuit conditions, but not under normal operating conditions (e.g. at nominal current or in over-current conditions), i.e. it is triggered by the V_{CESat} monitoring function.

The SSD function may also have performance limitations, such as at high DC-link voltages and/or high commutation loop stray inductances. If the application is operated at these boundary conditions, it is recommended to implement Basic Active Clamping.

For further details concerning the SSD function refer to the application manual of the gate driver core 2SC0106T.



Basic Active Clamping

Active clamping is a technique designed to partially turn on the IGBT in case the collector-emitter voltage exceeds a predefined threshold. The IGBT is then kept in linear operation. Basic Active Clamping topologies implement a single feedback path from the IGBT's collector through transient voltage suppressor (TVS) diodes to the IGBT gate.

In the schematic and bill of material the TVS networks (D106 to D109 and D206 to D209) are marked with "N.A." (not assembled) as their specific value depends on the IGBT power module and applied DC-link voltage. Recommended values are listed in the following tables.

IGBT	Max. DC-	D105,	D106 D108,	D109,
voltage	link	D205	D206 D208	D209
	voltage			
1200V	800V	SB340	1.5KE220A-E3	1.5KE250CA-E3
1700V	1200V	SB340	1.5KE350A-E3	1.5KE300CA-E3

For further details refer to the application manual of the gate driver core 2SC0106T.

Minimum Pulse Suppression

This design possesses a minimum pulse suppression with a time constant τ of typically 470ns. If required the setting can be changed by adjusting C302 and C303. The time constant τ is given by the following equations:

$$\tau_1 = 4.7k\Omega \cdot C302$$

$$\tau_2 = 4.7 k\Omega \cdot C303$$

Recommended values of C302 and C303 are in the range of 33pF (τ_x = 155ns) to 120pF (τ_x = 564ns), depending on actual application conditions.

Blocking Time

During the blocking time the gate driver ignores incoming command signals. The blocking time starts once a fault was detected by the gate driver's secondary side (undervoltage lock-out or a short-circuit event) or when an undervoltage condition ends on the primary side.

The terminal TB allows the default blocking time of typically 99ms (R310) to be reduced by connecting an optional external resistor to GND. The external resistor R_b needs to be equal or larger than $129k\Omega$ to fulfill the following formula:

$$(R_b + 6.8k\Omega) \mid \mid 150k\Omega \triangleq T_b + 51ms$$
 with $20ms < T_b < 99ms$

In case the terminal TB is directly shorted to GND ($R_b = 0\Omega$), the blocking time is set to its minimum value as descripted in the datasheet of the gate driver core 2SC0106T.



Interfaces

Electrical Interfaces

	Х3			
Pin	Designation	Description		
1	n.c.	Not connected		
3	n.c.	Not connected		
5	VCC	15V supply (referenced to GND)		
7	VCC	15V supply (referenced to GND)		
9	SO2	Status output channel 2		
11	INB	Command input channel 2		
13	SO1	Status output channel 1		
15	INA	Command input channel 1		
17	MOD	Mode selector		
19	ТВ	Set blocking time		

Х3			
Pin	Designation	Description	
2	GND	Ground	
4	GND	Ground	
6	GND	Ground	
8	GND	Ground	
10	GND	Ground	
12	GND	Ground	
14	GND	Ground	
16	GND	Ground	
18	GND	Ground	
20	GND	Ground	





CAD Data

The set of CAD data, which includes the circuit schematics, Gerber files, BOM and Pick-and-Place file are available as separate documents bundled together with this documentation.

Layout Example

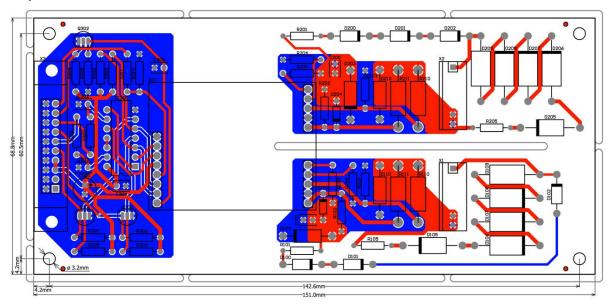An example for a suitable layout is shown in the following picture. The recommended PCB thickness is 1.55mm (for gate driver cores with terminal length of 2.54mm) and 2.0mm (for gate driver cores with terminals length ≥ 3.1 mm).



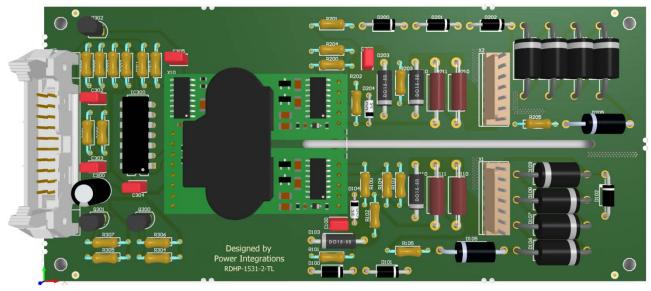




Switching Characteristic


Turn-On/Off

The following measurement examples were carried out at room temperature with the IGBT power module FF300R17KE3 from Infineon Technologies ($R_{Gon} = 4.7\Omega$ and $R_{Goff} = 4.7\Omega$) in a double-pulse test using a half-bridge topology setup with an initial DC-link voltage of $1200V_{DC}$. The adjusted load current is either 300A (I_{nom}) or 600A (I_{nom}).


Channel assignment:

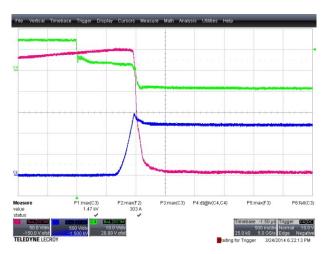


Turn-off bottom side (I_{nom})

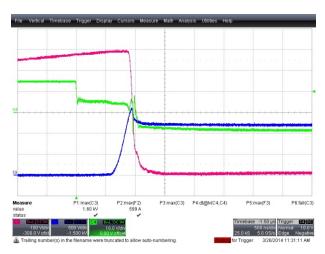

Turn-off bottom side (2x I_{nom})

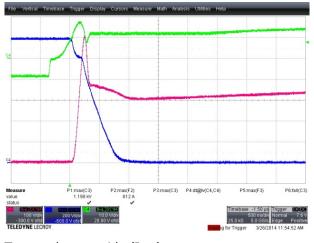

Turn-on bottom side (I_{nom})

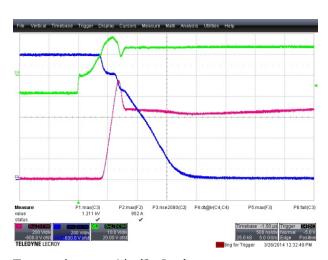

Turn-on bottom side ($2x I_{nom}$)




Short-Circuit

The following measurement example was carried out at room temperature with the IGBT power module FF300R17KE3 from Infineon Technologies ($R_{Gon} = 4.7\Omega$ and $R_{Goff} = 4.7\Omega$) with an initial DC-link voltage of $1200V_{DC}$.

Channel assignment:

Channel C1: Command input signal Channel C2: Gate-emitter voltage
Channel C3: Status output signal Channel C5: Collector current

Channel C7: Collector-emitter voltage

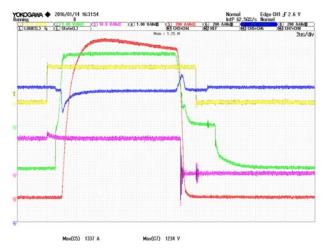

Bottom side



Handling

To avoid possible failures caused by ESD, a handling- and assembly-process with persistent ESD protection is necessary /3/.

References

- /1/ 2SC0106T2Ax-12 Data Sheet, Power Integrations
- /2/ 2SC0106T2Ax-12 Description & Application Manual, Power Integrations
- /3/ Application Note AN-0902, "Avoiding ESD with CONCEPT Drivers", Power Integrations

Technical Support

Power Integrations provides expert help with your questions and problems:

Website http://www.power.com/igbt-driver/go/support

Email igbt-driver.support@power.com

Quality

The obligation to high quality is one of the central features laid down in the mission statement of Power Integrations. Our total quality management system assures state-of-the-art processes throughout all functions of the company, certified by ISO9001:2008 standards.

Legal Disclaimer

Reference Designs are technical proposals concerning how to use Power Integrations' gate drivers in particular applications and/or with certain power modules. These proposals are "as is" and are not subject to any qualification process. The suitability, implementation and qualification are the sole responsibility of the end user.

The statements, technical information and recommendations contained herein are believed to be accurate as of the date hereof. All parameters, numbers, values and other technical data included in the technical information were calculated and determined to our best knowledge in accordance with the relevant technical norms (if any). They may base on assumptions or operational conditions that do not necessarily apply in general. We exclude any representation or warranty, express or implied, in relation to the accuracy or completeness of the statements, technical information and recommendations contained herein. No responsibility is accepted for the accuracy or sufficiency of any of the statements, technical information, recommendations or opinions communicated and any liability for any direct, indirect or consequential loss or damage suffered by any person arising therefrom is expressly disclaimed.



Power Integrations Sales Offices

WORLD HEADQUARTERS

5245 Hellyer Avenue San Jose, CA 95138 USA Tel: +1-408-414-9200 Fax: +1-408-414-9765 Email: usasales@power.com

AMERICAS WEST

5245 Hellyer Avenue San Jose, CA 95138 USA Tel: +1-408-414-8778 Fax: +1-408-414-3760 Email: usasales@power.com

GERMANY (AC-DC/LED Sales)

Lindwurmstrasse 114 80337 München, Germany Tel: +49-89-5527-39100 Fax: +49-89-1228-5374 Email: <u>eurosales@power.com</u>

INDIA (Mumbai)

Unit: 106-107, Sagar Tech Plaza-B Sakinaka, Andheri Kurla Road Mumbai, Maharashtra 400072 India Tel 1: +91-22-4003-3700

Tel 2: +91-22-4003-3600 Email: <u>indiasales@power.com</u>

JAPAN

Kosei Dai-3 Bldg. 2-12-11, Shin-Yokohama, Kohoku-ku Yokohama-shi, Kanagawa Japan 222-0033

Tel: +81-45-471-1021 Fax: +81-45-471-3717 Email: japansales@power.com

TAIWAN

5F, No. 318, Nei Hu Rd., Sec. 1

Nei Hu Dist. Taipei, 114 Taiwan Tel: +886-2-2659-4570 Fax: +886-2-2659-4550 Email: taiwansales@power.com

AMERICAS EAST

7360 McGinnis Ferry Road Suite 225 Suwannee, GA 30024 USA Tel: +1-678-957-0724 Fax: +1-678-957-0784

Email: usasales@power.com

CHINA (Shanghai)

Room 2410, Charity Plaza No. 88 North Caoxi Road Shanghai, 200030 China Tel: +86-21-6354-6323 Fax: +86-21-6354-6325 Email: chinasales@power.com

GERMANY (IGBT Driver Sales)

HellwegForum 1 59469 Ense, Germany Tel: +49-2938-64-39990

Email: igbt-driver.sales@power.com

INDIA (New Dehli) #45, Top Floor

Okhla Industrial Area, Phase - III New Dehli, 110020 India Tel 1: +91-11-4055-2351 Tel 2: +91-11-4055-2353

Tel 2: +91-11-4055-2353 Email: indiasales@power.com

KOREA

RM602, 6FL, 22 Teheran-ro 87-gil, Gangnam-gu Seoul, 06164 Korea Tel: +82-2-2016-6610 Fax: +82-2-2016-6630 Email: koreasales@power.com

UNITED KINGDOM

Bulding 5, Suite 21 The Westbrook Centre Milton Road Cambridge, CB4 1YG United Kingdom

Tel: +44-7823-557-484 Email: <u>eurosales@power.com</u>

AMERICAS CENTRAL

333 Sheridan Road Winnetka, IL 60093 USA Tel: +1-847-721-6293 Email: usasales@power.com

CHINA (Shenzhen)

17/F, Hivac Building, No 2 Keji South 8th Road, Nanshan District

Shenzhen, 518057 China Tel: +86-755-8672-8689 Fax: +86-755-8672-8690 Email: chinasales@power.com

INDIA (Bangalore) #1, 14th Main Road

Vasanthangar Bangalore, 560052 India Tel 1: +91-80-4113-8020 Tel 2: +91-80-4113-8028 Fax: +91-80-4113-8023

Email: indiasales@power.com

ITALY

Via Milanese 20 20099 Sesto San Giovanni (MI), Italy

Tel: +39-02-4550-8708 Email: <u>eurosales@power.com</u>

SINGAPORE

51 Newton Road #19-01/05 Goldhill Plaza Singapore, 308900 Tel 1: +65-6358-2160 Tel 2: +65-6358-4480 Fax: +65-6358-2015

Email: singaporesales@power.com