



www.nemko.com

TEST REPORT IEC 60950-1 Information technology equipment - Safety -Part 1: General requirements Report Number. 246038 Date of issue: October 28, 2013 Total number of pages 11 Nemko A/S CB Testing Laboratory Address Gaustadalléen 30, NO-0373 Oslo, Norway Applicant's name..... Power Integrations, Inc. Manufacturer's name...... Power Integrations, Inc. Test specification: IEC 60950-1:2005 (Second Edition) + Am 1:2009 with Standard.....: CTL Decision, DSH 1080 Test procedure: **CB** Scheme Non-standard test method.....: N/A Test Report Form No. IEC60950_1C Test Report Form(s) Originator SGS Fimko Ltd Master TRF..... Dated 2012-08 Copyright © 2012 Worldwide System for Conformity Testing and Certification of Electrotechnical Equipment and Components (IECEE), Geneva, Switzerland. All rights reserved. This publication may be reproduced in whole or in part for non-commercial purposes as long as the IECEE is acknowledged as copyright owner and source of the material. IECEE takes no responsibility for and will not assume liability for damages resulting from the reader's interpretation of the reproduced material due to its placement and context. If this Test Report Form is used by non-IECEE members, the IECEE/IEC logo and the reference to the CB Scheme procedure shall be removed. This report is not valid as a CB Test Report unless signed by an approved CB Testing Laboratory and appended to a CB Test Certificate issued by an NCB in accordance with IECEE 02. Test item description: IC including capacitor discharge function (ICX) Trade Mark.....: CAPZero Manufacturer Power Integrations, Inc. Model/Type reference: CAP002DG; CAP003DG; CAP004DG; CAP005DG; CAP006DG; CAP007DG; CAP008DG; CAP009DG; CAP012DG; CAP013DG; CAP014DG; CAP015DG; CAP016DG; CAP017DG; CAP018DG; CAP019DG; SC1143 230V AC Ratings:

TRF No. IEC60950_1C

This Test Report, when bearing the Nemko name and logo is only valid when issued by a Nemko laboratory, or by a laboratory having special agreement with Nemko.



| Testing procedure and testing location: | | | |
|---|--|--------------------|--|
| CB Testing Laboratory: | Nemko A/S | | |
| Testing location/ address: | Gaustadalléen 30, NO-0373 Oslo, Norway | | |
| Associated CB Laboratory: | | | |
| Testing location/ address: | | | |
| Tested by (name + signature): : | Ole Morten Aaslund | Ole Morten Gastind | |
| Approved by (name + signature): | Hans-Eirik Lie | How for for | |
| Testing procedure: TMP | | | |
| Testing location/ address: | | | |
| Tested by (name + signature): | | | |
| Approved by (name + signature) : | | | |
| Testing procedure: WMT | | | |
| Testing location/ address: | | | |
| Tested by (name + signature): : | | | |
| Witnessed by (name + signature) : | | | |
| Approved by (name + signature): | | | |
| Testing procedure: SMT | | | |
| Testing location/ address: | | | |
| Tested by (name + signature) : | | | |
| Approved by (name + signature) : | | | |
| Supervised by (name + signature) : | | | |
| Testing procedure: RMT | | | |
| Testing location/ address: | | | |
| Tested by (name + signature) : | | | |
| Approved by (name + signature) : | | | |
| Supervised by (name + signature) : | | | |



List of Attachments (including a total number of pages in each attachment):

CTL Decision, DSH 1080 (2 pages) Photos (5 pages) Data sheet (8 pages) Application note (10 pages)

Summary of testing:

This report covers only tests applicable for IC including capacitor discharge function (ICX). Requirements for such components are covered by CTL Decision, DSH 1080, refer attachment.

The following clauses are not applicable for such components and are removed from this report: 1.5, 1.6, 1.7 (except for 1.7.1 and 1.7.11), 2.1 (except for 2.1.1.7), 2.2, 2.3, 2.4, 2.5, 2.6, 2.7, 2.8, 2.9 (except for 2.9.2), 2.10, 3.1, 3.2, 3.3, 3.4, 3.5, 4.1, 4.2, 4.3, 4.4, 4.5, 5.1, 5.2, 5.3 (except 5.3.7 and 5.3.9) and all Annexes.

However, all relevant clauses must be considered for end products using this ICX.

The following tests were performed as per DSH 1080:

- humidity treatment for 120 h at a temperature of (40±2)°C and a relative humidity of (93±3)%

Humidity treatment performed on models CAP002DG, CAP009DG, CAP012DG and CAP019DG, refer also clause 2.9.2 in this report.

- 100 positive impulses and 100 negative impulses between line and neutral using a capacitor with the largest capacitance and a resistor with the smallest resistance specified by the manufacturer of the ICX; and repeated with a capacitor with the smallest capacitance and the resistor with the largest resistance. The time between any two impulses shall not be less than 1 s. The impulse shall be as specified in circuit 2 of Table N.1 (60950-1) / 1.2/50µs in Table K.1 (60065), with Uc equal to the transient voltage.

Impulse tests as described performed on models CAP002DG, CAP009DG, CAP012DG and CAP019DG. Uc = 2500Vpeak. X-capacitor was only mounted during the discharge tests, refer General product information and 2.1.1.7.

- Application of an a.c. voltage that is 110% of the rated voltage for 2.5 minutes.

A voltage of 253V AC applied for 2.5 minutes on models CAP002DG, CAP009DG, CAP012DG and CAP019DG.

- 10 000 cycles of power on and off using a capacitor with the smallest capacitance and a resistor with the largest resistance as specified by the manufacturer of ICX. The power on and off cycles time shall not be less than 1 s.

10 000 cycles of power on and off (cycle time is 1 s) performed on models CAP002DG and CAP012DG.

If any of the associated circuitry components other than those critical for the discharge function fails, it may be replaces with a new component.

No components failed.

Compliance criteria:

Compliance is checked by evaluation of the available data or by conducting the above tests. The capacitor discharge test is conducted after above tests, ensuring the ICX or the EUT provided with the ICX continues to provide the safeguard function.

NOTE: Evaluation of available data should include information of failure of any associated circuitry components keeps the discharge modes in the on/stay mode.



Summary of testing (continued):

After above tests the capacitor discharge tests were performed according to clause 2.1.1.7 on models CAP002DG, CAP009DG, CAP012DG and CAP019DG. The circuit tested continue to comply with 2.1.1.7, refer 2.1.1.7 for details. Note that compliance with 2.1.1.7 must also be checked when the ICX forms part of an end product.

In addition to above tests, evaluation of available data from the manufacturer have been made to prove that the discharge function of the ICX remains the same also during single fault conditions. Refer general product information and clause 5.3.7 for details.

| Tests per | formed (name of test and test clause): | Testing location: |
|--|--|---|
| 1.7.11 2.1.1.7 2.9.2 | Durability (markings) Discharge of capacitors in equipment Humidity conditioning | Nemko A/S Gaustadalléen 30, NO-0373 Oslo, Norway |
| Summary of compliance with National Differences | | |
| Samples tested comply with the applicable requirements covered by CTL Decision, DSH 1080, attached | | |

Samples tested comply with the applicable requirements covered by CTL Decision, DSH 1080, attached to this report.

Copy of marking plate

The artwork below may be only a draft. The use of certification marks on a product must be authorized by the respective NCBs that own these marks.

(Additional requirements for markings. See 1.7 NOTE)

The following markings are printed on the body of the ICX:

- Power Integrations Logo
- Date code
- Part no.
- Serial no.



| Test item particulars | |
|---|---|
| Equipment mobility: | [] movable [] hand-held [] transportable [] stationary [x] for building-in [] direct plug-in |
| Connection to the mains: | [] pluggable equipment [] type A [] type B [] permanent connection [] detachable power supply cord [] non-detachable power supply cord [] not directly connected to the mains |
| | Must be evaluated in the end product. |
| Operating condition: | [x] continuous [] rated operating / resting time: |
| Access location: | [x] operator accessible [] restricted access location |
| Over voltage category (OVC): | [] OVC I [x] OVC II [] OVC III [] OVC IV [] other: |
| Mains supply tolerance (%) or absolute mains supply | |
| values: | |
| Tested for IT power systems | |
| | Not applicable for this type of component. |
| IT testing, phase-phase voltage (V) | 230V |
| Class of equipment | [] Class I [] Class II [] Class III [x] Not classified |
| Considered current rating of protective device as part of the building installation (A) | N/A |
| Pollution degree (PD) | [] PD 1 [x] PD 2 [] PD 3 |
| IP protection class | IP20 |
| Altitude during operation (m) | < 2000m |
| Altitude of test laboratory (m) | < 2000m |
| Mass of equipment (kg) | < 10g |
| Possible test case verdicts: | |
| - test case does not apply to the test object: | N/A |
| - test object does meet the requirement: | P (Pass) |
| - test object does not meet the requirement:: | F (Fail) |
| Testing | |
| Date of receipt of test item: | October 1, 2013 |
| Date(s) of performance of tests: | October 4 – October 18, 2013 |




| General remarks: | | | |
|--|--|--|--|
| The test results presented in this report relate only to the object tested. This report shall not be reproduced, except in full, without the written approval of the Issuing testing laboratory. "(see Enclosure #)" refers to additional information appended to the report. "(see appended table)" refers to a table appended to the report. Throughout this report a comma / point is used as the decimal separator. | | | |
| Manufacturer's Declaration per sub-clause 6.2.5 of | | | |
| The application for obtaining a CB Test Certificate includes more than one factory location and a declaration from the Manufacturer stating that the sample(s) submitted for evaluation is (are) representative of the products from each factory has been provided | | | |
| When differences exist; they shall be identified in the General product information section. | | | |
| Name and address of factory (ies) No. 351 Guo Shou Jing Rd., Z.J. Hi Tech Park Pudong New Area, Shanghai, 201203 CHINA | | | |



General product information:

The equipment under tests are IC including discharge function (ICX). It is used to cope with environmental issues, as it limits the power consumption in standby conditions. The ICX blocks current through X-capacitor discharge resistor when AC voltage is connected, and it automatically discharges X-capacitor trough discharge resistors when AC is disconnected.

Figure below shows a typical application for the ICX:

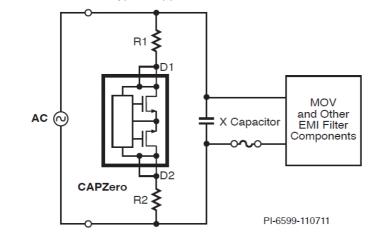

Models covered by this report are listed in table below. Models CAP002DG, CAP009DG, CAP012DG and CAP019DG were chosen to represent all models. During testing the ICX was mounted on a PCB together with a mains fuse (1A) and discharge resistors. Refer attached photos. X-capacitor was only mounted during the discharge tests, refer summary of testing and 2.1.1.7. Values of X-capacitor and discharge resistors are as per recommendation from the manufacturer. Refer table below.

| Model/Part No. (ICX) | BV _{DSS} | Maximum total X-capacitance | Total series resistance (R1+R2) |
|-------------------------|-------------------|--------------------------------|---------------------------------------|
| CAP002DG | 825V | <= 500nF | 1.5MΩ |
| CAP003DG | 825V | 750nF | 1.02MΩ |
| CAP004DG | 825V | 1µF | 780kΩ |
| CAP005DG | 825V | 1.5µF | 480kΩ |
| CAP006DG | 825V | 2µF | 360kΩ |
| CAP007DG | 825V | 2.5µF | 300kΩ |
| CAP008DG | 825V | 3.5µF | 200kΩ |
| CAP009DG | 825V | 5µF | 150kΩ |
| CAP012DG | 1000V | <= 500nF | 1.5MΩ |
| CAP013DG | 1000V | 750nF | 1.02MΩ |
| CAP014DG | 1000V | 1µF | 780kΩ |
| CAP015DG | 1000V | 1.5µF | 480kΩ |
| CAP016DG | 1000V | 2µF | 360kΩ |
| CAP017DG | 1000V | 2.5µF | 300kΩ |
| CAP018DG | 1000V | 3.5µF | 200kΩ |
| CAP019DG | 1000V | 5µF | 150kΩ |
| SC1143 | 1000V | 5µF | 150kΩ |

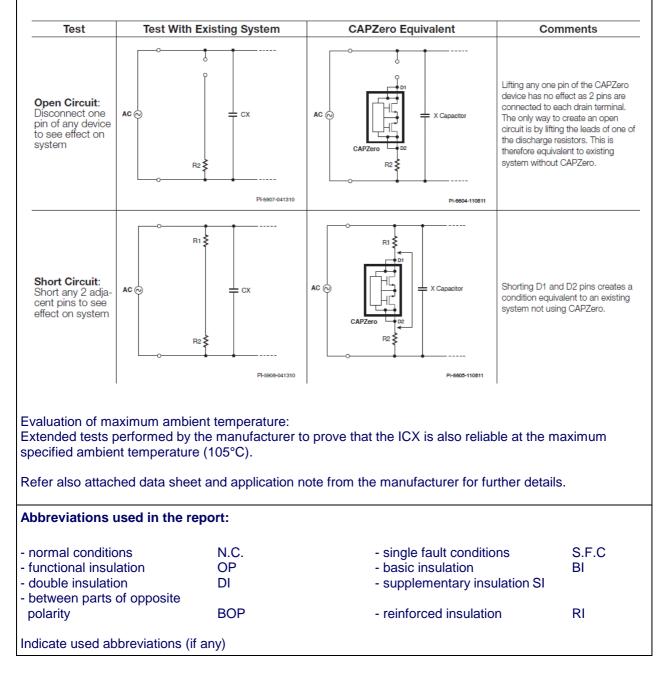


Table on previous page includes tolerances as referred to in the attached data sheet i.e. 5% for resistors and 20% for total capacitance.

Resistors R1+R2 shall be rated for 50% of the system input voltage to allow for the short-circuit of the ICX, D1 to D2 pins, during single fault test.

Evaluation of singe fault conditions (refer also clause 5.3.7):

The ICX has two dedicated pins for the D1 and D2 terminals which add redundancy during single fault testing (short-circuit or open-circuits). Thus if one pin is physically disconnected from the device or PCB, the ICX will continue to function normally. During a short-circuit the outcome is the same as if the ICX had not been used and results in the discharge resistors being connected in series continuously. Figure below summarizes the results of the worst case single fault tests.





| IEC 60950-1/Am1 | | | |
|-----------------|--------------------|-----------------|---------|
| Clause | Requirement + Test | Result - Remark | Verdict |

| 1.7.1 | Power rating and identification markings | The required marking is located on the outside surface of the component. | Ρ |
|---------|--|--|-----|
| 1.7.1.1 | Power rating marking | Refer below: | Р |
| | Multiple mains supply connections: | Must be considered when installed in the end product. | N/A |
| | Rated voltage(s) or voltage range(s) (V) | Rated nominal voltage is declared to be 230V AC. | Ρ |
| | Symbol for nature of supply, for d.c. only | AC supplied. | N/A |
| | Rated frequency or rated frequency range (Hz): | Must be considered when installed in the end product. | N/A |
| | Rated current (mA or A): | Must be considered when installed in the end product. | N/A |
| 1.7.1.2 | Identification markings | Refer below: | Р |
| | Manufacturer's name or trade-mark or identification mark | CAPZero | Ρ |
| | Model identification or type reference: | CAP002DG; CAP003DG; CAP004DG; CAP005DG; CAP006DG; CAP007DG; CAP008DG; CAP009DG; CAP012DG; CAP013DG; CAP014DG; CAP015DG; CAP016DG; CAP017DG; CAP018DG; CAP019DG; SC1143 | Ρ |
| | Symbol for Class II equipment only | Must be considered when installed in the end product. | N/A |
| | Other markings and symbols | The additional marking does not give rise to misunderstandings. | Ρ |
| | Language(s): | Must be considered when installed in the end product. | |
| 1.7.11 | Durability | The marking withstands required tests. | Ρ |



| | IEC 60950-1/Am1 | | |
|---------|--|--|---------|
| Clause | Requirement + Test | Result - Remark | Verdict |
| 2.1.1.7 | Discharge of conseitors in equipment | Conseitor discharge teste | Р |
| 2.1.1.7 | Discharge of capacitors in equipment | Capacitor discharge tests performed on models CAP002DG, CAP009DG, CAP012DG and CAP019DG after tests described in Summary of testing were perfomed. Refer test results below. Discharge tests must also be performed when the ICX forms part of an end product. | P |
| | Measured voltage (V); time-constant (s): | CAP002DG: Vpeak: 360V Vpeak, 37%: 133.2V Time-constant: 702ms CAP009DG: Vpeak: 348V Vpeak, 37%: 129V Time-constant: 796ms CAP012DG: Vpeak: 356V Vpeak, 37%: 132V Time-constant: 720ms CAP019DG: Vpeak: 360V Vpeak, 37%: 133.2V Time-constant: 796ms | |

| 2.9.2 | Humidity conditioning | Humidity treatment for 120 h performed. | Р |
|-------|--|---|---|
| | Relative humidity (%), temperature (°C): | 40°C, 91% | _ |



| | IEC 60950-1/Am1 | | |
|--------|----------------------|---|---------|
| Clause | Requirement + Test | Result - Remark | Verdict |
| 5.3.7 | Simulation of faults | The ICX has two dedicated pins for the D1 and D2 terminals which add redundancy during single fault testing (short-circuit or open- circuits). Thus if one pin is physically disconnected from the device or PCB, the ICX will continue to function normally. During a short- circuit the outcome is the same as if the ICX had not been used and results in the discharge resistors being connected in series continuously. Refer also figure in general product information.Extended surge tests performed by the manufacturer to maximize the voltage stress of the ICX. Tests showed that the ICX continued to function as intended even when exposed to surge levels far beyond its intended application. | P |

| 5.3.9 | Compliance criteria for abnormal operating and fault conditions | Refer 5.3.7 above. | Р |
|---------|---|--------------------|---|
| 5.3.9.1 | During the tests | - | Р |
| 5.3.9.2 | After the tests | - | Р |



DSH 1080

Report No. 246038

| | ECEE |
|--|------|
|--|------|

IEC System for Conformity Testing and Certification of Electrotechnical equipment and Components

CTL DECISION SHEET (DSH)


| | Subclause(s) | No. | Year |
|--|--|---|---|
| IEC 60950-1:2005 + A1:2009 (ed. 2.1) IEC 60065:2001 + A1:2005 + A2:2010 (ed. 7.2) | 2.1.1.7 9.1.6 | DSH 1080 | 2013 |
| Category | | | |
| OFF, TRON | | | |
| Subject | Keywords | Developed by | Approved at |
| Zero loss automatic X cap discharge | IC including capacitor discharge function (ICX) IC, capacitor discharge, Zero loss | ETF2 | 2013 CT Plenary Meeting |
| Question | | | • |
| How should an equipment with IC | ncluding a capacitor discharge | TUNCTION DE TESTE | a : |
| Decision | | | |
| | and the second state of the sta | | 41 4 4 - 1 1 |
| the ICX and the associated cir If discharge components exter the ICX tested separately com components external to the IC they shall be included in the | onents (such as varistors and G cuitry are disconnected. nal to the ICX are necessary, the plies with the requirements and t X are necessary: ne test; and | DT's) that attenua ey shall not fail du | ate the impulse to uring the tests; or |
| Any impulse attenuating comp the ICX and the associated cir If discharge components exter the ICX tested separately com components external to the IC they shall be included in the they shall not fail during the | onents (such as varistors and Gl cuitry are disconnected. nal to the ICX are necessary, the plies with the requirements and t X are necessary: ne test; and le tests; and | DT's) that attenua ey shall not fail du ests below. If dis | ate the impulse to iring the tests; or charge |
| Any impulse attenuating comp the ICX and the associated cir If discharge components exter the ICX tested separately com components external to the IC they shall be included in the they shall not fail during the | onents (such as varistors and Gl cuitry are disconnected. nal to the ICX are necessary, the plies with the requirements and f X are necessary: ne test; and te tests; and s used in the equipment shall be | DT's) that attenua ey shall not fail du cests below. If dis within the range t | ate the impulse to rring the tests; or charge tested |
| Any impulse attenuating comp the ICX and the associated cir If discharge components exter the ICX tested separately com components external to the IC they shall be included in the they shall not fail during the the discharge components <u>Tests</u> | onents (such as varistors and Gl cuitry are disconnected. nal to the ICX are necessary, the plies with the requirements and to X are necessary: ne test; and se tests; and s used in the equipment shall be the test set up shall be as recom | DT's) that attenua ey shall not fail du ests below. If dis within the range t mended by the I0 | ate the impulse to rring the tests; or charge tested CX manufacturer. |
| Any impulse attenuating comp the ICX and the associated cir If discharge components exter the ICX tested separately com components external to the IC they shall be included in the they shall not fail during the the discharge components Tests Where the ICX is tested by itself, humidity treatment for 120 h at of the largest capacitance and a of the ICX; and repeated with a largest resistance. The time be | onents (such as varistors and Gl cuitry are disconnected. nal to the ICX are necessary, the plies with the requirements and to X are necessary: ne test; and se tests; and s used in the equipment shall be the test set up shall be as recom | DT's) that attenua ey shall not fail du eests below. If dis within the range t mended by the IG a relative humidit and neutral using nee specified by the acitance and the ot be less than 1 s | ate the impulse to uring the tests; or charge tested CX manufacturer. y of (93±3)% g a capacitor with he manufacturer resistor with the s. The impulse |
| Any impulse attenuating comp the ICX and the associated cir If discharge components exter the ICX tested separately com components external to the IC they shall be included in the they shall not fail during the the discharge components Tests Where the ICX is tested by itself, humidity treatment for 120 h at 100 positive impulses and 100 the largest capacitance and a of the ICX; and repeated with a largest resistance. The time be shall be as specified in circuit 2 equal to the transient voltage. | onents (such as varistors and Gl cuitry are disconnected. nal to the ICX are necessary, the plies with the requirements and f X are necessary: ne test; and s used in the equipment shall be the test set up shall be as recom t a temperature of (40±2)°C and negative impulses between line resistor with the smallest resistant a capacitor with the smallest cap etween any two impulses shall no | DT's) that attenua ey shall not fail du rests below. If dis within the range t mended by the lu a relative humidit and neutral using actance and the bit be less than 1 s µs in Table K.1 (| ate the impulse to uring the tests; or charge tested CX manufacturer. y of (93±3)% g a capacitor with he manufacturer resistor with the s. The impulse |




DSH 1080

| IEC System for Conformity Testing and Certification of Electrotechnical equipment and Components | on |
|--|--------------------|
| 10 000 cycles of power on and off using a capacitor with the smallest capacitance and a resi with the largest resistance as specified by the manufacturer of ICX. The power on and off cyc time shall not be less than 1 s. | |
| If any of the associated circuitry components other than those critical for the discharge function it may be replaced with a new component | fails, |
| <u>Compliance criteria</u> Compliance is checked by evaluation of the available data or by conducting the above tests. Th capacitor discharge test is conducted after the above tests, ensuring the ICX or the EUT provid with the ICX continues to provide the safeguard function. | |
| NOTE: Evaluation of available data should include information of failure of any associated circu components keeps the discharge mode in the on/stay mode | uitry |
| Explanatory notes | |
| An ICX is introduced to cope with environmental issues. It limits power consumption in s conditions. | tandby |
| Product Highlights of ICX | |
| Blocks current through X-cap discharge resistor when AC voltage is connected Automatically discharges X-cap through discharge resistors when AC is disconnected | |
| Single fault condition (open circuit conditions) of the IC and associated circuitry components for the discharge function is the concern related to safety, when AC power is disconnected. capacitance of X-capacitors connected in the equipment is above a certain value, it would rest noncompliance with the requirements for plug discharge in IEC 60950-1 Clause 2.1.1.7 / IEC Clause 9.1.6. | If the ult in a |
| IEC TC108 HBSDT agreed to include requirements for IC including capacitor discharge function (ICX) to the FDIS for IEC 62368-1 ed2.0. The Decision above is in accordance with this. | n |
| Amd.2 to IEC 60950-1 ed2.0 and IEC 60065 ed8.0 (assumed to be the last updates to these s not include these requirements. IEC TC108 MT1/MT2 has therefore been asked to confirm th proposal. | |
| Recommendation by IEC TC108 MT1/MT2, 10 May 2013 | |
| The TC108 management discussed the issue and feels that the approach to use the requireme from the latest draft IEC 62368-1, edition 2 is very reasonable. It is also in line with the stateme the drafts of IEC 60065 and IEC 60950-1 that allow components and subassemblies to be used are evaluated according to IEC 62368-1. | nts in |
| | |
| | 2012 |
| CTL-OP 106 Ed 9.2 2/2 © IEC – IECEE 2013-05-23/24 | 2013 |




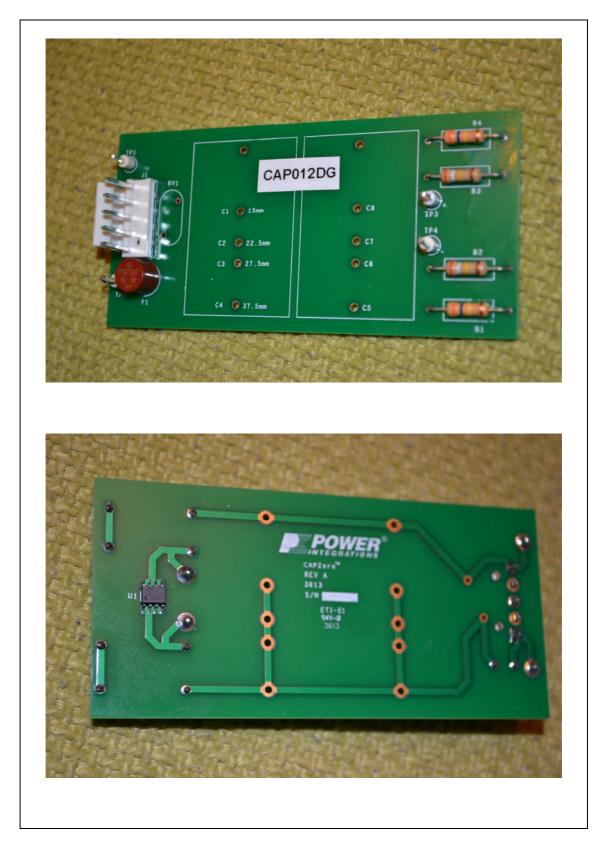




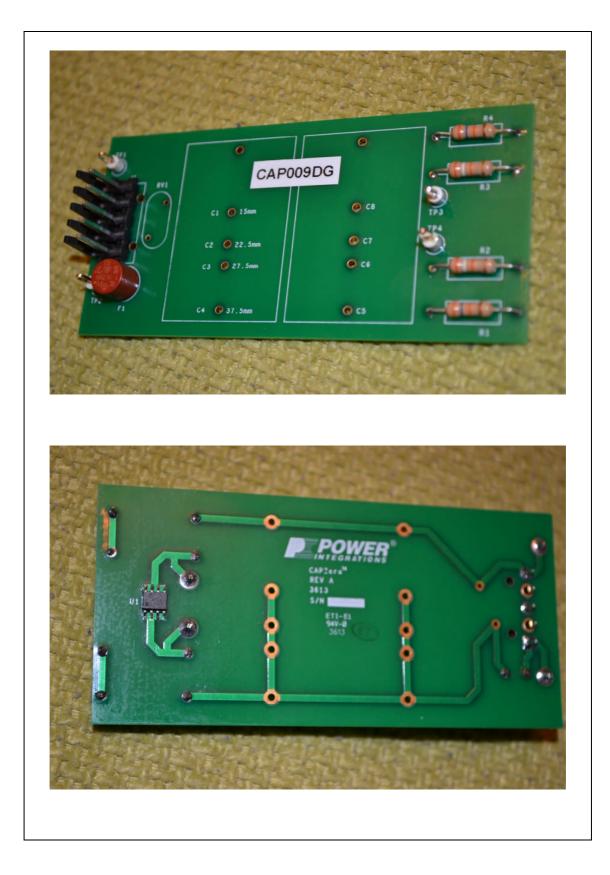




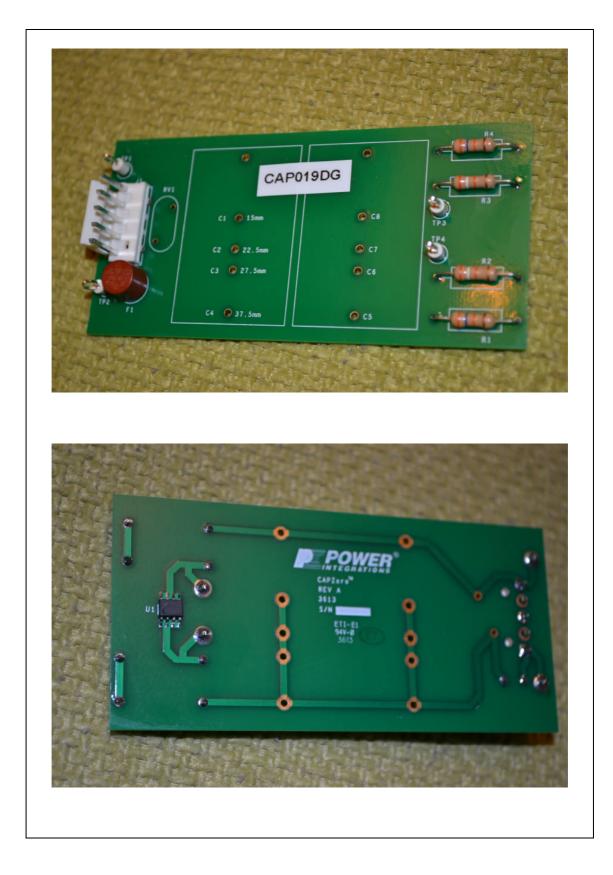



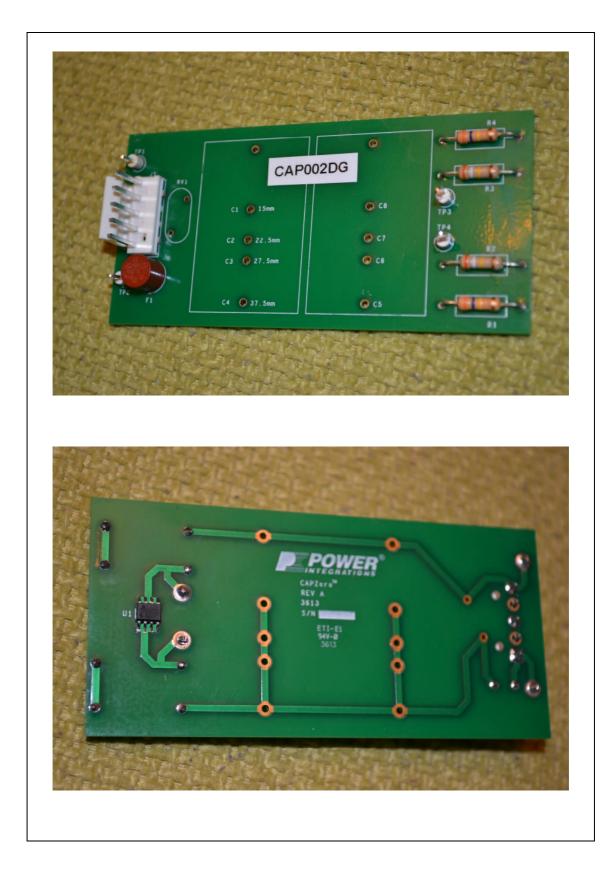



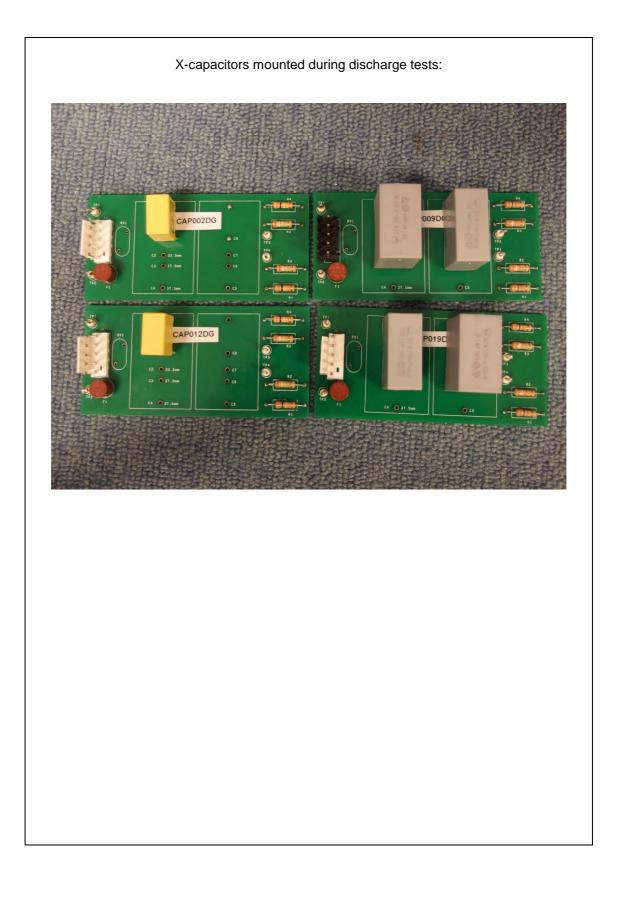



Report No. 246038

CAPZero[®] Family OWER Zero¹ Loss Automatic X Capacitor Discharge IC **Product Highlights** Blocks current through X capacitor discharge resistors when AC voltage is connected Automatically discharges X capacitors through discharge R1 ≶ resistors when AC is disconnected Simplifies EMI filter design - larger X capacitor allows smaller inductive components with no change in consumption Only two terminals - meets safety standards for use before or MOV and Other EMI Filter AC 心 after system input fuse X Capacitor >4 mm creepage on package and PCB Compone Self supplied – no external bias required High common mode surge immunity - no external ground . CAPZero connection · High differential surge withstand - 1000 V internal MOSFETs PI-6599-110711 EcoSmart[®] – Energy Efficient Figure 1. Typical Application – Not a Simplified Circuit <5 mW consumption at 230 VAC for all X capacitor values Applications All ACDC converters with X capacitors >100 nF Appliances requiring EuP Lot 6 compliance **Component Selection Table** · Adapters requiring ultra low no-load consumption Total Series All converters requiring very low standby power Maximum Total Product³ **BV**_{DSS} Resistance X Capacitance (R1 + R2) Description When AC voltage is applied, CAPZero blocks current flow in the CAP002DG 825 V ≤ 500 nF 1.5 MΩ X capacitor safety discharge resistors, reducing the power loss to CAP012DG 1000 V less than 5 mW, or essentially zerol at 230 VAC. When AC voltage is disconnected, CAPZero automatically discharges the CAP003DG 825 V 750 nF 1.02 MΩ

X capacitor by connecting the series discharge resistors. This operation allows total flexibility in the choice of the X capacitor to optimize differential mode EMI filtering and reduce inductor costs, with no change in power consumption. Designing with CAPZero is simply a matter of selecting the

appropriate CAPZero device and external resistor values in Table 1 for the X capacitor value being used. This design choice will provide a worst case RC time constant, when the AC supply is disconnected, of less than 1 second as required by international safety standards.

The simplicity and ruggedness of the two terminal CAPZero IC makes it an ideal choice in systems designed to meet EuP Lot 6 requirements.

The CAPZero family has two voltage grades: 825 V and 1000 V. The voltage rating required depends on surge requirement and circuit configuration of the application. See Key Applications Considerations section for details.

CAP013DG 1000 V CAP004DG 825 V 780 kΩ 1μF CAP014DG 1000 V CAP005DG 825 V 1.5 uF 480 kQ CAP015DG 1000 V CAP006DG 825 V 2μF 360 kΩ CAP016DG 1000 V CAP007DG 825 V 2.5 µF 300 kQ CAP017DG 1000 V CAP008DG 825 V 3.5 uF 200 kQ CAP018DG 1000 V CAP009DG 825 V 150 kΩ 5 µF CAP019DG 1000 V

Table 1. Component Selection Table.

IEC 62301 clause 4.5 rounds standby power use below 5 mW to zero.
 Values are nominal. RC time constant is <1 second with ±20% X capacitor and ±5% resistance from these nominal values.
 Packages: D: SO-8.

www.powerint.com

November 2011



Report No. 246038

CAPZero Family Pin Functional Description The pin configuration of Figure 2 ensures that the width of the SO-8 package is used to provide creepage and clearance distance of over 4 mm. D Package (SO-8) 8 ____ NC 0 Although electrical connections are only made to pins 2, 3, 6 and 7, it is recommended that pins 1-4 and pins 5-8 are coupled together on the PCB – see Applications Section. _____7 ____ D2 D1 🚞 6 ____ D2 D1 🗖 PI-5608-060810 Figure 2. Pin Configuration. POWER® v. D 11/1 www.powerint.com



Report No. 246038

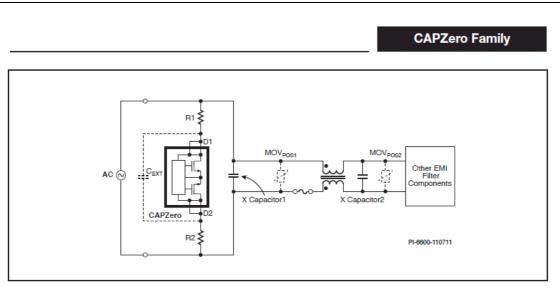


Figure 3. Placement Options of MOV and C_{ECT}

Key Application Considerations

Breakdown Voltage Selection

Figure 3 illustrates possible system configurations influencing the choice of CAPZero breakdown voltage. The system configuration variables include the placement of the system MOV and X capacitor(s) as well as the differential surge voltage specifications of the application.

As shown in Table 1, each device in the CAPZero family has a 825 V or 1000 V option. For applications where the system MOV is placed in position 1 (MOV_{POS1} in Figure 3), the 825 V option will typically provide adequate voltage withstand for surge requirements up to 3 kV or more. The 1 kV CAPZero would be recommended for higher surge requirements or if additional voltage margin is required.

For MOV placement that is not directly across the X Capacitor1 (for example $\mathrm{MOV}_{\mathrm{POS2}}$ in Figure 3) the 1000 V CAPZero devices can be used up to a surge specification of 1.5 kV. For differential surge voltage specifications of >1.5 kV it is recommended that the MOV is always placed in the location shown in Figure 3 as $\mathrm{MOV}_{\mathrm{POS1}}$.

It is always recommended that the peak voltage between terminals D1 and D2 of CAPZero is measured during surge tests in the final system. Measurements of peak voltage across CAPZero during surge tests should be made with oscilloscope probes having appropriate voltage rating and using an isolated supply to the oscilloscope to avoid ground currents influencing measurement results. When making such measurements, it is recommended that 50 V engineering margin is allowed below the breakdown voltage specification (for example 950 V with the 1000 V CAPZero). If the measured peak Drain voltage exceeds 950 V, an external 1 kV ceramic capacitor of value up to 47 pF can also be placed between D1 and D2 terminals to attenuate the voltage applied between the CAPZero terminals during surge. This optional external capacitor placement is shown as $C_{\rm Ext}$ in Figure 3. It should be noted that use of an external capacitor in this way will increase power consumption slightly due to the $C_{\rm Ext}$ charge/discharge currents flowing in R1 and R2 while AC is connected. A $C_{\rm Ext}$ value of 33 pF will add approximately 0.5 mW at 230 VAC, 50 Hz.

PCB Layout and External Resistor Selection

Figure 4 shows a typical PCB layout configuration for CAPZero. The external resistors in this case are divided into two separate surface mount resistors to distribute loss under fault conditions – for example where a short-circuit exists between CAPZero terminals D1 and D2. R1 and R2 values are selected according to Table 1.

Under a fault condition where CAPZero terminals D1 and D2 are shorted together, each resistor will dissipate a power that can be calculated from the applied AC voltage and the R1 and R2 values. For example in an application using CAP004 or CAP014, R1=R2=390 k Ω . If CAPZero is shorted out at 265 VAC R1 and R2 will each dissipate 45 mW.

Resistors R1 and R2 should also be rated for 50% of the system input voltage again to allow for the short-circuitry of CAPZero D1 to D2 pins during single point fault testing.

If lower dissipation or lower voltage across each resistor is required during fault tests, the total external resistance can be divided into more discrete resistors, however the total resistance must be equal to that specified in Table 1.







Report No. 246038

CAPZero Family

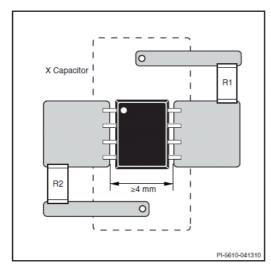


Figure 4. Typical PCB Layout.

Safety

CAPZero meets safety requirements even if placed before the system input fuse. If a short-circuit is placed between D1 and D2 terminals of CAPZero, the system is identical to existing systems where CAPZero is not used.

With regard to open circuit tests, it is not possible to create a fault condition through a single pin fault (for example lifted pin test) since there are two pins connected to each of D1 and D2. If several pins are lifted to create an open circuit, the condition is identical to an open circuit X capacitor discharge resistor in existing systems where CAPZero is not used. If redundancy against open circuit faults is required, two CAPZero and R1 / R2 configurations can be placed in parallel.

Discharge Operation

To meet the safety regulations, when the AC supply is disconnected, CAPZero will discharge the X capacitor to the safety extra low voltage (SELV) levels according to the above functional description. Although there are no specific safety requirements below SELV, CAPZero still continues the discharge until the X capacitor is fully discharged. As such CAPZero can be safely used at low input voltages such as the common industrial 18 VAC and 24 VAC supply rails while retaining X capacitor discharge when the AC source is disconnected.

-• Rev. D 11/11 


Report No. 246038

| Storage Temperature Lead Temperature ³ Operating Ambient Te | CAP002-CAP009 CAP012-CAP019 CAP002/CAP012 CAP003/CAP013 CAP004/CAP014 CAP005/CAP015 CAP006/CAP016 CAP007/CAP017 CAP008/CAP018 CAP009/CAP019 CAP009/CAP019 | | RAIN current is ously less thar n case for 5 se | allowed wi 400 V. conds. atings spec sing permar plute Maxim | hile the DRA ified may be hent damage hum Rating | AIN voltage e applied e to the conditions |
|--|---|--|---|---|---|--|
| Parameter | Symbol | Conditions T _A = -10 to 105 °C (Unless Otherwise Specified) | Min | Тур | Max | Units |
| Control Functions | | | | | | |
| Detection Time | t _{DETECT} | Line Cycle Frequency 47-63 Hz | | 22 | 31.4 | ms |
| | | CAP002/012 | 0.25 | | | ļ |
| | | CAP003/013 | 0.37 | | | - |
| | | CAP004/014 | 0.48 | | | - |
| Drain Saturation Current ^{a, B} | I _{DSAT} | CAP005/015 | 0.78 | | | mA |
| Surrent | | CAP006/016 | 1.04 | | | + |
| | | CAP007/017 | 1.25 | | | + |
| | | CAP008/018 | 1.88 | | | - |
| Supply Current | ISUPPLY | CAP009/019 T _A = 25 °C | 2.5 | | 21.7 | μA |
| resistor values spe | cified in Component | e a natural RC discharge characteristic a Eselection Table 1. acterization and design. | t all voltages u | p to 265 VA | NC pk with th | ne externa |




5 Rev. D 11/11



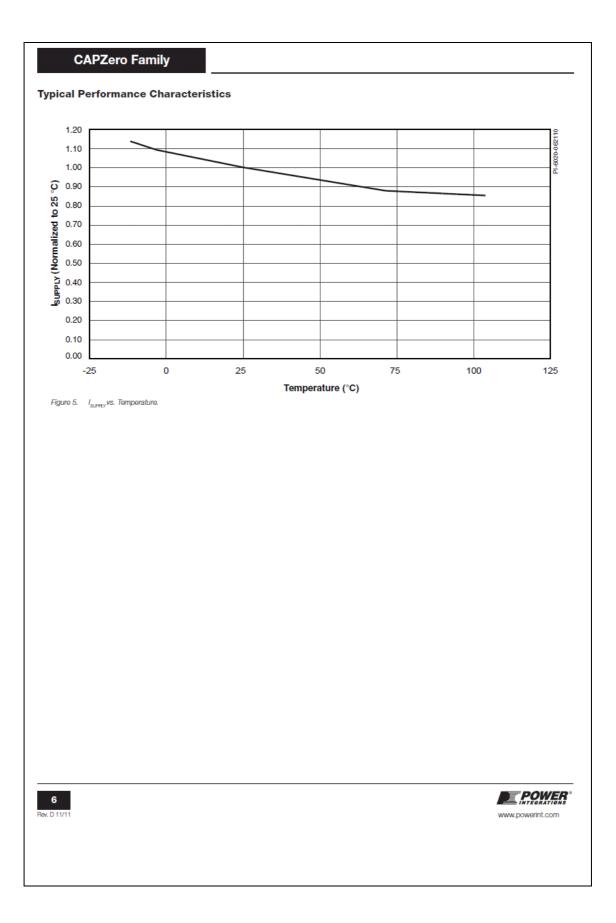



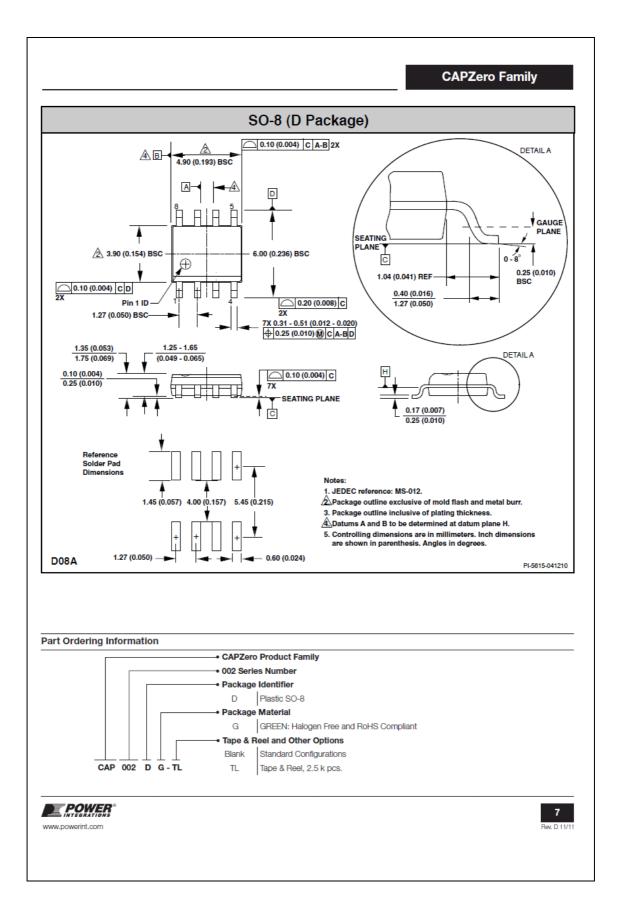



Report No. 246038

| Revision | Notes | Date |
|----------|--|----------|
| А | Code A release. | 04/14/10 |
| В | Updated I _{supply} condition. Added figure 5. Parameter T _{DETECT} was updated. | 06/08/10 |
| С | Updated Table 1. Updated Note 1 in Table 1. Added "Discharge Operation" paragraph. Updated Absolute Maximum Ratings Table. | 02/11 |
| С | Added Maximum Junction Temperature specification. | 04/11 |
| D | Updated Figures 1 and 3. | 11/07/11 |

For the latest updates, visit our website: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARBANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARBANTIES INCLUDING, WITHOUT LIMITATION. THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS.

Patent Information

The products and applications illustrated herein (including transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents, or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations patents may be found at www.powerint.com, Power Integrations grants its customers a license under certain patent rights as set forth at http://www.powerint.com/ip.htm.

LIFE Support Policy POWER INTEGRATIONS PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF POWER INTEGRATIONS. As used herein:

- A Life support device or system is one which, (i) is intended for surgical implant into the body, or (ii) supports or sustains life, and (iii) whose failure to perform, when properly used in accordance with instructions for use, can be reasonably expected to result in significant injury or death to the user.
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness

The PI logo, TOPSwitch, TinySwitch, LinkSwitch, DPA-Switch, PeakSwitch, CAPZero, SENZero, LinkZero, HiperPFS, HiperLCS, Qspeed, EcoSmart, Clampless, E-Shield, Filterfuse, StakFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2011, Power Integrations, Inc.

Power Integrations Worldwide Sales Support Locations

World Headquarters

5245 Hellyer Avenue San Jose, CA 95138, USA. Main: +1-408-414-9200 Customer Service: Phone: +1-408-414-9665 Fax: +1-408-414-9765 e-mail: usasales@powerint.com

China (Shanghai) Rm 1601/1610, Tower 1, Kerry Everbright City No. 218 Tianmu Road West, Shanghai, P.R.C. 200070 Phone: +86-21-6354-6323 Fax: +86-21-6354-6325 e-mail: chinasales@powerint.com Italy

China (ShenZhen) 3rd Floor, Block A, Zhongtou International Business Center, No. 1061, Xiang Mei Rd, FuTian District, ShenZhen, China, 518040 Phone: +86-755-8379-3243 Fax: +86-755-8379-5828 e-mail: chinasales@powerint.com

Germany Rueckertstrasse 3 D-80336, Munich Germany Phone: +49-89-5527-3910 Fax: +49-89-5527-3920 e-mail: eurosales@powerint.com Phone: +81-45-471-1021

India

#1, 14th Main Road Vasanthanagar Bangalore-560052 India Phone: +91-80-4113-8020 Fax: +91-80-4113-8023 e-mail: indiasales@powerint.com

Via De Amicis 2 20091 Bresso MI Italy Phone: +39-028-928-6000 Fax: +39-028-928-6009 e-mail: eurosales@powerint.com Japan Kosei Dai-3 Bldg. 2-12-11, Shin-Yokomana, Kohoku-ku Yokohama-shi Kanagwan 222-0033 Japan Fax: +81-45-471-3717 e-mail: japansales@powerint.com

Korea

BM 602, 6EL Korea City Air Terminal B/D, 159-6 United Kingdom Samsung-Dong, Kangnam-Gu, Seoul, 135-728, Korea Phone: +82-2-2016-6610 Fax: +82-2-2016-6630 e-mail: koreasales@powerint.com Applications Hotline

Singapore 51 Newton Road #15-08/10 Goldhill Plaza

Singapore, 308900 Phone: +65-6358-2160 Fax: +65-6358-2015 e-mail: singaporesales@powerint.com

Taiwan

5F, No. 318, Nei Hu Rd., Sec. 1 Nei Hu Dist. Taipei, Taiwan 114, R.O.C. Phone: +886-2-2659-4570 Fax: +886-2-2659-4550 e-mail: taiwansales@powerint.com

Furope HQ

1st Floor, St. James's House East Street, Farnham Surrey GU9 7TJ Phone: +44 (0) 1252-730-141 Fax: +44 (0) 1252-727-689 e-mail: eurosales@powerint.com

World Wide +1-408-414-9660

Applications Fax World Wide +1-408-414-9760



POWER

Application note

Report No. 246038

Application Note AN-48 CAPZero[™]Family

Design Considerations

Introduction

CAPZero is a family of self powered ICs designed to reduce the losses associated with the input filter capacitor discharge resistors when the AC voltage is present. Designed to be connected in series with existing discharge resistors each CAPZero device contains an integrated loss of AC detector and back-to-back MOSFETs in an SO-8 package.

When the AC input voltage is present, CAPZero remains in an OFF state, blocking current flow in the discharge path and eliminating power losses. When the AC is removed the CAPZero turns on, thereby switching in the resistors and allowing discharge of the input filter capacitance. CAPZero is self powered from the AC line with a power consumption of less than 5 mW at 230 VAC.

Given the small footprint of the package, it is possible to place the CAPZero IC on the bottom side of the printed circuit board (PCB) directly beneath the X capacitor. This eliminates the need for a major redesign of the PCB allowing existing designs to quickly benefit from reduced power consumption.

Background

Applications that contain off-line switching power electronics, for example motor drives, domestic appliances, industrial equipment and power supplies in general, have high voltage and high current switching waveforms that generate Electro Magnetic Interference (EMI).

To reduce this electro magnetic interference (EMI) a filter stage is included at the AC input (Figure 1). As part of this filter, capacitors are commonly placed directly across the AC input terminals to reduce differential mode EMI. Due to their location safety agency recognized X class capacitors are typically selected. X capacitors are rated to withstand the line surges that appear across the AC line with the numerical suffix indicating the specific voltage rating (X1, X2 or X3).


As the capacitor appears across the input terminals a voltage, up the peak of the incoming AC, can appear across the input prongs of the AC plug. This could potentially cause an electric shock to the user if touched or sparks should the prongs of the AC plug be shorted.


To prevent these risks once the supply is unplugged, safety agencies mandate that capacitance values above 100 nF be discharged automatically with a time constant of <1 second. Typically this is achieved by placing discharge resistors directly across the capacitor. The value of the resistance is selected to meet the 1 second time constant requirement and two resistors


www.powerint.com

are usually connected in series to meet safety agency single point failure testing. Should one resistor become shorted then the presence of the second prevents a short circuit across the AC input.

The presence of discharge resistors results in a constant power loss while AC is applied. With more stringent no-load and standby input power requirements, this power loss has become a significant portion of the overall power budget. For example, a power supply that uses a capacitance of 1 μ F across the incoming AC will require a maximum discharge resistance value of 1 M Ω which dissipates 53 mW at 230 VAC independent of the output load. Figure 2 shows typical dissipation in the discharge resistors as a function of the X capacitor value with a 0.75 second RC time constant. The value of 0.75 seconds provides margin to account for capacitor and resistor tolerances such that the maximum time constant is <1 second.

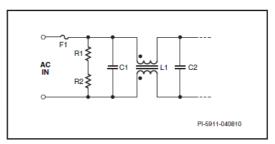

 

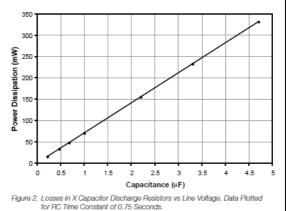

December 2011



AN-48

Application note

Report No. 246038

Application Note

Quick Start

Step - 1 Selecting the Correct CAPZero Device Size and **Discharge Resistor Value**

Select CAPZero device and discharge resistors from Table 1 based on the total input stage capacitance. Table 1 accounts for 5% tolerance of resistors and a 20% tolerance of the total capacitance by using a RC time constant of 0.75 seconds.

| Product | BV | Max Total X Capacitance | Total Series Resistance (R1 + R2) | |
|----------|--------|----------------------------|---|--|
| CAP002DG | 825 V | 500 pF | | |
| CAP012DG | 1000 V | 500 nF | 1.5 MΩ | |
| CAP003DG | 825 V | 750 nE | 1.02 MQ | |
| CAP013DG | 1000 V | 750 hF | 1.02 MΩ | |
| CAP004DG | 825 V | 4.5 | 780 kΩ | |
| CAP014DG | 1000 V | 1 μF | | |
| CAP005DG | 825 V | 1.5 μF | 480 kΩ | |
| CAP015DG | 1000 V | | | |
| CAP006DG | 825 V | 2 µF | 360 kΩ | |
| CAP016DG | 1000 V | | | |
| CAP007DG | 825 V | 0.5 | 300 kΩ | |
| CAP017DG | 1000 V | 2.5 μF | | |
| CAP008DG | 825 V | 05.5 | 200 10 | |
| CAP018DG | 1000 V | 3.5 μF | 200 kΩ | |
| CAP009DG | 825 V | E E | 150 kQ | |
| CAP019DG | 1000 V | 5 μF | 150 KΩ | |

Step 2 – Selecting the Appropriate CAPZero Voltage Rating CAPZero is available in two voltage ratings, 825 V and 1 kV. The 825 V rating is ideal for most consumer applications with

Metal Oxide Varistor (MOV) located in position 1 (see Figure 5 for $\rm MOV_{\rm posi}),$ where the differential line surge requirement is up to 3 kV. CAPZero devices with a 1 kV rating are applicable for <1 kV level without MOV, and for >3 kV with MOV at position 1 together with an optional external ceramic capacitor C_{ext} to lower the surge stress voltage. For applications with no MOV for >1 kV and up to 3 kV level, either a 825 V or 1 kV rated part can be used depending on measured surge voltage across the CAPZero together with an external ceramic capacitor C_{EXT} of up to 47 pF.

| | | | altana | |
|--------------|--|---------------------------------------|--|---------------------------------------|
| Differential | CAPZero V | | onage | Comments |
| Mode | MOV | MOV _{POS2} | No MOV | Comments |
| <1 kV | 82 | 5 V | 1000 V | |
| 1 to 1.5 kV | 825 V | 1000 V | 825 V or 1000 V with C _{EXT} | C _{EXT} up to 47 pF, 1 kV |
| 1.5 to 3 kV | 825 V | 825 V or 1000 V with C _{EXT} | | increases |
| >3 kV | 825 V or 1000 V + C _{EXT} (option) | Not Recommended | | Drain voltage margin |

Table 2. Selection of CAPZero Voltage Ratings vs Differential Surge Withstand Requirement. See Figure 5 for MOV position.

Tips for Design

Recommended Circuit Locations for CAPZero

For differential surge levels above 1 kV the use of a MOV is recommended. The presence of the MOV substantially reduces the voltage stress on both the X capacitor as well as the CAPZero. This can be seen from Figure 3 which shows the maximum voltage across the CAPZero device with differential surge voltages ranging from 1 kV to 3 kV.

Table 1. Component Selection Table.

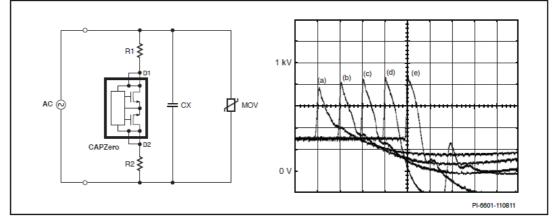


Figure 3. Recommended Position of CAPZero for a Single Stage EMI Filter. Waveforms Show Peak Voltage Across CAPZero in Presence of MOV. 200 V / Division and Time Base = 50 µs / div. Waveforms (a) Through (a) Represent Voltage Measured Across the CAPZero Device Under Differential Mode Input Surge Voltages of 1, 1.5, 2, 2.5 and 3 kV Respectively. MOV Used was 14 mm 275 VAC.



POWER www.powerint.com



Report No. 246038

AN-48

Application Note

As large currents flow through the MOV when it is clamping there can be significant voltage drops across filter components in the input stage. Therefore it is recommended that the CAPZero be located close to the MOV to minimize the voltage across the device during differential surge events. For designs where the MOV is placed at the input side of the power supply (Figure 3), before any inductive filter components, the CAPZero can be placed directly underneath the X capacitor. For designs where the MOV is placed after a common-mode choke, differential choke or other EMI filter components (Figure 4), it is recommended that if possible the CAPZero also be placed after the common mode choke and be physically close to the MOV allowing the 825 V device to be used up to 3 kV differential surge. If CAPZero cannot be placed after the common mode choke, the 1000 V device is recommended up to a surge level of 1.5 kV. For surge levels greater than 1.5 kV, it is always recommended to have the MOV located on the same side of the common-mode choke as the CAPZero.

One exception is if the X capacitor is on the AC input side of a system input fuse. In these cases if the X capacitor is greater than 100 nF, to meet safety requirements, the CAPZero must typically also be placed before the system input fuse directly across the X capacitor and voltage ratings. CAPZero is designed to meet safety requirements in this position – see 'Safety Considerations' section below.

Adding an External Parallel Capacitor to Reduce CAPZero Voltage Stress

While the use of a MOV is recommended, an external capacitor $C_{\rm Ext}$ (Figure 5) may be placed across the CAPZero to reduce surge voltage stress and may be sufficient in some design. This capacitor does not have to be an X class type, since it is not directly placed across the AC input terminals, but should be rated at or above the CAPZero being used. Figure 6 shows the effect of adding external capacitance directly across a CAPZero device in a design without a MOV. With no external capacitor at

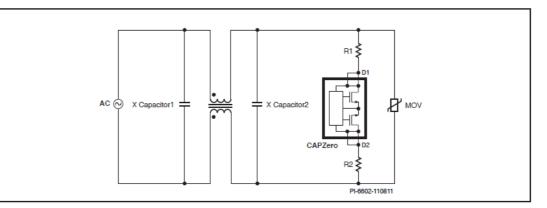


Figure 4. Recommended Location of CAPZero for a Two Stage EMI Filter With a MOV Located After Input Common Mode Choke.

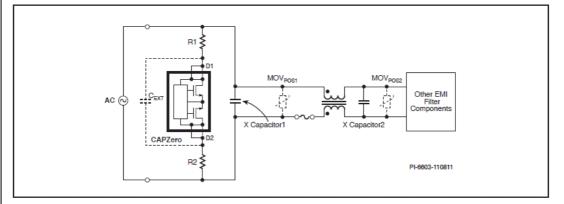


Figure 5. The Addition of an External Capacitor Across the CAPZero can Reduce Voltage Stress Across the Device During a Surge Event.

POWER INTEGRATIONS

www.powerint.com



Report No. 246038

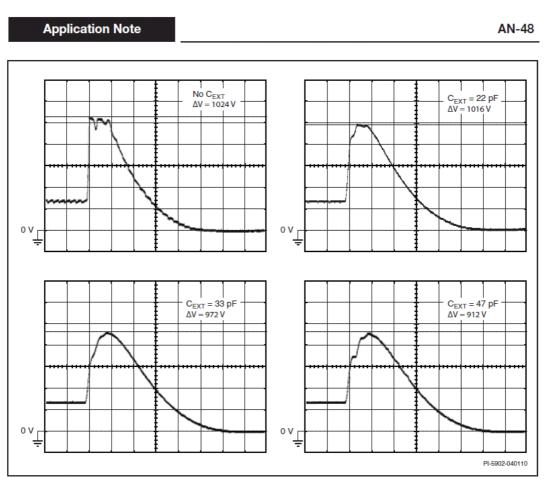


Figure 6. External Capacitor Placed Across CAPZero May Reduce Peak Voltage During Surge Event. No MOV present, 1.5 kV surge. 200 V / div., Time Base = 50 µs / div.

a 1.5 kV surge level, the CAPZero device exceeds its $\rm BV_{\rm DSS}$ rating however as the value of $\rm C_{\rm EXT}$ is increased to voltage level reduces.

Recommended values of C_{EXT} are between 22 pF and 47 pF. The use of 47 pF capacitor is not recommended in applications where the ambient temperature is in excess of 85 °C. Values above 47 pF are not recommended.

The presence of the external capacitor can for example reduce the voltage stress on the CAPZero by up to 100 V with 2 x 390 k Ω external resistors (1 μ F X capacitor) and 47 pF C_{EXT} . It should be also noted that the use of C_{EXT} will cause a slight increase in no load power consumption.

Measuring Device Voltage Stress

To measure the voltage stress across the CAPZero IC during differential line surge testing, it is recommended that the CAPZero be placed such that one terminal (D1 or D2) is connected to AC neutral. This reduces any effects due to common-mode noise. The area between the oscilloscope probe tip and the ground lead should be minimized. Finally it is necessary to float the oscilloscope or to use a battery powered oscilloscope while performing the surge tests. Please note that if using a floating scope proper care must be exercised as the scope chassis will assume high potential with respect to earth ground.



www.powerint.com



Report No. 246038

AN-48

| Class | Differential Mode Surge | Common Mode Surge | Comments |
|-------|----------------------------|-------------------------|---|
| | $Z_{OUT} = 2 \Omega$ | Z _{out} = 12 Ω | |
| 1 | No requirement | 0.5 kV | Protected environment |
| 2 | 0.5 KV | 1 KV | Electrical environment where cables are well separated |
| 3 | 1 KV | 2 KV | Electrical environment where cables (power and elec- tronic) run in parallel (residen- tial environment) |
| 4 | 2 KV | 4 KV | Electrical environment where cables (power and elec- tronic) run in parallel (industrial environment) |
| 5 | >2 KV | >4 KV | Severe surge environment (rural/sparsely populated areas) |

Table 3. Surge Voltage Levels.

Ensure that the surge voltage measured across the CAPZero device is less than its ${\rm BV}_{\rm nss}$ rating.

Surge Severity

The severity of the surge signal is defined in the IEC61000-4-5 standard published by the International Electrotechnical

Application Note

Commission (IEC). The surge voltage levels are described in Table 3 depending on the operating environment of the power supply.

Certain applications may require surge levels higher than those described in Class 4. For surge voltages greater than 3 kV the use of external capacitors across the CAPZero will help reduce voltage stress across its terminals by a few hundreds of volts as discussed above. It should be noted that at higher surge voltages the energy involved is very high and the MOV should be appropriately selected to handle this excess energy. Varistors have a energy rating which should exceed the applied energy to the system to ensure that this energy can be safely absorbed by the MOV.

Use in DC Input Environments

Since CAPZero relies on detecting the AC voltage at the input, under DC input the CAPZero will remain on all the time. This is a perfectly acceptable mode of operation for CAPZero although this operation will remove any energy savings from the use of CAPZero.

Use with Uninterruptable Power Supplies (UPS)

UPS systems often have a pseudo square wave output waveform, which although AC in nature are not sinusoidal. CAPZero can accept this type of input waveform.

Safety Considerations and Single Point Failure Testing

As with all offline power supplies, all safety requirements must

| Test | Test With Existing System | CAPZero Equivalent | Comments |
|--|---------------------------|--------------------|---|
| Open Circuit: Disconnect one pin of any device to see effect on system | | AC O | Lifting any one pin of the CAPZero device has no effect as 2 pins are connected to each drain terminal. The only way to create an open circuit is by lifting the leads of one of the discharge resistors. This is therefore equivalent to existing system without CAPZero. |
| | PI-5007-041310 | PI-6604-110811 | |
| Short Circuit: Short any 2 adja- cent pins to see effect on system | AC (%) | AC CAPZERO | Shorting D1 and D2 pins creates a condition equivalent to an existing system not using CAPZero. |
| | PI-5008-041310 | PI-5605-110811 | |

Table 4. Single Point of Failure (SPOF) Tests as Pertaining to Failure Modes of CAPZero. CAPZero Passes Both Tests.



www.powerint.com





Report No. 246038

Application Note

still be met when including CAPZero. To achieve this CAPZero has two dedicated pins for the D1 and D2 terminals which add redundancy during single point of failure testing (pin short / pin open testing). Thus if one pin is physically disconnected from the device or PCB, the IC will continue to function normally. During pin shorting the outcome is the same as if CAPZero had not been used and simply results in the discharge resistors being connected in series continuously; a safe condition. Table 4 summarizes the results of single point fault testing.

Accurate Measurement of No-load Input Power

X capacitors do not consume real power but they to cause a substantial reactive current to flow from the AC source. This reactive current leads to real power loss in the cables that connect the power supply to the AC source and power meter as shown in Figure 7. This cable loss can cause inaccurate measurements of no-load and light load input power. Normally the consumption of the discharge resistors is much larger as compared to this loss. However when CAPZero is used, and this loss is eliminated, the cable loss may become the most dominant component of no-load losses.

Also, at such low levels of input power, the leakage current of the MOV must also be considered. Typically this leakage current is approximately 10 μA and is large enough to increase no-load consumption by 1 – 2 mW at 265 VAC.

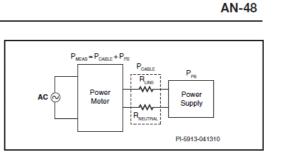



Figure 7. Measured Power can be Misleading Due to Significant RMS Current Resulting in Measurable Power Loss in Cables.

To measure the power consumption of a CAPZero IC, the X capacitor and the MOV (if used) should therefore be physically disconnected from the circuit.

Also ensure that the power meter is configured such that the current drawn by the voltage sensing element is not included in the measurement.

CAPZero Selection for Different X Capacitor Discharge Time Constants

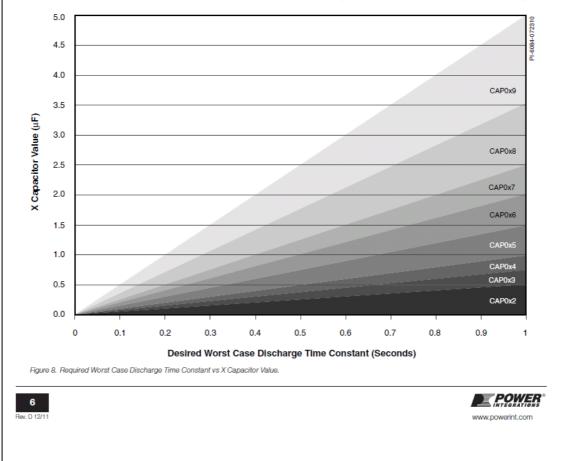In cases where a faster discharge time constant is required the curves of Figure 8 can be used to the select CAPZero for worst case discharge time constants and X capacitor values ranging





Report No. 246038

Application Note

AN-48


from 0 to 5 uF. Although safety standards do not generally require discharge resistors for X capacitors values up to 100 nF, data to zero capacitance is included for completeness.

The use of the curves is best demonstrated by an example. Referring to Figure 9, an example is illustrated for a 680 nF X capacitor with a desired worst case discharge time constant of 0.5 seconds. The solid arrows illustrate how the intersection of the 680 nF (on Y axis) and 0.5 seconds (on X axis) provide the CAP0x5 as the correct device. The dotted lines shows the CAP0x3 recommendation as provided on the data sheet which assumes a worst case discharge time constant of 1 second.

The discharge resistor value can be determined from Table 1 based on the required CAPZero. In this example, the CAP0x5

external discharge resistance is 480 k Ω . This choice of external resistance will actually provide a worst case discharge time constant of about 0.45 seconds as illustrated by the dotted arrow in Figure 9. Since this has no impact on the power consumption, it is recommended to use the Table 1 resistor choice for simplicity.

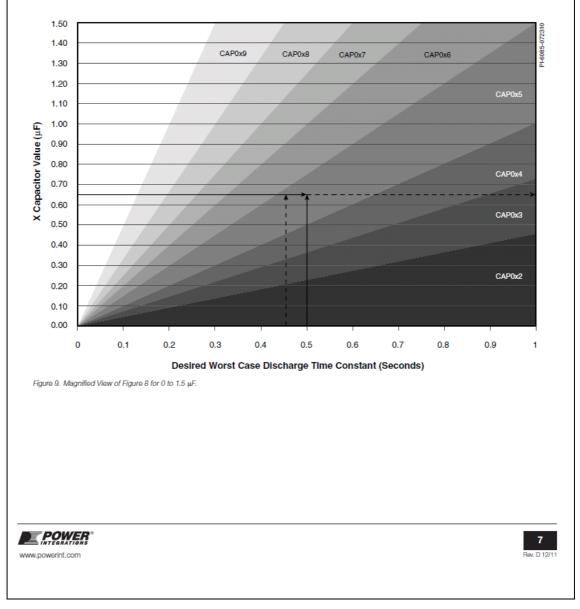Note that the Y axis of Figures 8 and 9 are the typical X capacitor value. However, the CAPZero recommendations allow for worst case X capacitor and discharge resistor tolerances to provide a worst case discharge time constant as shown on the X axis. Typical discharge time constants will be -30% lower than this.





Report No. 246038

Application Note

AN-48

www.powerint.com

Use of CAPZero for AC Line Voltage Zero-Crossing Detection

Any CAPZero can be used for AC line voltage zero-crossing detection when an AC voltage is present. At the same time it can be used as an X capacitor discharging circuit when the AC voltage is removed. The zero-crossing detection circuit uses CAPZero supply current with no additional power consumption in a non-isolated system (it consumes slightly more power when detector circuit is used in an isolated system).

A simple example of CAPZero used as a zero-crossing detector in a non-isolated application is shown in Figure 10. The zerocrossing signal is generated by a low voltage Zener diode (VR1) which is placed in between the CAPZero device and the AC neutral. The voltage across the Zener is used to drive a small signal MOSFET thereby obtaining the zero crossing signal. Figure 11 shows an example where the zero crossing detection circuit is required with isolation from the input line. While the concept of generating the signal remains the same, an optocoupler and a bias supply are required for isolation.


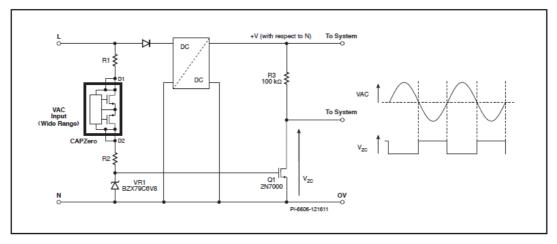


Figure 10. Example of CAPZero for AC Line Voltage Zero-Crossing Detection in a Non-Isolated System.

8

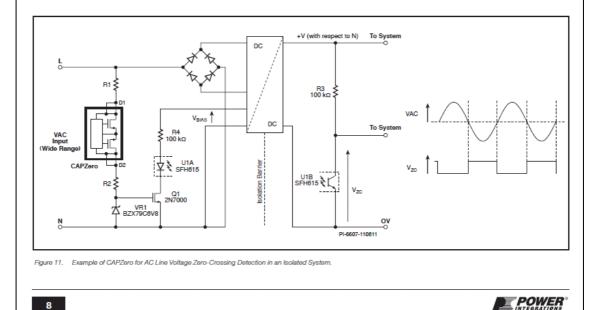



Application note Report No. 246038

| AN-48 | Application Note |
|-----------------|------------------|
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| POWER | 9 |
| ww.powerint.com | Rev. D 12/11 |
| | |
| | |
| | |
| | |



Report No. 246038

Revision Notes

С

D

Initial Release в Updated Surge Application Information. Added Discharge Resistor Selection Information 04/14/10 07/28/10 9/28/10 12/16/11

Date

Updated Figures 3, 4, 5 and Table 4. Added ZCD section.

Updated Step 2 paragraph and Table 2 on page 2.

For the latest updates, visit our website: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS.

Patent Information

The products and applications illustrated herein (including transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents, or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations patents may be found at www.powerint.com. Power Integrations grants its customers a license under certain patent rights as set forth at http://www.powerint.com/ip.htm.

LIFE SUPPORT POLICY POWER INTEGRATIONS PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF POWER INTEGRATIONS. As used herein:

- 1. A Life support device or system is one which, (i) is intended for surgical implant into the body, or (ii) supports or sustains life, and (iii) whose failure to perform, when properly used in accordance with instructions for use, can be reasonably expected to result in significant injury or death to the user
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness

The PI logo, TOPSwitch, TinySwitch, LinkSwitch, DPA-Switch, PeakSwitch, CAPZero, SENZero, LinkZero, HiperPFS, HiperTFS, HiperLCS, Aspeed, EcoSmart, Clampless, E-Shield, Filterfuse, StakFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2011, Power Integrations, Inc.

Power Integrations Worldwide Sales Support Locations

World Headquarters

5245 Hellyer Avenue San Jose, CA 95138, USA. Main: +1-408-414-9200 Customer Service: Phone: +1-408-414-9665 Fax: +1-408-414-9765 e-mail: usasales@powerint.com

China (Shanghai) Rm 1601/1610, Tower 1, Kerry Everbright City No. 218 Tianmu Road West, Shanghai, P.R.C. 200070 Phone: +86-21-6354-6323 Fax: +86-21-6354-6325 e-mail: chinasales@powerint.com

China (ShenZhen)

3rd Floor, Block A Zhongtou International Business Center, No. 1061, Xiang Mei Rd, FuTian District, ShenZhen, China, 518040 Phone: +86-755-8379-3243 Fax: +86-755-8379-5828 e-mail: chinasales@powerint.com Germany Rueckertstrasse 3 D-80336, Munich Germany Phone: +49-89-5527-3910 Fax: +49-89-5527-3920 e-mail: eurosales@powerint.com

India

#1, 14th Main Road Vasanthanagar Bangalore-560052 India Phone: +91-80-4113-8020 Fax: +91-80-4113-8023 e-mail: indiasales@powerint.com

20091 Bresso MI Italy Phone: +39-028-928-6000 Fax: +39-028-928-6009 e-mail: eurosales@powerint.com

Japan Kosei Dai-3 Bldg. 2-12-11, Shin-Yokomana, Kohoku-ku Yokohama-shi Kanagwan 222-0033 Japan Phone: +81-45-471-1021 Fax: +81-45-471-3717 e-mail: japansales@powerint.com

Korea RM 602, 6FL

Korea City Air Terminal B/D, 159-6 Samsung-Dong, Kangnam-Gu, Seoul, 135-728, Korea Phone: +82-2-2016-6610 Fax: +82-2-2016-6630 e-mail: koreasales@powerint.com

Singapore 51 Newton Road

#15-08/10 Goldhill Plaza Singapore, 308900 Phone: +65-6358-2160 Fax: +65-6358-2015 e-mail: singaporesales@powerint.com

Taiwan 5F, No. 318, Nei Hu Rd., Sec. 1 Nei Hu Dist. Taipei, Taiwan 114, R.O.C. Phone: +886-2-2659-4570 Fax: +886-2-2659-4550 e-mail: taiwansales@powerint.com

Europe HQ

1st Floor, St. James's House East Street, Farnham Surrey GU9 7TJ United Kingdom Phone: +44 (0) 1252-730-141 Fax: +44 (0) 1252-727-689 e-mail: eurosales@powerint.com

Applications Hotline World Wide +1-408-414-9660

Applications Fax World Wide +1-408-414-9760

Italy Via De Amicis 2